



**ON Semiconductor®**

# Half-Bridge Drivers A Transformer or an All-Silicon Drive?

# Agenda


- Topologies using a half-bridge configuration
- The difference between soft and hard-switching
- The gate-drive transformer
- The all-silicon-solution
- Comparison
- Conclusions

# Agenda


- Topologies using a half-bridge configuration
- The difference between soft and hard-switching
- The gate-drive transformer
- The all-silicon-solution
- Comparison
- Conclusions
 
# Topology Trend for High Efficiency

- Hard Switching
  - Flyback
  - Forward
  - 2-sw flyback
  - 2-sw forward
  - Full bridge




LLC-HB

 

- Soft Switching
  - LLC-HB resonant
  - Active clamp forward
  - Active clamp flyback
  - Asymmetrical half-bridge
  - Full bridge with phase shift
 
# The High-Side Switch

- To achieve high efficiency, the topologies with ZVS (Zero-Voltage Switching) behavior are preferred.
- All the soft switching topologies implement the power switch with floating reference pin, e.g. the source pin of MOSFET.
- Why are MOSFETs used in soft switching applications?
  - High frequency operation
  - Body diode (current loop for ZVS)




How to drive the high side MOSFET?


# Agenda

- Topologies using a half-bridge configuration
- The difference between soft and hard-switching
- The gate-drive transformer
- The all-silicon-solution
- Comparison
- Conclusions

# Turn-on Procedure for Hard-switching

 

 
The miller plateau is caused by  $C_{GD}$




- Stages 2 and 3 dominate the switching losses of MOSFET and driver.
- DRV's source capability as  $V_{GS}$  is around  $V_{GS,Miller}$  is important.

# Turn-off Procedure for Hard-switching

The Miller plateau

 


 The miller plateau is caused by  $C_{GD}$




- Stages 2 and 3 dominate the switching losses of MOSFET and driver.
- DRV's sink capability as  $V_{GS}$  is around  $V_{GS,Miller}$  is important.

# Simulation Circuit of Flyback

 


- Simulate the  $V_{GS}$ ,  $V_{DS}$ , and  $I_{DS}$  on Flyback.

# Turn-on Simulation of Flyback

 


- $V_{GS}$  rises with Miller effect.

# Turn-off Simulation of Flyback

 


- Turn off with Miller effect.

# Turn-on Procedure for Soft-switching

 


- Because of ZVS, there is no Miller effect as turning on.
- The switching losses are dominated by
  - The dead time (to reduce  $S_1$ ), and
  - Source capability to charge  $C_{GS}$  to reduce  $S_2$
- Less driver capability requirement.

# Turn-off Procedure for Soft-switching

 


- Similar as hard-switching: The Miller plateau exists as turning off.
- The difference is that  $I_{DS}$  also reduces at this duration since  $I_{DS}$  will go through the opposite MOSFET as  $V_{DS}$  changes.
- To avoid overlap between 2 MOSFETs, minimize the duration of  $S_1 \sim S_4$ .
- Strong DRV's sink capability is needed.

# Simulation Circuit of LLC-HB

 


- Simulate the  $V_{GS\_MU}$ ,  $V_{DS\_MU}$ , and  $I_{MU}$  on LLC-HB
- To ease the reading of current, the direction of  $I_{MU}$  and  $I_{ML}$  is referred to  $I_{CS}$ .

# Turn-on Simulation of LLC-HB

 

- $V_{GS\_ML}$  off,  $I_{CS}$  reduces  $V_{DS\_MU}$  for ZVS.
- $V_{DS\_MU}$  is 0 V BEFORE  $V_{GS\_MU}$ , so  $V_{GS\_MU}$  rises smoothly.

# Turn-off Simulation of LLC-HB

 

- Strong turn off capability is required.

# Driver Comparison between Hard-Switching and Soft-Switching

	Hard-switching	Soft-switching
Source capability requirement	Medium	Low
Sink capability requirement	High	High
Dead time accuracy requirement	Accurate	Accurate

# The Solutions for High-Side Driver

- Transformer-based solution
  - Single DRV input
  - Dual DRV inputs
- Silicon integrated circuit driver: dual outputs
  - Single DRV input
  - Dual DRV inputs


# Agenda

- Topologies using a half-bridge configuration
- The difference between soft and hard-switching
- The gate-drive transformer
- The all-silicon-solution
- Comparison
- Conclusions

# Consideration as Designing Driver Transformer

- Ground-referenced floating drive – keep 500 V isolation if a 400 V pre-regulated PFC exists.
- Minimize the leakage inductance - the delay between output and input windings may kill the power MOSFETs.
- Follow Faraday's law – keep  $V*T$  constant, otherwise, saturate.
- Keep enough margin from saturation – the worst case happens with transient load at high line.
- High permeability ferrite – minimize the  $I_M$ .
- Keep high sink current capability

# Single DRV Input

 

$$V_C = DV_{DRV}$$


$$Q > \frac{1}{R_c} \sqrt{\frac{L_M}{C_c}} = 0.5$$

$$R_c \geq \frac{1}{Q} \sqrt{\frac{L_M}{C_c}} = 2 \sqrt{\frac{L_M}{C_c}}$$

$C_c$  to reset the driver transformer and  $R_c$  to damp the  $L$ - $C$  resonance.

- An ac coupling capacitor ( $C_c$ ) is needed to reset the driver transformer flux.
- The amplitude of  $V_{GS}$  is dependent on duty. 😞
- With  $(-V_C)$  to turn off at steady state, but the sink capability is limited at start-up. 😞
- Need a fast time constant ( $L_M//R_{GS} * C_c$ ) to avoid flux walking due to the fast transient.
- Watch out the ringing between  $C_c$  and drive transformer at skip mode or UVLO, a diode is needed to damp the ringing.


# Single DRV Input with DC Restore

 

- $V_{GS}$  amplitude is independent on duty ratio at steady state. 😊
- Limited sink capability. ☹




# Single DRV Input with PNP Turn-Off

 


- A pnp transistor + diode help to improve the switching off.

# Don't Forget the AND Gate

 

- Add the totem-pole drivers if output capability of AND gate is limited.
- Is the design finished?
  - ➔ No, not yet. Pay attention to the ringing among  $C_{C1}$ ,  $C_{C2}$  and driver transformer when skip or UVLO. A diode and resistor to damp the ringing. ☹

# Dual Polarity Symmetrical DRV Inputs

 

- $DRV_A$  and  $DRV_B$  are opposite-polarity and symmetrical → no ac coupling capacitor. 😊
- This is suitable for push-pull type circuit, e.g. LLC-HB, but NOT for asymmetrical type, e.g. AHB or active clamp. 😞
- Pay attention to the flux of driver transformer at line/load transient.
- The strong turn off capability is still needed. 😞
- Pay attention to the delay caused by the leakage inductance. → minimize the leakage inductance and use dual output windings instead of single output winding.
- Extra losses caused by voltage drop on  $R_{off}$ . 😞

# The Driver Transformer



- Pros
  - A transformer is more robust than a die!
  - Less sensitivity to spurious noise and high  $dV/dt$  pulses
  - Cheap?
- Cons
  - Complicated circuits
  - Pay attention on extreme line/line condition & off mode .....
  - Pay attention on the leakage inductance and isolation
  - Is the sink capability strong enough?

# Agenda

- Topologies using a half-bridge configuration
- The difference between soft and hard-switching
- The gate-drive transformer
- **The all-silicon-solution**
- Comparison
- Conclusions
  
# Silicon Half Bridge Driver Principle


- Principle
  - Single or dual inputs
  - High & low side driver



# Silicon Solution, What are its Limits?


- High-side isolation – 600 V is reached within the silicon.
- Matched propagation delay between high and low side drive – Prevents any unbalanced transformer usage.
- High side driver supply – Bootstrap supply is requested.
- Noise immunity – Negative voltage robustness of the high side driver.
 
# Silicon Solution, High Voltage Isolation




- Pulse trigger: generates pulse on each edge from **IN\_HI** input.
- Level shifter: shifts pulses from GND reference to GND\_HI reference.
- SR flip flop: latches pulses information from the level shifter.
 
# Silicon Solution, Matched Propagation Delay



- Delay is inserted on the fastest path: Low side driver path  
➔ to compensate: Pulse trigger + level shifter and SR flip-flop delays.
 
# Silicon Solution, High Side Driver Supply





## Bootstrap Step:

- Step 1:  $M_2$  is closed  $\rightarrow C_{boot}$  is grounded:  $C_{boot}$  is refueled via  $V_{cc}$ .
- Step 2:  $M_1$  &  $M_2$  are opened  $\rightarrow$  Bridge pin is floating,  $D_{boot}$  is blocked &  $C_{boot}$  supplies floating area.
- Step 3:  $M_1$  is closed  $\rightarrow$  bridge pin moved to bulk level,  $D_{boot}$  is still blocked &  $C_{boot}$  supplies floating area.

- Bootstrap technique is used for supplying the high side driver
  
# Root of High Side Driver Negative Voltage?


- Let's focus on the half-bridge branch:
  - the load connected to a half-bridge branch is inductive:
  - like an LLC-HB
  - Or with the most simple case in a synchronous buck (**where body diodes of the mosfet are represented**).



LLC-HB

 
# Theory: Buck Converter Operation

- 1<sup>st</sup> step of the buck converter:




 
# Theory: Buck Converter Operation

- 2<sup>nd</sup> step of the buck converter:



 
 
# Theory: Buck Converter Operation

- 3<sup>rd</sup> step of the buck converter:



  
# Theory: Buck Converter Operation

- 4<sup>th</sup> step of the buck converter:



 
# Bench: Buck Converter Operation

- Anywhere but in a ppt file there are parasitic elements:
  - True buck converter:


 
# Bench: Buck Converter Operation


- 1<sup>st</sup> step of the buck converter:



Step 1:


$M_1 \text{ ON}$

$M_2 \text{ OFF}$

 

 
# Bench: Buck Converter Operation

- 2<sup>nd</sup> step of the buck converter:




Step 2:  
 $M_1$  OFF  
 $M_2$  OFF

 

 
# Bench: Buck Converter Operation

- 3<sup>rd</sup> step of the buck converter:




Step 3:  
 $M_1$  OFF  
 $M_2$  ON

 
 
# Bench: Buck Converter Operation


- 4<sup>th</sup> step of the buck converter:



Step 4:


$M_1$  OFF

$M_2$  OFF

 

 
# Bench: Buck Converter Operation

- Negative voltage on bridge pin will create negative current injection inside the IC driver.




→ This leakage path could create some trouble inside the driver IC.
 
# How to Characterize the Negative Voltage?




Principle:

 - Negative pulse is added on bridge pin:
  - With adjustable Negative voltage
  - And adjustable Width




At each pulse width the neg. voltage is increased until the driver IC fails.
 
# How the Negative Voltage has Been Created?


 
# Example of Negative Voltage Measurement


When the bridge pin is released, it generates some noise on the hi-side driver.



Note: Negative voltage pulse is applied when the bridge pin voltage is reaching zero.
 
# Negative Voltage Characterization

Negative Voltage versus Neg. pulse duration @  
+25°C




If the negative pulse is inside  
this area, the driver will work  
properly.

If the negative pulse is inside  
this area, the driver will not work  
properly or can be damaged.

# Negative Voltage Characterization in Temperature

 **Negative Voltage versus Neg. pulse duration @ different Temp**



- Note: These characterizations will be available in each IC driver datasheet

# Driver IC Remarks

- ON Semiconductor defines electrical parameters over overall temperature range (here  $-40^\circ\text{C} < T_j < +125^\circ\text{C}$ ). See electrical table & characterization curves.
- Competitors define the electrical parameters only at  $T_{amb} = +25^\circ\text{C}$ . Temp characterization is not always available
  - what about min & max over extended temperature range?
- The competitors values extracted from the curves probably do not take into account the lot to lot process variations
  - the range variation is probably wider.


# ON Semiconductor IC Driver Cross Reference

	Drive trise / tfall typ. ( $C_L=1\text{ nF}$ )	Propag. Delay typ. $t_{ON} / t_{OFF}$	Matching Delay Typ / Max	Cross Conduction Protection	Pin-Out Compatibility	Remarks
NCP5181	40 ns / 20 ns	100 ns / 100 ns	20 ns / 35 ns	-	IR2181 – IRS2181	• 3.3 V CMOS/TTL inputs
NCP5106A	85 ns / 35 ns	100 ns / 100 ns	20 ns / 35 ns	-	IR2106 – IRS2106, FAN7382	• 3.3 V CMOS/TTL inputs
NCP5106B	85 ns / 35 ns	100 ns / 100 ns	20 ns / 35 ns	✓	IR2106 – IRS2106, FAN7382	• 3.3 V CMOS/TTL inputs • Internal fixed dead time 100 ns
NCP5304	85 ns / 35 ns	100 ns / 100 ns	20 ns / 35 ns	✓	IR2304 - IRS2304, L6388/84 FAN7380	• 3.3 V CMOS/TTL inputs • Internal fixed dead time 100 ns
NCP5111	85 ns / 35 ns	750 ns / 100 ns	30 ns / 60 ns	NA	IR2111 – IRS2111,	• 3.3 V CMOS/TTL input • Internal fixed dead time 650 ns • One pin for creepage
NCP5104	85 ns / 35 ns	620 ns / 100 ns	10 ns / 45 ns	NA	IR2104 – IRS2104	• 3.3 V CMOS/TTL input • Internal fixed dead time 520 ns

# Agenda


- Topologies using a half-bridge configuration
- The difference between soft and hard-switching
- The gate-drive transformer
- The all-silicon-solution
- Comparison
- Conclusions
 
# LLC-HB Schematic with Driver Transformer




- LLC-HB with 24 V @ 10 A
- NCP1395, the LLC controller with dual DRV outputs.
- Transformer drivers the MOSFETs of LLC converter.

# LLC-HB Schematic with Driver IC

 

- LLC-HB with 24 V @ 10 A
  - NCP1395, the LLC controller with dual DRV outputs.
  - NCP5181, driver IC drives the MOSFETs of LLC converter.

# $V_{GS}$ Waveform

 


Driver transformer

Driver IC (NCP5181)


- The waveforms seem similar.

# High Side MOSFET Turns Off

 

- The driver IC turns off the MOSFETs more vigorously.
- IC turn-off is 70 ns faster, lowering the switching losses

# High side MOSFET Turns On

 

Driver transformer

Driver IC (NCP5181)

- The driver IC keeps safe and enough dead time between high and low side MOSFETs.

# The Efficiency Comparison

	Input power (W)	Output power (W)	$V_{out}$ (V)	$I_{out}$ (A)	$\eta$
Driver IC	128.33	119.72	23.96	5.00	93.29%
	257.2	235.46	23.57	9.99	91.55%
Driver Transformer	128.34	119.72	23.96	5.00	93.29%
	258.5	236.46	23.67	9.99	91.48%


- There is no efficiency difference between the IC driver and transformer solutions.

# Agenda

- Topologies using a half-bridge configuration
- The difference between soft and hard-switching
- The gate-drive transformer
- The all-silicon-solution
- Comparison
- Conclusions
 
# Conclusion: Transformer or IC?

- Both solutions work if well-trimmed.
- We recommend the IC solution because:
  - We don't sell the transformer. 😊
  - Manual insertion for the transformer.
  - Ease the layout
  - Ease the design
  - Free of transformer problems, e.g.:
    - isolation is destroyed,
    - flux walking away,
    - unexpected ringing after turn off,
    - Height of the transformer in low profile PSU



# For More Information

- View the extensive portfolio of power management products from ON Semiconductor at [www.onsemi.com](http://www.onsemi.com)
- View reference designs, design notes, and other material supporting the design of highly efficient power supplies at [www.onsemi.com/powersupplies](http://www.onsemi.com/powersupplies)