



Is Now Part of



ON Semiconductor®

To learn more about ON Semiconductor, please visit our website at
www.onsemi.com

ON Semiconductor and the ON Semiconductor logo are trademarks of Semiconductor Components Industries, LLC dba ON Semiconductor or its subsidiaries in the United States and/or other countries. ON Semiconductor owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of ON Semiconductor's product/patent coverage may be accessed at www.onsemi.com/site/pdf/Patent-Marking.pdf. ON Semiconductor reserves the right to make changes without further notice to any products herein. ON Semiconductor makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does ON Semiconductor assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using ON Semiconductor products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by ON Semiconductor. "Typical" parameters which may be provided in ON Semiconductor data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. ON Semiconductor does not convey any license under its patent rights nor the rights of others. ON Semiconductor products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use ON Semiconductor products for any such unintended or unauthorized application, Buyer shall indemnify and hold ON Semiconductor and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that ON Semiconductor was negligent regarding the design or manufacture of the part. ON Semiconductor is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

LVDS Compatibility with RS422 and RS485 Interface Standards

Abstract

Low Voltage Differential Signaling (LVDS) technology offers one of the best serial data transmission profiles available today for physical layer interfaces. With many existing interface standards to choose from, this applications note provides guidelines on the inter-operation of

LVDS devices with other differential interface standards such as RS-422/485. An example is included of an LVDS receiver configured to be inter-operable with an RS-422 driver.

Interface Standards

With so many electrical interface standards having separately evolved within particular industries, many serial data interface standards now exist. To simplify designers'

choices, the following table summarizes some of the key electrical specifications for the different serial data interface standards listed.

TABLE 1. Interface Standards Specifications

Parameter	RS-422	RS-485	RS-644 (LVDS)
Differential Voltage Swing (typ)	3.0V	3.0V	350mV
Common Mode Voltage	1.8V	1.8V	1.2V
Driver Output Rise Time	10%tui	30%tui	30%tui
Receiver Common-Mode Voltage	± 7V	-7V/+12V	0V to +2.4V
Receiver Sensitivity	± 200mV	± 200mV	± 100mV
Signaling Rate	< 50Mbps	< 50Mbps	> 400Mbps
Transmission Distance (Note 1)	≤1200m	≤1200m	≤100m

Note 1: The transmission distance is shorter with faster signaling rates.

The three standards in Table 1 are hardware specifications that define the driver and receiver electrical characteristics. Software protocols are not discussed in any of the standards, and it is up to the system designer to define a protocol suitable for their system. The RS-422 differential standard was established to provide a balanced interconnect system (in preference to the single-ended interface) for use at higher signaling rates. The RS-422 standard is

suited for point-to-point and multi-drop interconnects and not so well suited for multipoint systems. The RS-485 differential standard was issued to provide the driver/receiver electrical characteristics for balanced multipoint systems. One of the principle differences between RS-422 and RS-485 standards is that the RS-485 driver can be placed into a high impedance tristate mode, allowing drivers to transmit over the same pair of wires.

Compatibility with RS-422 and RS-485 Standards

The LVDS interface circuit is not intended for direct inter-operation with other interface technologies, like RS-422, RS-485, or even Positive Emitter Coupled Logic (PECL).

Under certain conditions, inter-operation of LVDS with other interface circuits mentioned above may be possible but may require modification in the interface or within the equipment. Limitations on certain performance parameters, like common mode range, may be required; satisfactory operation is not assured and additional provisions may need to be employed.

In determining whether direct inter-operation of LVDS TIA/EIA-644 compliant devices is possible with other interface standards, it is necessary to compare the generator (driver) output and the receiver input electrical specifications. Specifically the driver's differential output voltage (V_{OD}) and the driver offset voltage (V_{OS}) must be within the bounds of the LVDS RS-644 receiver's input ranges. Correspondingly, the receiver's input thresholds and voltage range must be able to accept the LVDS RS-644 driver's output levels.

Drivers compliant to the TIA/EIA-644 standard feature a current source capable of delivering a loop current in the range of 2.5 to 4.5mA. As illustrated in Figure 1, the resulting differential voltage (V_{OD}) will be a minimum of 250 mV up to a maximum of 450mV across the 100Ω termination resistor. The driver offset voltage (V_{OS}), also referred to as the center point, is typically +1.2V referenced to circuit common ground.

Any balanced receiver that guarantees the input voltage range of 0V to +2.4V and input thresholds of 200mV or less may be compatible and directly inter-operate with other balanced drivers. Compatibility is possible provided the balanced driver does not violate the maximum receiver input voltage range and develops a differential voltage (V_{OD}) of at least 100mV and not greater than 600mV. Inter-operation with drivers with larger output differential voltages is possible by using an attenuation circuit with the interface points of the components. Refer to Figure 2 for the illustration.

Compatibility with RS-422 and RS-485 Standards (Continued)

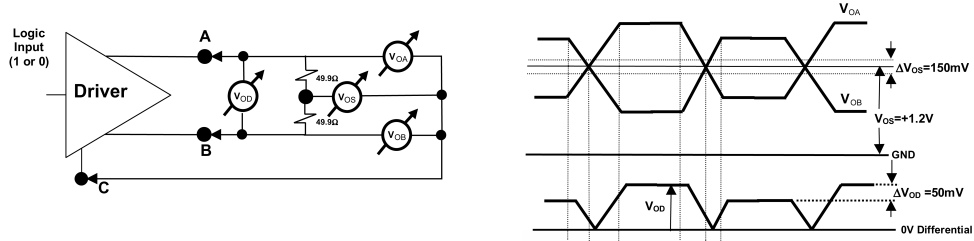


FIGURE 1. Driver Output Levels

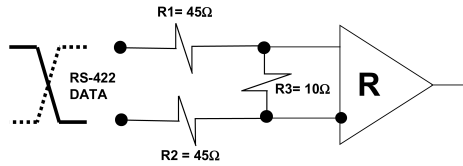


FIGURE 2. Application of RS-422 Data to an LVDS Receiver

The R1, R2, and R3 resistor divider network collectively is a total differential load of 100Ω to match the characteristic impedance of the transmission line and reduces the typical RS-422 differential signal amplitude of 3.3V down to a 330mV level. Essentially, the resistor network is a 10:1

attenuation circuit. Refer to the equation below to calculate the voltage drops across the resistors.

The majority (90%) of the RS-422 voltage is dropped across resistors R1 and R2, leaving the remaining voltage to be dropped across R3 which is compatible to the LVDS receiver.

$$\begin{aligned}
 I_{TOT} &= V_{TOT}/R_{TOT} && \text{(Current through the resistor network)} \\
 &= 3.3V / (R1 + R2 = R3) \\
 &= 3.3V / 100\Omega \\
 &= 33 \text{ mA}
 \end{aligned}$$

(Voltage across R1)	(Voltage across R2)	(Voltage across R3)
$V1 = I_{TOT} * R1$	$V2 = I_{TOT} * R2$	$V3 = I_{TOT} * R3$
$= (33\text{mA})(45\Omega)$	$= (33\text{mA})(45\Omega)$	$= (33\text{mA})(10\Omega)$
$= 1.485V$	$= 1.485V$	$= 330mV$

Summary

Compatibility of TIA/EIA-644 LVDS drivers and receivers with other interface standards can be achieved by employing additional attenuation circuitry within the interface points of the system. When inter-operation of LVDS compliant devices is desired, provisions should be made to implement the attenuation circuitry that adjusts the differential

amplitude voltages of the balanced driver to be within the receiver voltage range. As always, application specific requirements and needs may dictate what design techniques must be implemented to make a reliable interconnect system.

Fairchild does not assume any responsibility for use of any circuitry described, no circuit patent licenses are implied and Fairchild reserves the right at any time without notice to change said circuitry and specifications.

LIFE SUPPORT POLICY

FAIRCHILD'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT OF FAIRCHILD SEMICONDUCTOR CORPORATION. As used herein:

1. Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, and (c) whose failure to perform when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in a significant injury to the user.
2. A critical component in any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.

www.fairchildsemi.com

ON Semiconductor and  are trademarks of Semiconductor Components Industries, LLC dba ON Semiconductor or its subsidiaries in the United States and/or other countries. ON Semiconductor owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of ON Semiconductor's product/patent coverage may be accessed at www.onsemi.com/site/pdf/Patent-Marking.pdf. ON Semiconductor reserves the right to make changes without further notice to any products herein. ON Semiconductor makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does ON Semiconductor assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using ON Semiconductor products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by ON Semiconductor. "Typical" parameters which may be provided in ON Semiconductor data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. ON Semiconductor does not convey any license under its patent rights nor the rights of others. ON Semiconductor products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use ON Semiconductor products for any such unintended or unauthorized application, Buyer shall indemnify and hold ON Semiconductor and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that ON Semiconductor was negligent regarding the design or manufacture of the part. ON Semiconductor is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

PUBLICATION ORDERING INFORMATION

LITERATURE FULFILLMENT:

Literature Distribution Center for ON Semiconductor
19521 E. 32nd Pkwy, Aurora, Colorado 80011 USA
Phone: 303-675-2175 or 800-344-3860 Toll Free USA/Canada
Fax: 303-675-2176 or 800-344-3867 Toll Free USA/Canada
Email: orderlit@onsemi.com

N. American Technical Support: 800-282-9855 Toll Free
USA/Canada
Europe, Middle East and Africa Technical Support:
Phone: 421 33 790 2910
Japan Customer Focus Center
Phone: 81-3-5817-1050

ON Semiconductor Website: www.onsemi.com
Order Literature: <http://www.onsemi.com/orderlit>
For additional information, please contact your local
Sales Representative