

# ON Semiconductor

## Is Now

# onsemi™

To learn more about onsemi™, please visit our website at  
[www.onsemi.com](http://www.onsemi.com)

---

**onsemi** and **onsemi** and other names, marks, and brands are registered and/or common law trademarks of Semiconductor Components Industries, LLC dba "**onsemi**" or its affiliates and/or subsidiaries in the United States and/or other countries. **onsemi** owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of **onsemi** product/patent coverage may be accessed at [www.onsemi.com/site/pdf/Patent-Marking.pdf](http://www.onsemi.com/site/pdf/Patent-Marking.pdf). **onsemi** reserves the right to make changes at any time to any products or information herein, without notice. The information herein is provided "as-is" and **onsemi** makes no warranty, representation or guarantee regarding the accuracy of the information, product features, availability, functionality, or suitability of its products for any particular purpose, nor does **onsemi** assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using **onsemi** products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by **onsemi**. "Typical" parameters which may be provided in **onsemi** data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. **onsemi** does not convey any license under any of its intellectual property rights nor the rights of others. **onsemi** products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use **onsemi** products for any such unintended or unauthorized application, Buyer shall indemnify and hold **onsemi** and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that **onsemi** was negligent regarding the design or manufacture of the part. **onsemi** is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner. Other names and brands may be claimed as the property of others.

## Off-Line Critical Conduction Switching Power Supply with Voltage and Current Limiting



ON Semiconductor®

[www.onsemi.com](http://www.onsemi.com)

---

### APPLICATION NOTE

#### Abstract

The need for a small, economical solution for switching power supplies and for battery chargers has increased. These applications generally require both voltage limiting and current limiting. These must be very efficient and produce a low amount of EMI radiated noise. The MC33364 is a critical conduction control IC that can be configured in a resonant turn-off mode to reduce the amount of EMI

generated during turn-off of the power MOSFET. The MC33341 is a secondary side controller that contains the band gap reference to provide a very tight tolerance voltage reference. The MC33341 also allows for current limiting thus providing an almost square loop of voltage and current needed for lithium-ion battery charging. Combining these two devices produces a much more cost-effective solution than other approaches offer.

#### THE CLASSIC APPROACH

In prior years, a very cost efficient and economical design approach was demanded for battery chargers and power supplies. The unit had to be current limited on the secondary side and provide the proper voltage output. The supply often did not support universal input. One circuit approach to meet this need is shown in Figure 1. This is a classical blocking oscillator. This circuit has its roots back to the old vacuum tube days, and was updated by Bob Haver in 1984 and presented at various switching power supply seminars [1], [2]. This is a variable frequency unit that operates in what is known today as the critical conduction mode.

The unit starts by having the gate of the TMOS™ or power MOSFET turned on by the series resistors R1 and R2. The current through the primary of the coupled inductor transformer ramps up linearly. The auxiliary winding on the transformer is phased to provide positive (in phase) gate voltage. The TMOS device is “turned off” when the primary current produces approximately 0.7 V across the source resistor (R<sub>source</sub>), the bipolar junction transistor (BJT) becomes forward biased and “turns on”.

When the BJT is “turned on”, the charge on the gate is removed and the TMOS power FET is “turned off”. The auxiliary voltage is reversed as the voltage on the primary is

reversed in order to release its stored energy to the secondary. As long as there is energy flowing to the secondary, the auxiliary voltage is negative and the gate voltage is negative. The small signal diode (1N914) in series with the collector of the BJT keeps the device from operating in a reverse mode. In lieu of 1N914, a 1N4148 or 1N4150 may be used.

With the TMOS power FET in the “off” mode, the coupled energy stored in the air gap of the inductor is released to the secondary. The secondary energy flows to the load by way of Schottky diode D2. When the coupled energy is depleted, the voltage across the both the primary, secondary and auxiliary windings decreases to zero.

The transformer is not a perfect device, so there is a small amount of energy remaining in the primary. This is the energy in the leakage inductance of the primary. This causes the voltage across the transformer to start to ring with the C<sub>oss</sub> capacitance of the FET. This “turn-off” ring has the effect of reducing the drain-source voltage of the FET, and causes the auxiliary winding to develop a positive voltage. This positive voltage, along with two resistors R1 and R2 places a positive voltage on the gate of the TMOS power FET; this restarts the energy storage cycle.

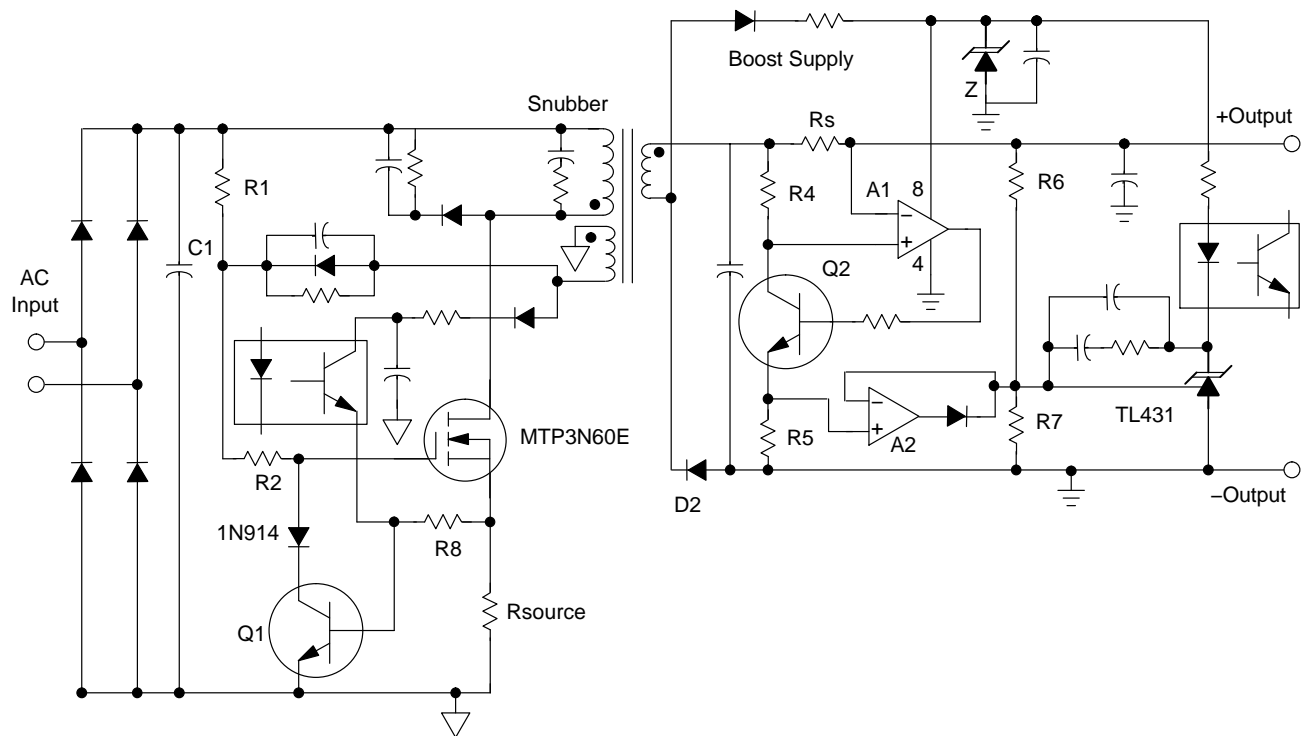


Figure 1. Blocking Oscillator with Voltage and Current Limit on the Secondary Side

**Classic Voltage and Current Feedback**

The secondary side contains all the control functions. The voltage feedback is determined by the classic TL431 with resistors R6 and R7. The voltage across R7 is 2.54 V. The current through the LED of the optocoupler causes the NPN photo-transistor to conduct, thereby developing a small voltage across the resistor R8, which produces an offset voltage to the base of Q1. This causes the primary current to be reduced during a switching or energy storage cycle.

The current limiting is accomplished by the section to the left of the voltage divider resistors R6 and R7. The series resistor, Rs, has the same voltage across it as R4. The ratio of R4/Rs can be thought as a current gain. The operational amplifier, A1, provides current to the base of a high h<sub>FE</sub> NPN transistor to maintain VR4 equal to VRs. (In some applications Q2 is an N-channel JFET.) The current through R4 is the same current through R5. When voltage across R5 (VR5) exceeds 2.54 V, the buffer stage composed of A2 and the series diode increases the voltage across R7, which causes the LED current to increase and raises the offset voltage on the primary side. Only when VR5 exceeds the TL431 reference voltage is the current limit applied.

In order to have the operational amplifiers A1 and A2 (MC33072) function properly, a boosted supply voltage is

necessary. This is accomplished by using the forward voltage mode of the transformer. This boosted supply voltage is limited by the zener, Z.

The maximum load current can be defined by Equation 1:

$$I_{LoadMax} = \frac{2.5}{R_5} \cdot \frac{R_4}{R_S} \quad (\text{eq. 1})$$

As an example, if the maximum is 3.0 A, Rs is chosen to dissipate less than 0.5 W at full load. This calculates to be a 0.05556 Ω resistor, therefore a more practical value of 0.05 Ω is chosen, which is typically composed of two 0.1 Ω resistors. The next item to be chosen is the current gain. A value of 200 would produce a maximum current of 15 mA through R4 and R5. This would make R4 equal to 10 Ω (0.05 \* 200 = 10). The value of R5 then becomes 166.667 Ω. This value can be created by using two series resistors, a 160 Ω and a 6.8 Ω, both of which are 0.25 W or less.

The effect of the feedback is to create a square output characteristic as shown in Figure 2. Because there is no perfect square output characteristic, the current is raised slightly. In this case only a 150 Ω resistor would be used for R5 which raises the output current to 3.33 A. A 160 Ω resistor would provide 3.125 A.

 


Figure 2. Square Voltage and Current Output Characteristics

**Problems and Issues with the Blocking Oscillator**

There are many issues associated with the blocking oscillator. The first issue is that it can only be designed for a single voltage input, such as 120 VAC or 220 VAC. This will not operate over the entire range from 85 to 270 VAC input, due to the auxiliary voltage variation. The auxiliary voltage is proportional to the rectified DC line voltage across the input electrolytic capacitor C1. If the auxiliary voltage is 7 V with the valley of voltage of C1 equal to 100 volts, this would mean 13 V for 132 VAC input and 21.77 V for a 220 VAC input. There are two problems with this. First, 7 V is very near the threshold of the high voltage power FET for good saturation. The lowest voltage for a non-logic level device using “Engineering Rule of Thumb” is 8 V. The highest gate voltage which should be applied using good engineering practice is 8 V. Clearly, this is not a “Universal Input” candidate.

The second issue is the gate turn-off. The transistor Q1 has a limit to its ability to rapidly “turn-off” the power FET. The

power FET therefore dissipates additional energy, requiring a large heat sink. The third issue occurs under a no load condition, where the frequency of operation becomes very high.

**Problems and Issues with the Classic Secondary Side Control**

The initial problem is operation under a short circuit condition. When the LED is connected to the +Output, there is no voltage to power the LED to cut back on the short circuit current. Therefore, the LED should be connected to the “Boosted Supply”.

The current should be limited through the LED to maintain a voltage on the “Boosted Supply”.

The second issue is the large number of components necessary to implement this circuit. Even though all of the components are available as surface mount components, it is important to note that quality, cost and space are usually impacted as component count increases.

**THE IMPROVED APPROACH**

**Primary Side Integrated Circuit, MC33364**

Today, a power supply is required have a universal input. Laptop computer, cellular phone, and various other pieces of equipment are required to be able to operate in any country or place on earth where AC or DC electrical energy is available. The requirement today is to only change the plug, which connects to power supply. The requirements are:

1. Universal Input Voltage
2. Circuit Short Operation
3. Open Circuit Operation
4. Power Limit or Square Loop Load Operation

There are various integrated circuits today that can perform this function; one of them is the MC33364. The MC33364 is labeled a critical conduction controller, which is the same as the traditional blocking oscillator shown in Figure 1. Therefore, the transformer design is identical to that of the blocking oscillator.

The advantages of this IC over the discrete blocking oscillator are:

1. Wide input voltage range from 40 to 700 VDC. This IC can operate from the 48 V telecom DC bus to the 381 VAC line-to-line voltage common in Europe
2. Full gate drive to properly drive high voltage power FET or IGBTs in a TO-220 package that only need 15 V
3. Frequency clamp to limit the open circuit frequency
4. Reference to be able to perform primary side control

The essential difference between the traditional and the MC33364-based circuits is the phasing of the auxiliary winding. The auxiliary winding is phased the same as the output winding. This allows a control auxiliary supply

voltage that can be tightly coupled to the primary and secondary.

**Secondary Controller IC, MC33341**

The MC33341 is an 8 pin device the same size as the dual operational amplifier MC33072 in the discrete, classic system controller. An internal reference is set at approximately 1.2 V which allows for low voltage applications. This is similar to the TLV431. The advantages of the MC33341 approach are as follows:

1. Small size
2. Fewer components
3. LED is driven directly from the IC for easier short circuit operation
4. Positive (+bus) or negative (-bus) sensing

There are the following similarities:

1. Resistor divider network for voltage determination
2. Two resistors for current sensing

3. Need for a boosted supply for short circuit operation


**Design Example: An 85 to 270 VAC In; 3 A, 8.2 V Out Controller**

A complete design is shown in Figure 3. This implementation has the same function as that shown in Figure 1, except that now universal input is supported. This supply will operate over the input range from 85 to 270 VAC. The resultant power supply or battery charger will have a square loop output characteristic with the ability to supply 3.0 A continuously at 8.2 V. A full load frequency of 70 kHz at low line is chosen. The output is:

$$\text{Watts Load} = 3.0 \cdot 8.2 = 24.6 \text{ W} \quad (\text{eq. 2})$$

$$\text{Watts Input} = \frac{\text{Watts Load}}{\eta \text{ (efficiency)}} = \frac{24.6}{0.85} = 28.9 \text{ W} \quad (\text{eq. 3})$$

For this design, we will use 30 W to keep the numbers simple.

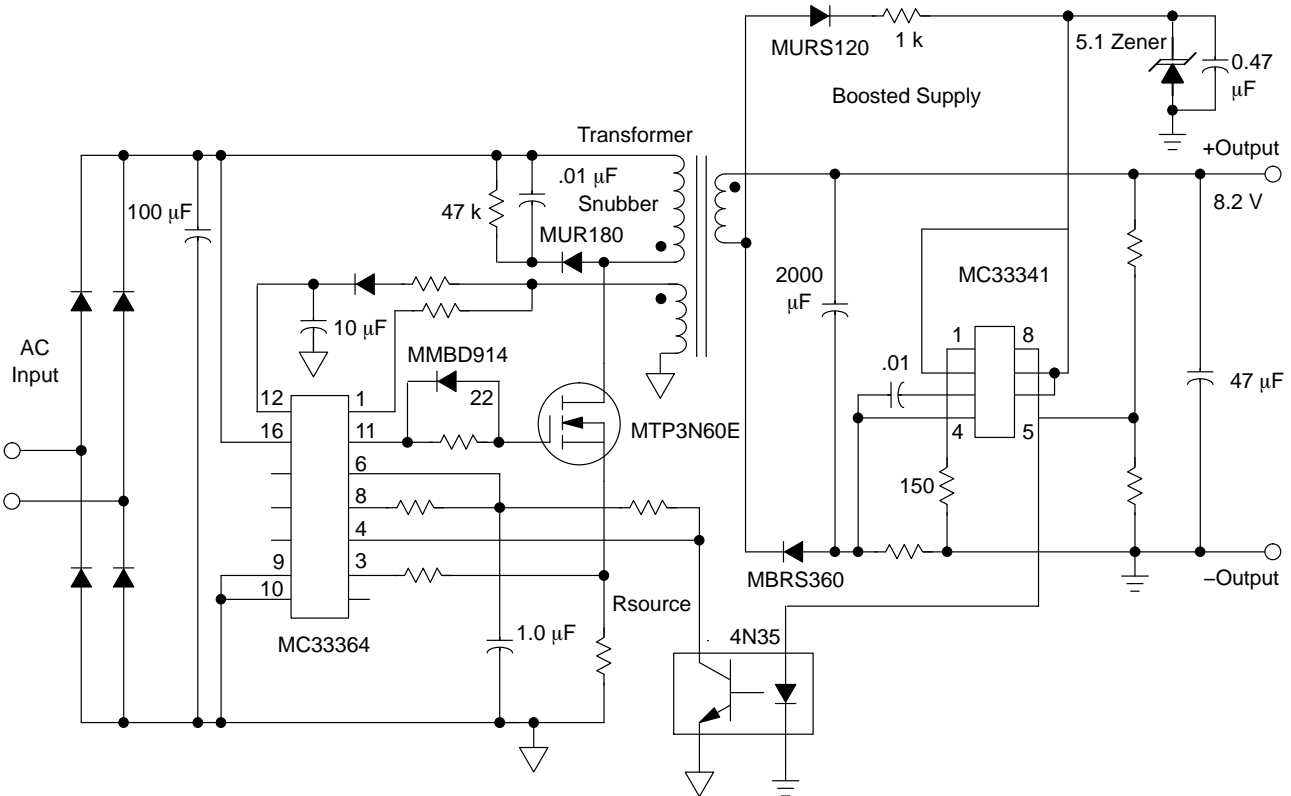

**Figure 3. Universal Input Controller with an Output at 3 A and 8.2 V**

Low line is an 85 VAC, 50 Hz input with a 20 V ripple on the electrolytic at this voltage. This defines the valley, from which the size of the electrolytic capacitor and the value of the inductor are determined. The value of the capacitor can be determined by several methods. Two will be given here. The first comes from a text by Savant et al [4] where:

$$C = \frac{V_{\text{PEAK at LOWLINE}}}{\Delta V_{\text{PEAK RIPPLE}} \cdot F_{\text{REQ}} \cdot R_{\text{LOAD}}} \quad (\text{eq. 4})$$

For a 20 V peak-to-peak ripple.

$$\frac{85 \cdot \sqrt{2}}{20 \cdot 100 \cdot 500} = 120 \mu\text{F} \quad (\text{eq. 5})$$

For a 25 V peak-to-peak ripple.

$$\frac{85 \cdot \sqrt{2}}{25 \cdot 100 \cdot 500} = 96 \mu\text{F} \quad (\text{eq. 6})$$

$$R_{\text{Load}} = \frac{V_{\text{CAP AVERAGE}}^2}{\text{Watts}} \quad (\text{eq. 7})$$

$$V_{\text{CAP AVERAGE}} = V_{\text{PEAK at LOWLINE}} - \frac{\Delta V_{\text{PEAK RIPPLE}}}{2} \quad (\text{eq. 8})$$

The second method uses the joules of energy to calculate the value of the capacitor. From engineering experience, the length of time the diodes conduct in a full wave bridge is approximately 2.5 ms for a 50 Hz system and about 2.25 ms for a 60 Hz system. This means the energy storage electrolytic capacitor must supply the energy during the non-conducting period. This is 7.5 ms for 50 Hz and 6 ms for a 60 Hz system.

$$\text{Joules} = \text{Watt} \cdot \text{Seconds} \quad (\text{eq. 9})$$

$$\text{Joules} = 30 \cdot 7.5e^{-3} = 0.225 \quad (\text{eq. 10})$$

$$\text{Joules} = \frac{1}{2} \cdot CV_{\text{PEAK}}^2 - \frac{1}{2} \cdot CV_{\text{VALLEY}}^2 \quad (\text{eq. 11})$$

$$C = \frac{2 \cdot \text{Joules Load}}{V_{\text{PEAK}}^2 - V_{\text{VALLEY}}^2} \quad (\text{eq. 12})$$

$$C = \frac{2 \cdot 0.225}{(85 \cdot \sqrt{2})^2 - (85 \cdot \sqrt{2} - 25)^2} = 83.5 \mu\text{F} \quad (\text{eq. 13})$$

Both methods indicate a large electrolytic capacitance value is needed for operation at 85 VAC 50 Hz. The DC rating of the electrolytic capacitor is defined by the AC high line voltage, which is 270 V. This means a 400 V electrolytic capacitor is necessary. The typical embodiment is one 100  $\mu\text{F}$  400 VDC electrolytic, or two 47  $\mu\text{F}$  400 VDC electrolytics in parallel.

As an added note, if the supply were to be used in the US and Canada on a 120 V, 60 Hz line, 2 times load is an "Engineering Rule of Thumb". This would be a 60  $\mu\text{F}$  capacitor, or a 68  $\mu\text{F}$  from manufacturers' catalogs. If in Europe, with its 220 VAC, 50 Hz line, the capacitor would be the 30  $\mu\text{F}$ , or as a typical catalog value, 33  $\mu\text{F}$ .

### Power Factor Correction (PFC) and Hold Up Time

The design of a universal input from 85 VAC 50 Hz to 270 VAC 50 Hz can be difficult, as seen by the size of electrolytic capacitors. The above capacitor sizing does not include any "hold-up" time for missing AC line cycles. If a "hold-up" time is required along with a universal input, it is strongly suggested that an active PFC circuit be considered. This would reduce the capacitance value of the electrolytic capacitor and reduce the current rating of the flyback power MOSFET. The voltage ratings of both parts would remain nearly identical. Using an active PFC circuit like the MC33262 or the MC33261 could help reduce the physical size of the unit. The data sheets for the MC33262 and MC33261 contain design equations, and several reference designs are included with data.

### Transformer or Coupled Inductor Design

Because the minimum voltage is defined, the value of the inductance can now be calculated. The minimum DC voltage across the electrolytic capacitor is 95 V. At this point, the duty cycle is a maximum of 0.5, meaning that the on-time is equal to the off-time of the switch. The peak current for the switch and the inductance value are both calculated. This is developed by Chrysis [5]. The minimum frequency at full load is calculated to be 70 kHz.

$$I_{\text{PEAK PRIMARY}} = \frac{2 \cdot \text{Watts}}{V_{\text{DC MIN}} \cdot \delta_{\text{max}}} = \frac{2 \cdot 30}{95 \cdot 0.5} = 1.26 \text{ A} \quad (\text{eq. 14})$$

$$E = L \cdot \frac{\alpha i}{\alpha t} = L \cdot \frac{V_{\text{DC MIN}} \cdot \delta_{\text{MAX}}}{\delta} \cdot \text{Freq} \quad (\text{eq. 15})$$

$$L = \frac{V_{\text{DC MIN}}^2 \cdot \delta_{\text{MAX}}^2}{2 \cdot \text{Watt} \cdot \text{Freq}} = \frac{95^2 \cdot 0.5^2}{2 \cdot 30 \cdot 70 \text{ e}^3} = 537 \mu\text{H} \quad (\text{eq. 16})$$

The core was chosen from parts readily available; Ferrite International (7070-30-15-07), Magnetic (P43007), Philips (E30/15/7-3C80). This core has the following parameters:

- Cross Sectional Area,  $A_e$  or  $A_c = 0.49 \text{ cm}^2$  min. center leg
- Magnetic Material Path Length,  $l_m = 6.56 \text{ cm}$

The turns are calculated using Equation 18, which is developed from Equation 17.

$$E = N \cdot \frac{\alpha \theta}{\alpha t} = N A_C \cdot \frac{\alpha B}{\alpha t} \quad (\text{eq. 17})$$

$$N = \frac{E \cdot \Delta t}{A_O \cdot \Delta B} \quad (\text{eq. 18})$$

For the primary, there are 68 turns using AWG 25 wire. Next, the air gap is calculated to determine the edge space. The gap is calculated using equations 19 and 20. The gap is the total gap including the edge gap and the center gap. Since ungapped cores are being used, the gap length is divided by two, and the spacer is placed on the outer legs. The total gap is  $2.05 \text{ e}^{-5}$  meters, or 0.008 inches. This means a spacer of 0.004 inches, which is the thickness of sheet of copier paper.

$$L = \frac{N^2}{\mathfrak{R}} = \frac{N^2}{\mathfrak{R}_{\text{CORE}} + \mathfrak{R}_{\text{MATERIAL}}} = \frac{N^2}{\frac{l_m}{\mu_0 \mu_R A_C} + \frac{l_{\text{GAP}}}{\mu_0 A_{\text{GAP}}}} \quad (\text{eq. 19})$$

$$l_{\text{GAP}} = \frac{\mu_0 A_C N^2}{L} - \frac{l_m}{\mu_R} \quad (\text{eq. 20})$$

Where:

L = Inductance in henries

$l_m$  = core magnetic path length in meters

$l_{\text{gap}}$  = gap length in meters

$A_C = A_e$  = Effective Cross Sectional Area in Meters<sup>2</sup>

$\mu_0 = 4\pi \cdot 10^{-7}$

$\mu_R$  = Core Permeability

N = Number of turns

The primary voltage divided by the primary turns defines the volts per turn, which is approximately 1.4 V per turn. The secondary turns is calculated to be 6.35 turns. A value of 7 turns is chosen for the 8.3 V secondary using two strands of 24 AWG magnet wire, and 10 turns is chosen for the auxiliary winding, using 30 AWG. If the power switch is an IGBT requiring 15 V, the auxiliary winding would be 13 turns. All of this easily fits onto the single section bobbin. Additional information is available in the form of application notes from ON Semiconductor, see references [6], [7], and [8].

**Transformer Sizing**

It is beyond the intent of this application note to teach exact transformer and inductor design. The information given is used as a guide for background information. Choosing the size of the transformer or coupled inductor is easy, but there are rules of thumb. One of the easier methods is to use the “Area Product” method. The equations are developed in the Magnetics Ferrite Core catalog [9]. Another set of equations along with data is found in C. McLyman’s books [10], [11], [12], which have become standards for transformer and inductor designers. The Area Product ( $A_P$ ) equation is defined below for single transistor forward converter transformers and flyback transformers. This defines the smallest possible core.

- $A_P$  = Area product in  $cm^4$
- $P_O$  = Output power of all the windings
- $C$  = Inverse of current density  $1/J = 3.55 \cdot 10^{-3} cm^2/Amp$

$$A_P = \frac{P_O C \cdot 10^8}{2eBFK} \quad (eq. 21)$$

This is similar to 500 circular mils per Amp.

- $e$  = Efficiency, often taken as 0.9 for a starting point
- $B$  = Peak flux density the core will see
- $F$  = Switching Frequency
- $K$  = Transformer utilization factor, typically 0.3  
For a transformer this can never exceed 0.5  
For an inductor this can be near 0.8

$$A_P = \frac{3 \cdot 3.22 \cdot 10^{-3} \cdot 10^8}{2 \cdot 0.9 \cdot 2000 \cdot 70 \cdot 10^3 \cdot 0.3} = 0.12778 cm^4 \quad (eq. 22)$$

The core chosen must be larger than  $0.127 cm^4$ . In order to meet many of the European regulator standards, the  $A_P$  may have to be increased by a factor between 2 and 3. This is where the art of transformer design begins to play an important part. The core chosen for this example has an  $A_P = 0.55 cm^4$ .

**Non-Dissipated Snubber Design For Quasi Resonant Mode Operation**

The snubber circuit can be modified to make the circuit dissipate less energy and to lower the switching transitions. This is shown in Figure 4. The lossless snubber described in Chapter 11 of the Rectifier Applications Handbook [13] reduces the turn-off losses of the power FET by limiting the dV/dt rise of the drain-source voltage. By starting with Equation 23 and rearranging into Equation 24, the turn-off energy to the power FET can be greatly reduced.

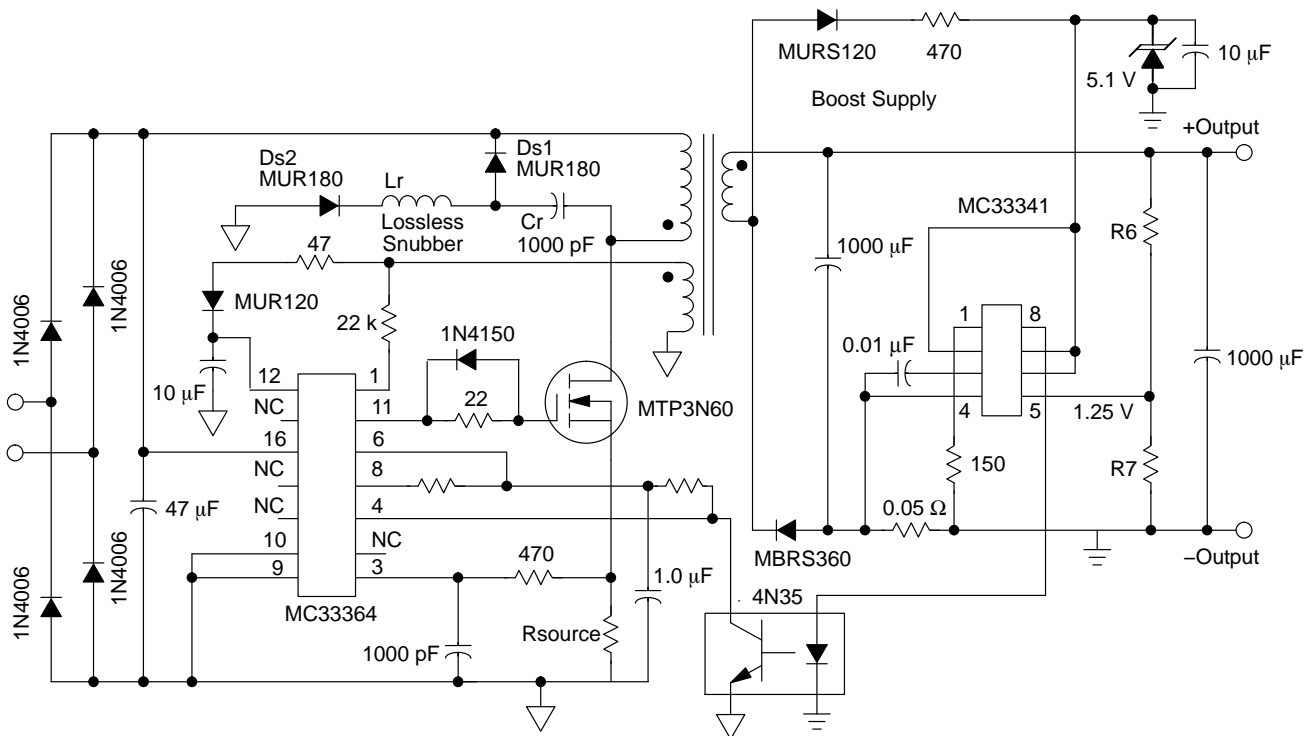


Figure 4. Lossless Snubber Circuit

During the beginning of the power FET “turn-off” period, the primary current wants to continue to flow, and forces the primary winding to change voltage direction. Instead of the primary current flowing through the FET, the current is directed through the capacitor, Cr, and diode, Ds1. The capacitor, Cr, charges to a voltage defined by Equation 25. The energy stored is given by Equation 26.

$$i = C \cdot \frac{\alpha V}{\alpha t} \quad (\text{eq. 23})$$

$$\frac{i}{C} = C \cdot \frac{\alpha V}{\alpha t} \quad (\text{eq. 24})$$

$$V_{Cr} = (V_{\text{OUTPUT}} + 0.7 \text{ V}) \cdot \frac{N_{\text{PRIMARY}}}{N_{\text{SECONDARY}}} \quad (\text{eq. 25})$$

$$86.4 = (8.2 + 0.7) \cdot \frac{68}{7}$$

$$J_{Cr} = \frac{1}{2} \cdot CV^2_{Cr} \quad (\text{eq. 26})$$

After all of the coupled energy is released to the secondary, the voltage on the auxiliary winding rings through zero and forces the MC33364 to start the next energy storage cycle. When the Power FET turns on, the drain of the FET is at ground potential. There is a complete circuit consisting of the FET, diode (Ds2), inductor (Lr), and capacitor (Cr). In an ideal condition the voltage on the capacitor reverses its polarity, this is explained by Rashid in Chapter 2 of his text “Power Electronics” [14]. The time for this transition to occur is defined by Equation 27.

$$t = \pi \cdot \sqrt{Cr \cdot Lr} \quad (\text{eq. 27})$$

The value of the peak current is defined by Equation 29.

$$i_R = V_{Cr} \cdot \sqrt{\frac{Cr}{Lr}} \quad (\text{eq. 28})$$

There are several limits that need to be considered. The time needs to be less than 1 μs. The value of the peak current needs to be less than the maximum peak current the power FET can handle. Table 1 shows this variation where Cr is 1000 pF and VCr = 86.4 V using Equation 25.

The construction of the inductor Lr is somewhat critical. The inductor should be a toroid using a powdered iron material with a ur less than 100. The reason for a toroid is to confine the flux in small space and not radiate to the rest of the circuit. Using a MicroMetals [15] toroidal core, T38–26 or T38–52, with 14 turns, an 9.6 μH inductor can be constructed. This corresponds to a transition time of just over 0.3 μs and a peak current of 0.9 A. This is considerably under the peak current rating of the MTP3N60E device.

**Table 1. Lr AND Ipeak FOR GIVEN TIMES**

Time in μs	Lr in H	Ipeak
0.2	4.05e – 06	1.357
0.3	9.12e – 06	0.905
0.4	1.62e – 05	0.679
0.5	2.53e – 05	0.543
0.6	3.65e – 05	0.452
0.7	4.96e – 05	0.388
0.8	6.48e – 05	0.339
0.9	8.21e – 05	0.302
1.0	1.01e – 04	0.271


There is an RC filter between the FET source sense resistor, Rsource, and the input to the IC, MC33364. The time constant of this RC network needs to be greater than the transition time of the snubber network. The purpose of this RC filter is to eliminate false triggering, and is often called leading edge blanking network.



## REFERENCES

- [1] Bob Haver, Semiconductors for Switching Power Supplies, Seminar handout 1985, © 1985, Motorola Inc.
- [2] Jim Spangler, “A Power Factor Corrected MOSFET, Multiple Output, Flyback Switching Supply”, Proceedings 10th PCIM '85 Conf. Oct 85, pp 19–32.
- [3] Data sheets, MC33364, MC33341, TL431, MC33072, MTP1N60E, MMBT2222, MBRS360, MRA4004, MURS160, MBT4N60E, NTD3N60 from ON Semiconductor, <http://www.onsemi.com>
- [4] Savant, Roden, Carpenter, “Electronic Design, Circuits and Systems, 2nd ed”, © 1987, 1991, Benjamin/Cummings Publishing Co., Redwood City, CA, ISBN 0–8053–0285–9, pp 38–42.
- [5] Chryssis, George C., “High-Frequency Switching Power Supplies, Design & Theory”, ©1989, 1994, McGraw–Hill, NY, ISBN 0–07–010951–6, Chapter 5.
- [6] Ondrej Pauk, AN1593, “Low Cost 1.0 A Current Source for Battery Chargers”, © 1997, Motorola Inc., <http://www.onsemi.com>
- [7] C. Basso, AN1681, “How to Keep a Flyback Switch Mode Supply Stable with a Critical-Mode Controller”, © 1999, Motorola Inc., <http://www.onsemi.com>
- [8] Petr Lidak, unpublished application note in 1996 “AC–DC battery charger (constant current with voltage limit) using the MC33364 and the MC33341.
- [9] Magnetic Ferrite Cores catalog, Butler, PA, 724–282–6955. <http://mag-inc.com>
- [10] C. McLyman, “Transformer and Inductor Design Handbook”, © 1978, Marcel Dekker, New York, NY; ISBN 0–8247–6801–9
- [11] C. McLyman, “Magnetic Core Selection for Transformers and Inductors”, © 1982, Marcel Dekker, New York, NY; ISBN 0–8247–1873–9
- [12] C. McLyman, © 1987, Designing Magnetic Components for High Frequency DC–DC Converters, Kg Magnetics, Inc., San Marino, CA; ISBN 1–883107–00–8
- [13] Rectifier Applications Handbook, HB214/D, ©1993, ISBN 0–929270–00–2; available from ON Semiconductor, Phoenix, AZ 85008
- [14] Rashid, “Power Electronics, Circuits, Devices, and Applications”; © 1988, Prentice Hall, Englewood Cliffs, NJ 07632, ISBN 0–13–687667–6, pp.18–23
- [15] MicroMetals Iron Powered Cores, Catalog 4 Issue G, ©1993, Anaheim, CA, 800–356–5977

TMOS is a trademark of Semiconductor Components Industries, LLC (SCILLC) or its subsidiaries in the United States and/or other countries.

ON Semiconductor and the  are registered trademarks of Semiconductor Components Industries, LLC (SCILLC) or its subsidiaries in the United States and/or other countries. SCILLC owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of SCILLC's product/patent coverage may be accessed at [www.onsemi.com/site/pdf/Patent-Marking.pdf](http://www.onsemi.com/site/pdf/Patent-Marking.pdf). SCILLC reserves the right to make changes without further notice to any products herein. SCILLC makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does SCILLC assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. “Typical” parameters which may be provided in SCILLC data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including “Typicals” must be validated for each customer application by customer's technical experts. SCILLC does not convey any license under its patent rights nor the rights of others. SCILLC products are not designed, intended, or authorized for use as components in systems intended for surgical implant into the body, or other applications intended to support or sustain life, or for any other application in which the failure of the SCILLC product could create a situation where personal injury or death may occur. Should Buyer purchase or use SCILLC products for any such unintended or unauthorized application, Buyer shall indemnify and hold SCILLC and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that SCILLC was negligent regarding the design or manufacture of the part. SCILLC is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

## PUBLICATION ORDERING INFORMATION

**LITERATURE FULFILLMENT:**  
Literature Distribution Center for ON Semiconductor  
19521 E. 32nd Pkwy, Aurora, Colorado 80011 USA  
**Phone:** 303–675–2175 or 800–344–3860 Toll Free USA/Canada  
**Fax:** 303–675–2176 or 800–344–3867 Toll Free USA/Canada  
**Email:** [orderlit@onsemi.com](mailto:orderlit@onsemi.com)

**N. American Technical Support:** 800–282–9855 Toll Free  
USA/Canada  
**Europe, Middle East and Africa Technical Support:**  
Phone: 421 33 790 2910  
**Japan Customer Focus Center**  
Phone: 81–3–5817–1050

**ON Semiconductor Website:** [www.onsemi.com](http://www.onsemi.com)  
**Order Literature:** <http://www.onsemi.com/orderlit>  
For additional information, please contact your local Sales Representative