

# ON Semiconductor

## Is Now

# onsemi™

To learn more about onsemi™, please visit our website at  
[www.onsemi.com](http://www.onsemi.com)

---

**onsemi** and **onsemi** and other names, marks, and brands are registered and/or common law trademarks of Semiconductor Components Industries, LLC dba "**onsemi**" or its affiliates and/or subsidiaries in the United States and/or other countries. **onsemi** owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of **onsemi** product/patent coverage may be accessed at [www.onsemi.com/site/pdf/Patent-Marking.pdf](http://www.onsemi.com/site/pdf/Patent-Marking.pdf). **onsemi** reserves the right to make changes at any time to any products or information herein, without notice. The information herein is provided "as-is" and **onsemi** makes no warranty, representation or guarantee regarding the accuracy of the information, product features, availability, functionality, or suitability of its products for any particular purpose, nor does **onsemi** assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using **onsemi** products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by **onsemi**. "Typical" parameters which may be provided in **onsemi** data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. **onsemi** does not convey any license under any of its intellectual property rights nor the rights of others. **onsemi** products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use **onsemi** products for any such unintended or unauthorized application, Buyer shall indemnify and hold **onsemi** and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that **onsemi** was negligent regarding the design or manufacture of the part. **onsemi** is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner. Other names and brands may be claimed as the property of others.



ON Semiconductor

# 1 W, Dual Output, Off-line Converter

Device	Application	Input Voltage	Output Power	Topology	I/O Isolation
NCP1012	Auxiliary off-line power supply for appliances	85 to 270 Vac	1 W	Buck/Flyback	None

Other Specifications				
	Output 1	Output 2	Output 3	Output 4
<b>Output Voltage</b>	- 5 V	- 12 V	N/A	N/A
<b>Ripple</b>	100 mV	200 mV	N/A	N/A
<b>Nominal Current</b>	100 mA	50 mA	N/A	N/A
<b>Max Current</b>	100 mA	50 mA	N/A	N/A
<b>Min Current</b>	10 mA	0 mA	N/A	N/A

<b>PFC (Yes/No)</b>	Passive due to low input C
<b>Minimum Efficiency</b>	70%
<b>Operating Temp Range</b>	0 to +55 °C
<b>Cooling Method/Supply Orientation</b>	Convection

## Circuit Description

This design is intended for low power applications where 5 V and/or 12 V may be necessary for control circuits in appliances or similar devices in which mains isolation is not required and low cost and simplicity are mandatory. The topology is an off-line buck converter configured for a 5 volt negative output with an additional negative 12 volt output derived from a secondary flyback winding on the buck choke. The schematic notes detail how this circuit can be converted for positive outputs if desired.


The input section uses half-wave rectification for simplicity and allows the output common to be referenced to the mains neutral line. An input EMI filter is provided for conducted emissions compliance. Good output cross regulation is achieved on the 12 V output with the use of stacked windings in the buck choke. Regulation feedback is achieved with a simple zener diode and optocoupler circuit that also provides the required offset floating for the NCP1012 controller.

## Key Features

- Extremely simple and cost effective low power supply to provide non-isolated, low voltage outputs.
- Good cross regulation due to stacked windings in the buck choke.
- Low cost monolithic NCP1012 integrated controller with self-biased Vcc used for buck converter.
- EMI filter on AC input for agency compliance.
- Output polarities easily reversible without component changes.
- Over current protection.
- 2 watt capability if NCP1014 is used for U1.

# DN06002/D

## Schematic

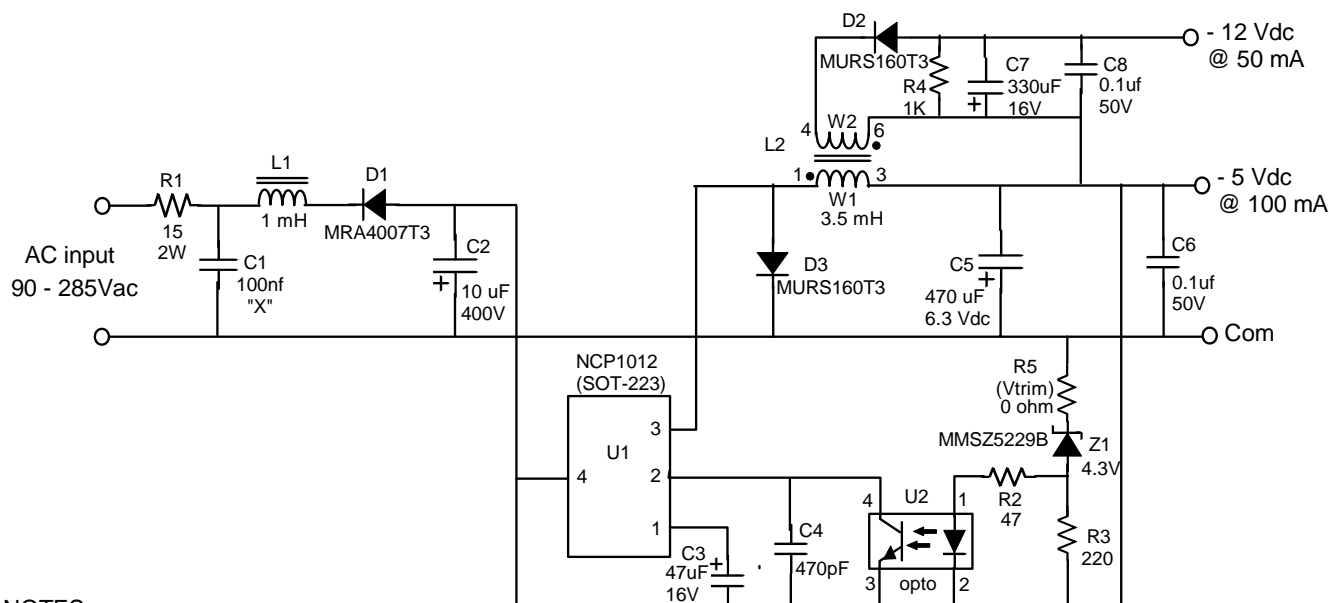

### NOTES:

1. Crossed lines on schematic are not connected.
2. U1 should have ground tab (pin 4) soldered to expanded ground plane area for good heatsinking (SOT-223 recommended package).
3. U2 is Vishay H11A817A optocoupler or equivalent
4. R1 provides inrush limiting at turn-on (optional).
5. C5 capacitance value dependent on max Vout ripple; 470 uF min recommended.
6. L1 is Cooper/Bussmann UP2B-102R inductor (Uni-Pac series - 1 mH, 0.3 A) or similar.
7. L2 is P18/11/I ferrite core (1811 pot core without hole) on 6 pin pc mount bobbin;  
W1 is 92 turns of #32HN (0.25 mm dia) magnet wire wound over 4 layers (23 turns per layer).  
W2 is 115 turns of #32 HN magnet wire wound over 5 layers (23 turns per layer).  
Core should be gapped to give an inductance of 3.4 to 3.6 mH across W1.
8. R5 is option voltage trim resistor - increasing resistance increases Vout.
9. For positive outputs: reverse diodes D1, D2, and D3; apply dc input to pin 3 of U1 and output will be on pin 4; reverse voltage sensing so cathode of zener goes to 5V output and pin 2 of U2 (opto) goes to output common; reverse polarity of input and output caps C2, C5 and C7.

**NCP1012 1 Watt, Dual Output Converter**  
ON Semiconductor Applications Group

© 2006 ON Semiconductor.

**Disclaimer:** ON Semiconductor is providing this design note "AS IS" and does not assume any liability arising from its use; nor does ON Semiconductor convey any license to its or any third party's intellectual property rights. This document is provided only to assist customers in evaluation of the referenced circuit implementation and the recipient assumes all liability and risk associated with its use, including, but not limited to, compliance with all regulatory standards. ON Semiconductor may change any of its products at any time, without notice.

Design note created by Frank Cathell, e-mail: [f.cathell@onsemi.com](mailto:f.cathell@onsemi.com)