



# Loop Stabilization with NCP1060

---


Christophe Basso – Technical Fellow  
IEEE Senior Member

**ON Semiconductor®**



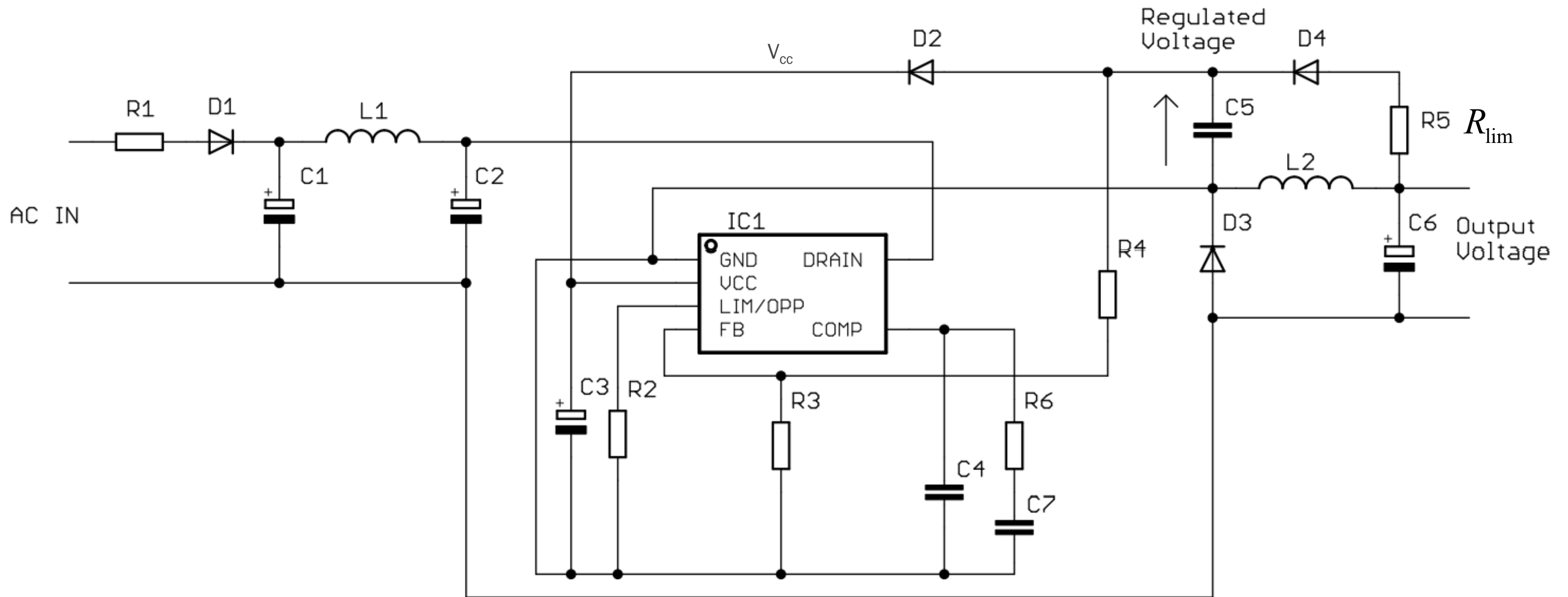
# Application Schematic

The NCP1060 lends itself well to building non-isolated buck converters. The feedback is made by reconstructing the output voltage  $V_{out}$  during the off-time period. This voltage is then internally compared to perform regulation.


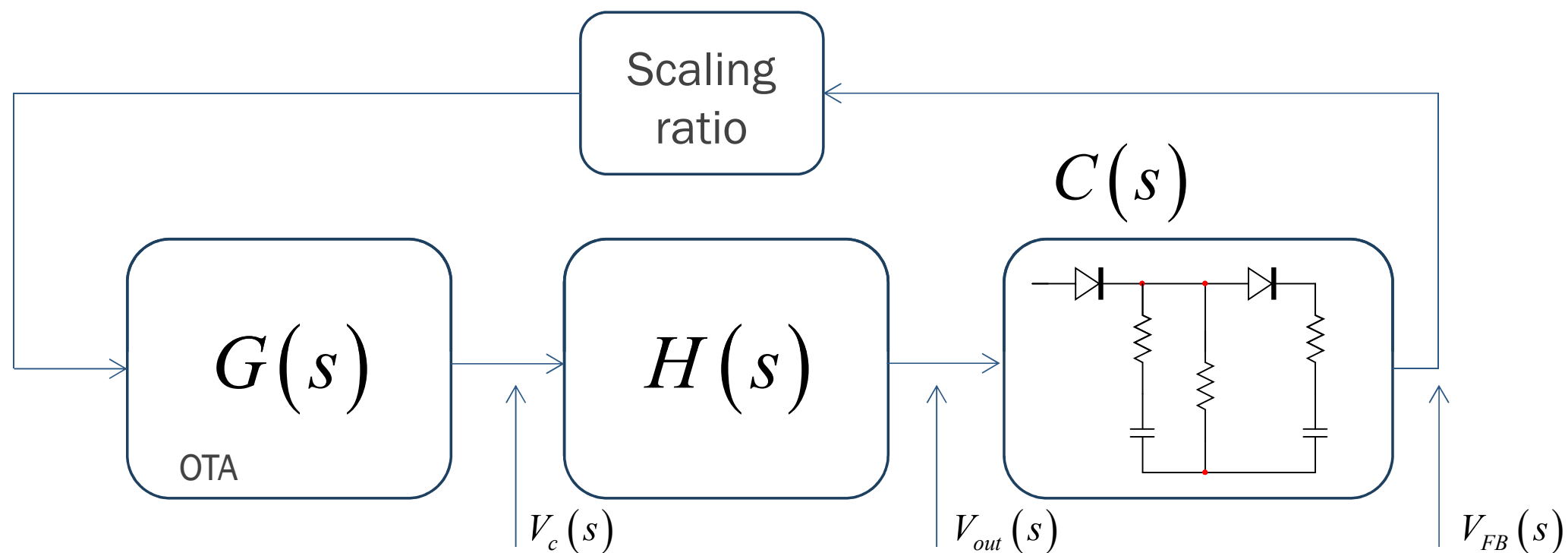
# Small-Signal Model

Before attempting to stabilize any converter, we need its control-to-output transfer function  $H(s)$ . However, in our case, we do not directly observe  $V_{out}$  but an image of it, adding a second transfer function.



The second transfer function  $C(s)$  is cascaded with that of the plant to form the dynamic response we need. From this response and based on the requirement (crossover frequency and phase margin), we can deduce a compensation strategy.

# The Power Plant Dynamic Response

The plant control-to-output transfer function is that of a CCM-operated current-mode buck converter:

$$H(s) \approx H_0 \frac{1 + \frac{s}{\omega_{z_1}}}{1 + \frac{s}{\omega_{p_1}}} \frac{1}{1 + \frac{s}{\omega_n Q} + \left(\frac{s}{\omega_n}\right)^2} \quad H_0 = \frac{R}{R_i} \frac{1}{1 + \frac{RT_{sw}}{L} [m_c(1-D) - 0.5]} \quad \omega_{z_1} = \frac{1}{r_c C}$$

$$\omega_{p_1} = \frac{1}{RC} + \frac{T_{sw}}{LC} [m_c(1-D) - 0.5] \quad \omega_n = \frac{\pi}{T_{sw}} \quad Q = \frac{1}{\pi [m_c(1-D) - 0.5]} \quad m_c = 1 + \frac{S_e}{S_n} \begin{array}{l} \text{Artificial ramp} \\ \text{Inductor on slope} \end{array}$$

In NCP1060, with have:

$$R_i = 300 \text{ m}\Omega \quad S_a = 8.4 \text{ mA}/\mu\text{s} \quad 1060/60 \text{ kHz} \quad S_a = 14 \text{ mA}/\mu\text{s} \quad 1060/100 \text{ kHz}$$

$$S_a = 15.6 \text{ mA}/\mu\text{s} \quad 1063/60 \text{ kHz} \quad S_a = 26 \text{ mA}/\mu\text{s} \quad 1063/100 \text{ kHz}$$

R. B. Ridley, *A new Continuous-Time Model for CM Control*, IEEE Transactions of Power Electronics, Vol. 6, April 1991





# Operating Conditions – Power Stage Alone

$$F_{sw} := 60\text{kHz} \quad L_1 := 1\text{mH} \quad R_L := 30\Omega \quad V_{in} := 125\text{V} \quad V_{out} := 14\text{V}$$

$$r_C := 0.2\Omega \quad C_{out} := 20\mu\text{F} \quad T_{sw} := \frac{1}{F_{sw}} = 16.667\mu\text{s}$$

$$T_{sw} := \frac{1}{F_{sw}} \quad S_e := \frac{V_{in} - V_{out}}{L_1} = 111 \frac{\text{kA}}{\text{s}} \quad S_a := 8.4 \frac{\text{mA}}{\mu\text{s}} \quad R_i := 0.3\Omega$$

$$m_c := 1 + \frac{S_a}{S_e} = 1.076 \quad D := \frac{V_{out}}{V_{in}} = 11.2\% \quad H_{div} := 0.078$$


$$H_0 := H_{div} \cdot \frac{R_L}{R_i} \cdot \frac{1}{1 + \frac{R_L \cdot T_{sw}}{L_1} \cdot [m_c \cdot (1 - D) - 0.5]} \quad 20 \cdot \log(H_0) = 16.061 \quad \text{dB}$$

↑  
Internal divider

$$\omega_{z1} := \frac{1}{r_C \cdot C_{out}} \quad \omega_{p1} := \frac{1}{R_L \cdot C_{out}} + \frac{T_{sw}}{L_1 \cdot C_{out}} \cdot [m_c \cdot (1 - D) - 0.5]$$



$$\omega_n := \frac{\pi}{T_{sw}} \quad Q_p := \frac{1}{\pi \cdot [m_c \cdot (1 - D) - 0.5]} = 0.699$$
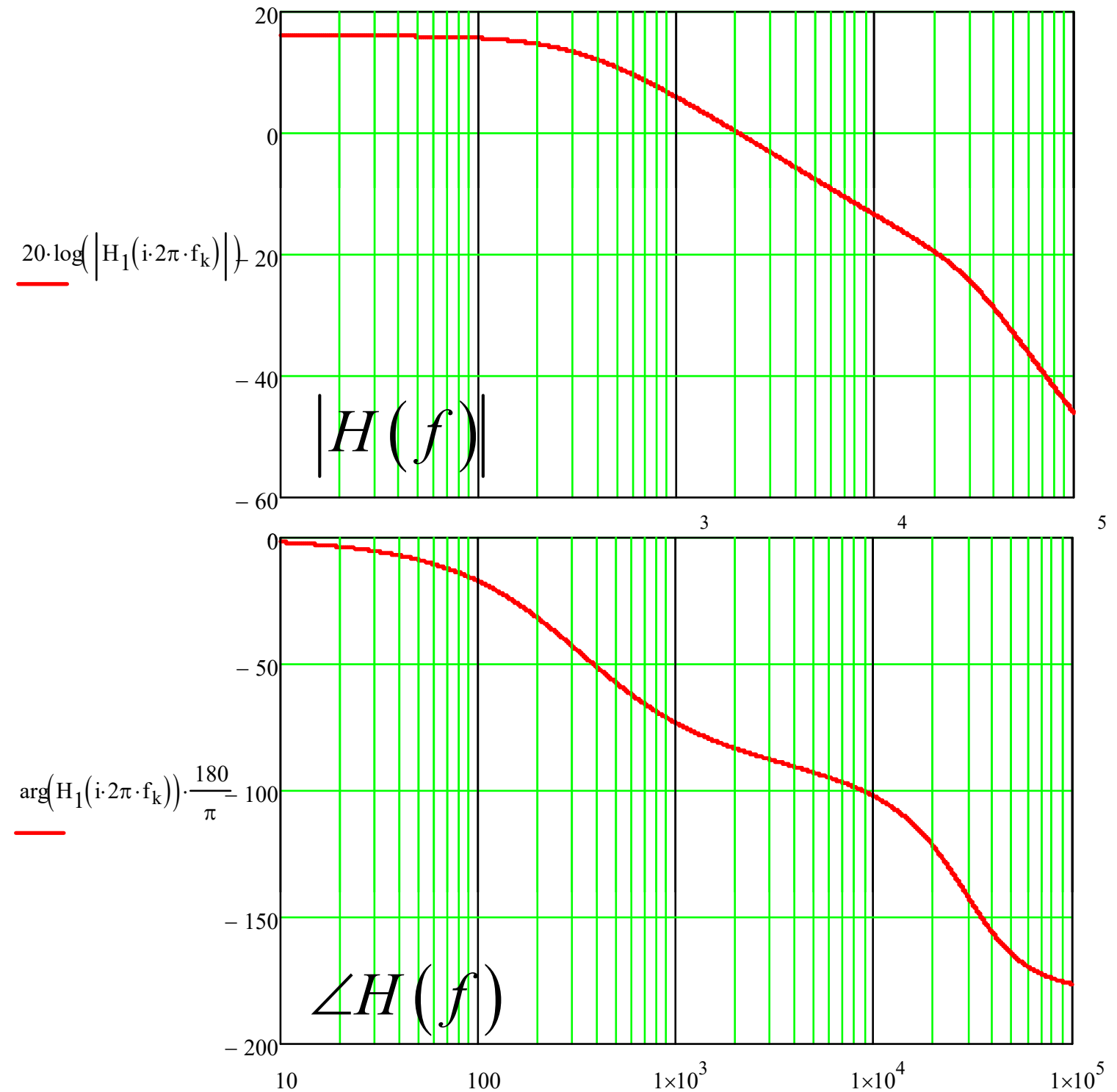
$$H_1(s) := H_0 \cdot \frac{1 + \frac{s}{\omega_{z1}}}{1 + \frac{s}{\omega_{p1}}} \cdot \frac{1}{1 + \frac{s}{\omega_n \cdot Q_p} + \left(\frac{s}{\omega_n}\right)^2}$$




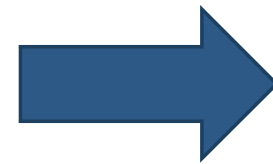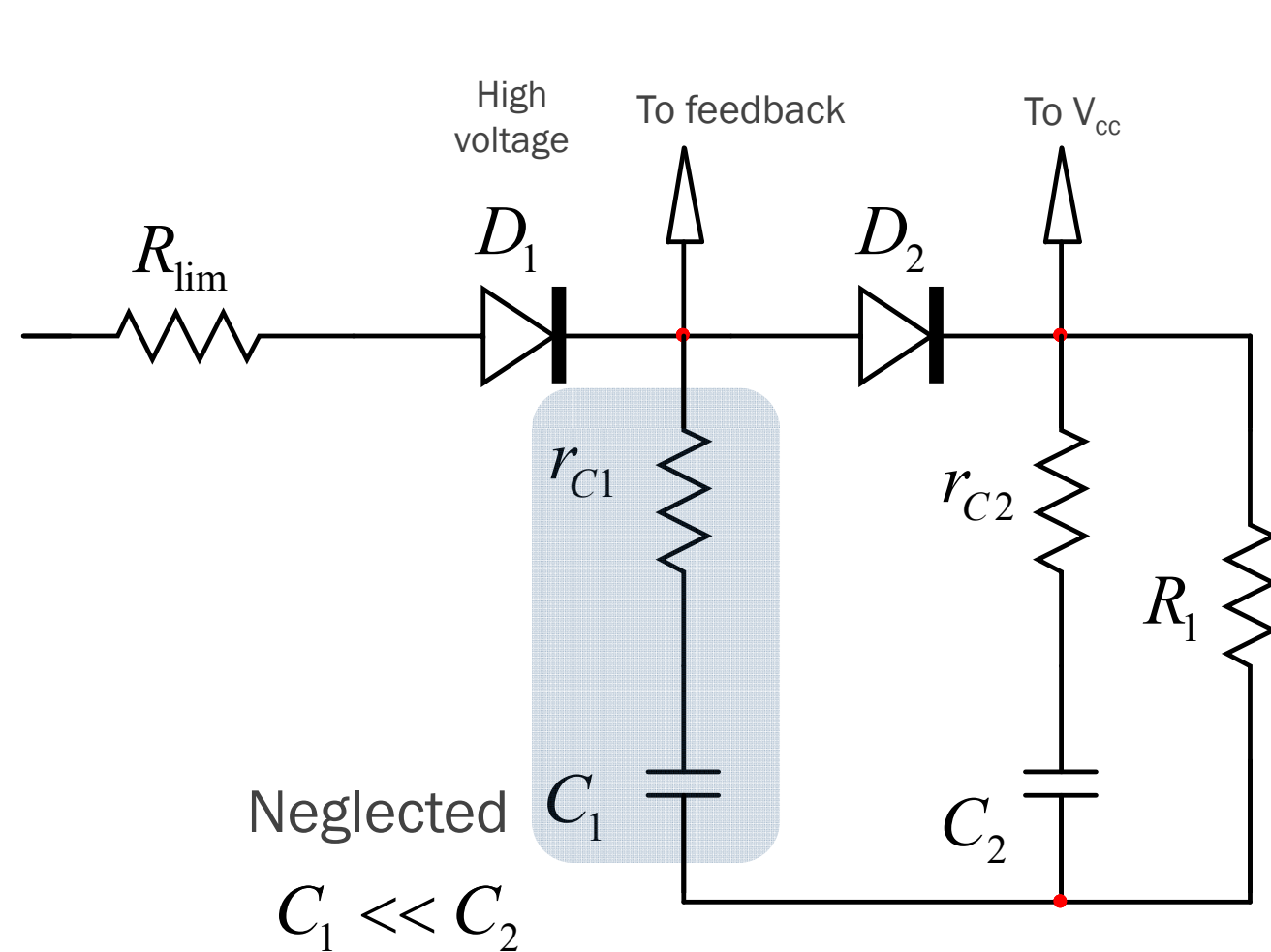
# Output Voltage Image

The circuit does not regulate  $V_{out}$  directly but an image obtained during the freewheeling operation. The rectifying diode is affected by a dynamic resistance  $r_d$ . The whole thing is then loaded by the  $V_{cc}$  capacitor and the IC consumption.



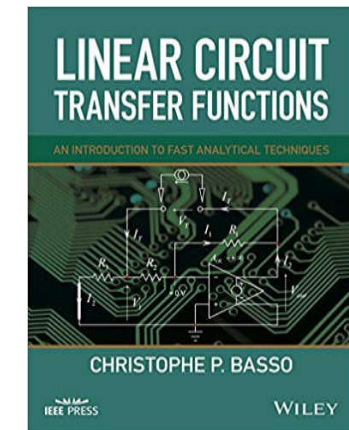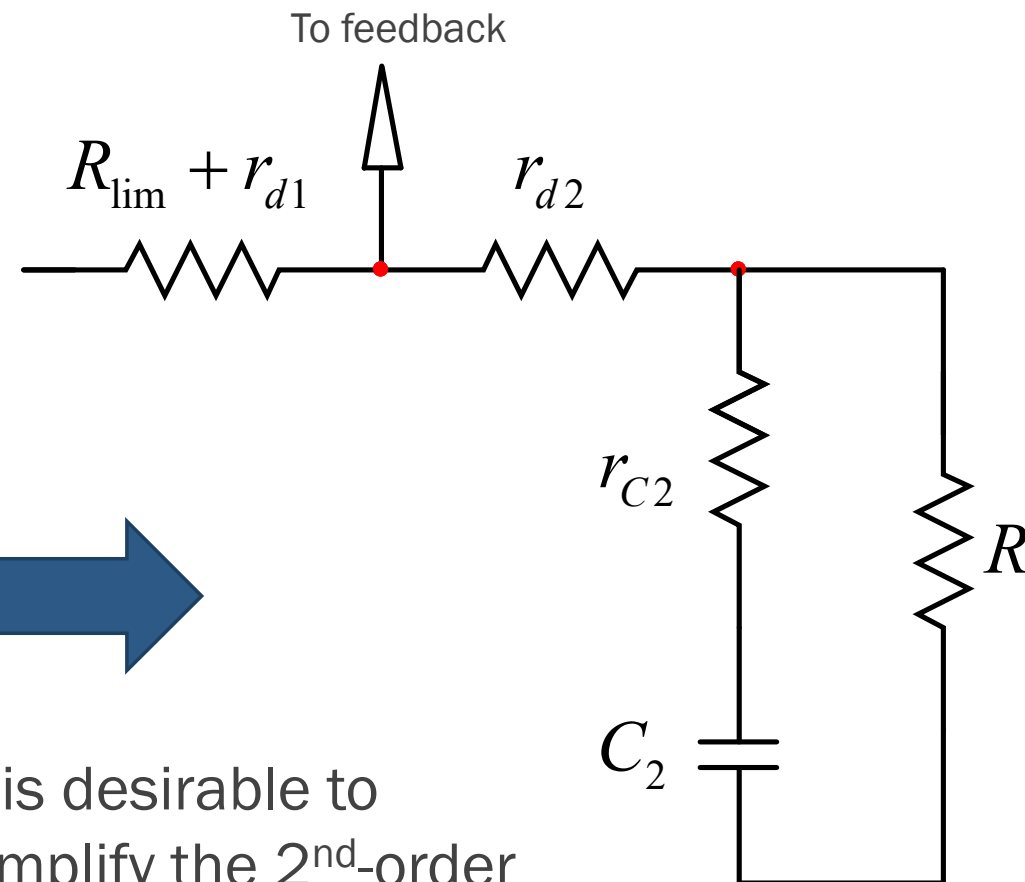It is desirable to simplify the 2<sup>nd</sup>-order circuitry to a 1<sup>st</sup>-order circuit for analysis.



Apply  
the  
FACTs!

$$C(s) = C_0 \frac{1 + \frac{s}{\omega_{z_2}}}{1 + \frac{s}{\omega_{p_2}}}$$


$$C_0 = \frac{R_1 + r_{d2}}{(R_{lim} + r_{d1}) + r_{d2} + R_1}$$

$$\omega_{z_2} = \frac{1}{C_2 [r_{C2} + r_{d2} \parallel R_1]}$$

$$\omega_{p_2} = \frac{1}{[R_1 \parallel (r_{d1} + R_{lim} + r_{d2}) + r_{C2}] C_2}$$



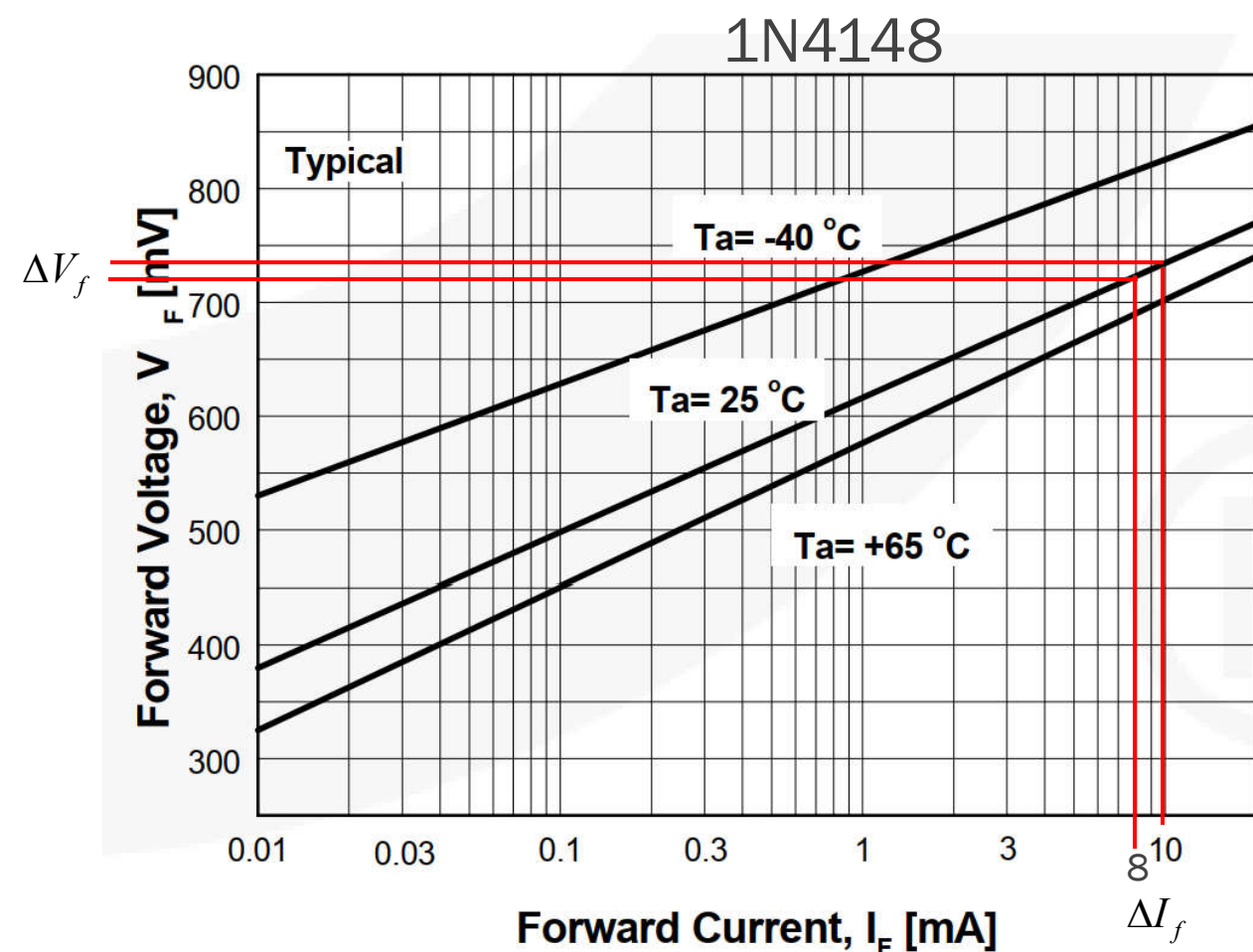
# Extracting the Diode Dynamic Resistance

You have to know the rectifying diode dynamic resistance to calculate  $C(s)$ :



1N4148:
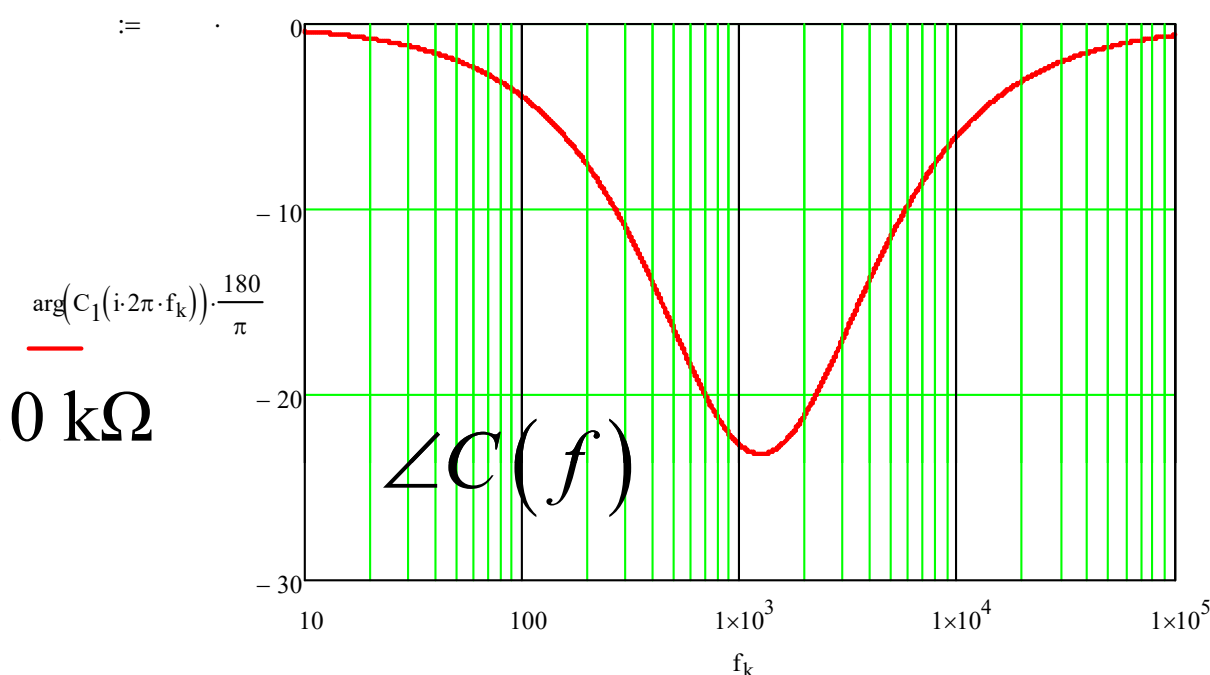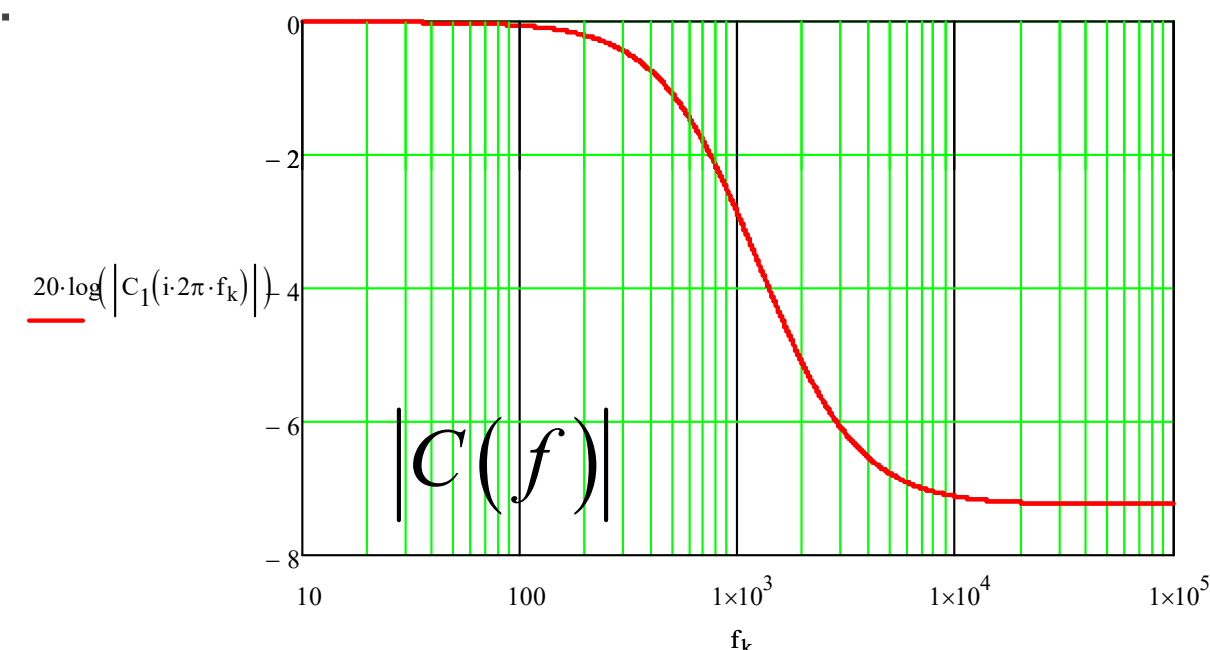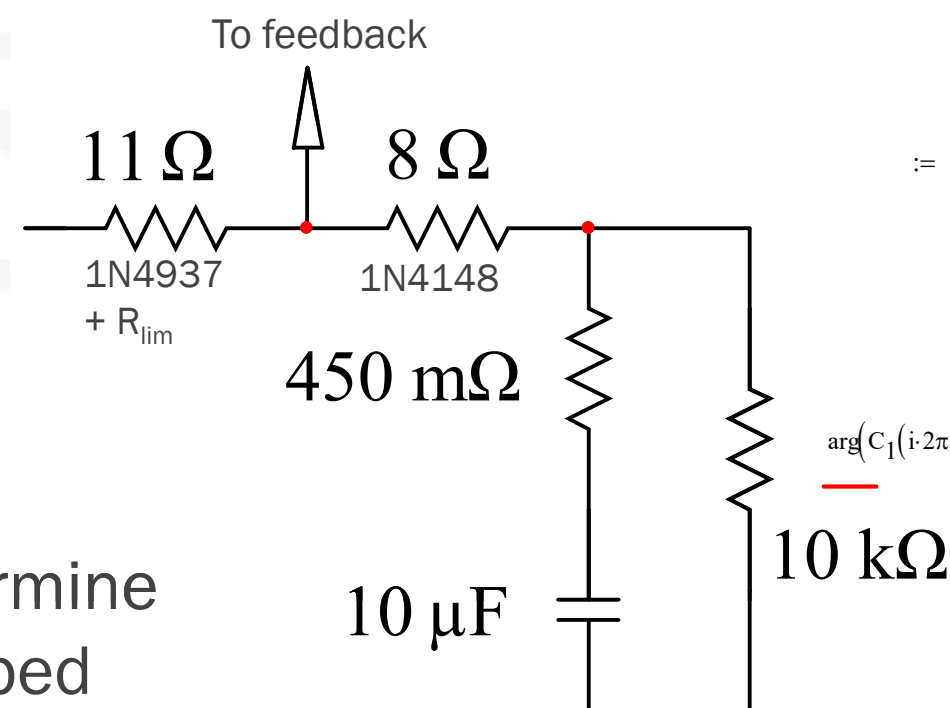
$$r_d = \frac{\Delta V_f}{\Delta I_f} = \frac{16\text{m}}{2\text{m}} = 8\text{ }\Omega$$



The 1N4937 resistance is difficult to determine at low  $I_d$ . It is assumed to be  $1\text{ }\Omega$  and lumped into an  $11\text{-}\Omega$  term considering  $10\text{ }\Omega$  for  $R_{lim}$ .

# The Control-to-Output Transfer Function

The final transfer function is the cascading of the plant expression with the extra filter going to the feedback pin:


$$H_{final}(s) \approx H_0 \frac{1 + \frac{s}{\omega_{z_1}}}{1 + \frac{s}{\omega_{p_1}}} \frac{1}{1 + \frac{s}{\omega_n Q} + \left(\frac{s}{\omega_n}\right)^2} C_0 \frac{1 + \frac{s}{\omega_{z_2}}}{1 + \frac{s}{\omega_{p_2}}}$$

Select a 1-kHz crossover frequency and extract data from the plots:

$$|H_{final}(1 \text{ kHz})| = 3 \text{ dB} \longrightarrow G_{f_c}$$

$$\angle H_{final}(1 \text{ kHz}) \approx -96^\circ \longrightarrow pf_c$$

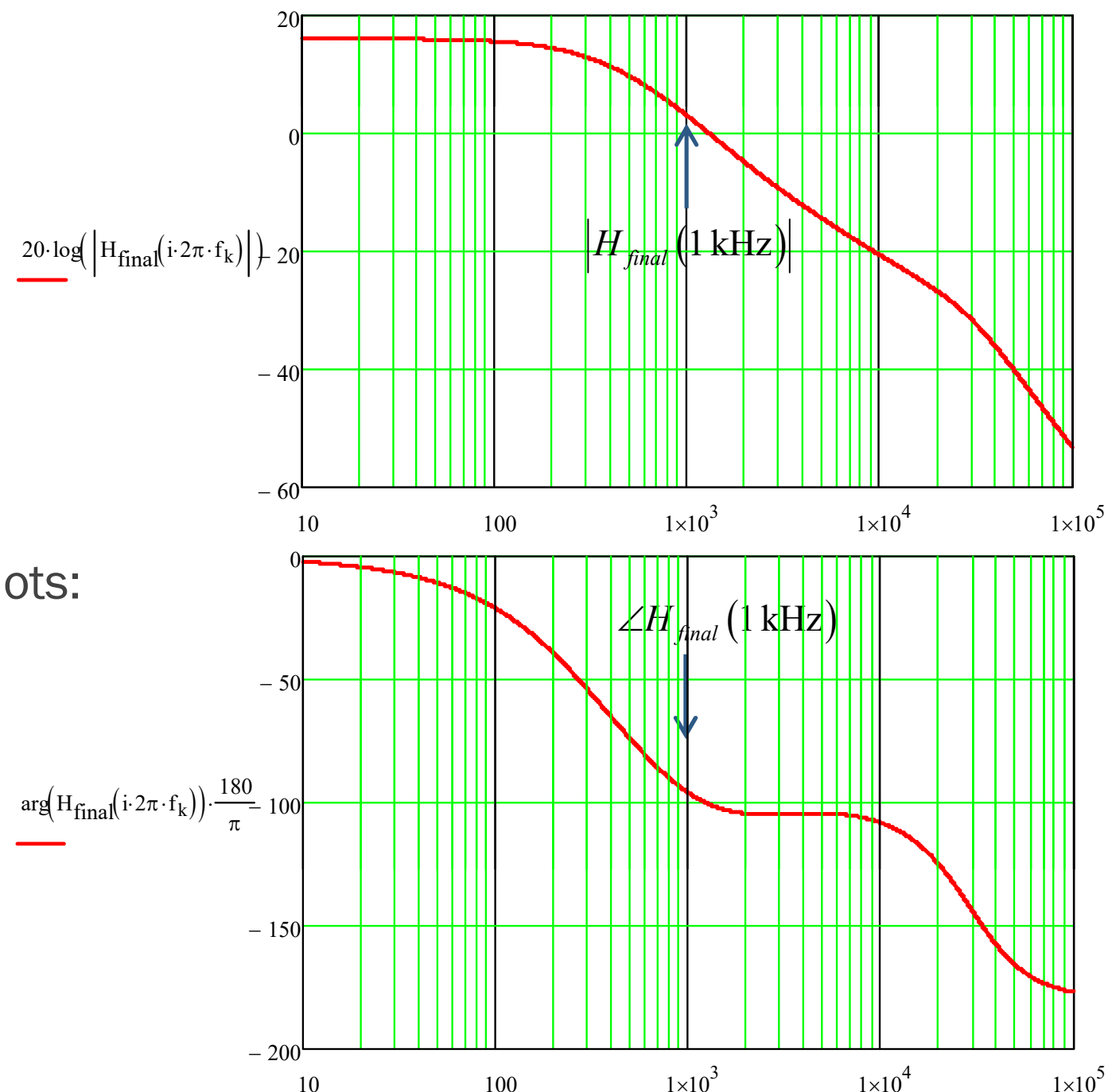Choose a phase margin goal, PM=70° for instance





# Determine how to Position Poles and Zeroes

The  $k$  factor method works well for current-controlled power converters:

$$G_{10} = 10^{\frac{-G_{fc}}{20}} \approx 0.71$$

$$boost = pm - (pf_c) - 90^\circ = 70^\circ - (-96^\circ) - 90^\circ \approx 76^\circ \quad k = \tan\left(\frac{boost}{2} + 45^\circ\right) = 8.123$$

$$f_z = \frac{f_c}{k} = 123 \text{ Hz} \quad f_p = k \cdot f_c = 8.1 \text{ kHz}$$

$$R_2 = \frac{G_{10} f_p}{f_p - f_z} \frac{R_{lower} + R_1}{R_{lower} g_m} \frac{\sqrt{1 + \left(\frac{f_c}{f_p}\right)^2}}{\sqrt{1 + \left(\frac{f_z}{f_c}\right)^2}} = 1.5 \text{ k}\Omega$$


Resistive divider network  
↓ ↓

$$C_1 = \frac{1}{2\pi f_z R_2} \approx 835 \text{ nF}$$

$$C_2 = \frac{R_{lower} g_m}{2\pi f_p G_{10} (R_{lower} + R_1)} \frac{\sqrt{1 + \left(\frac{f_z}{f_c}\right)^2}}{\sqrt{1 + \left(\frac{f_c}{f_p}\right)^2}} = 12.8 \text{ nF}$$

D. Venable, *The  $k$  Factor: a New Mathematical Tool for Stability Analysis and Synthesis*, Proceedings of Powercon 10, 1983

# Type 2 Transfer Function with an OTA

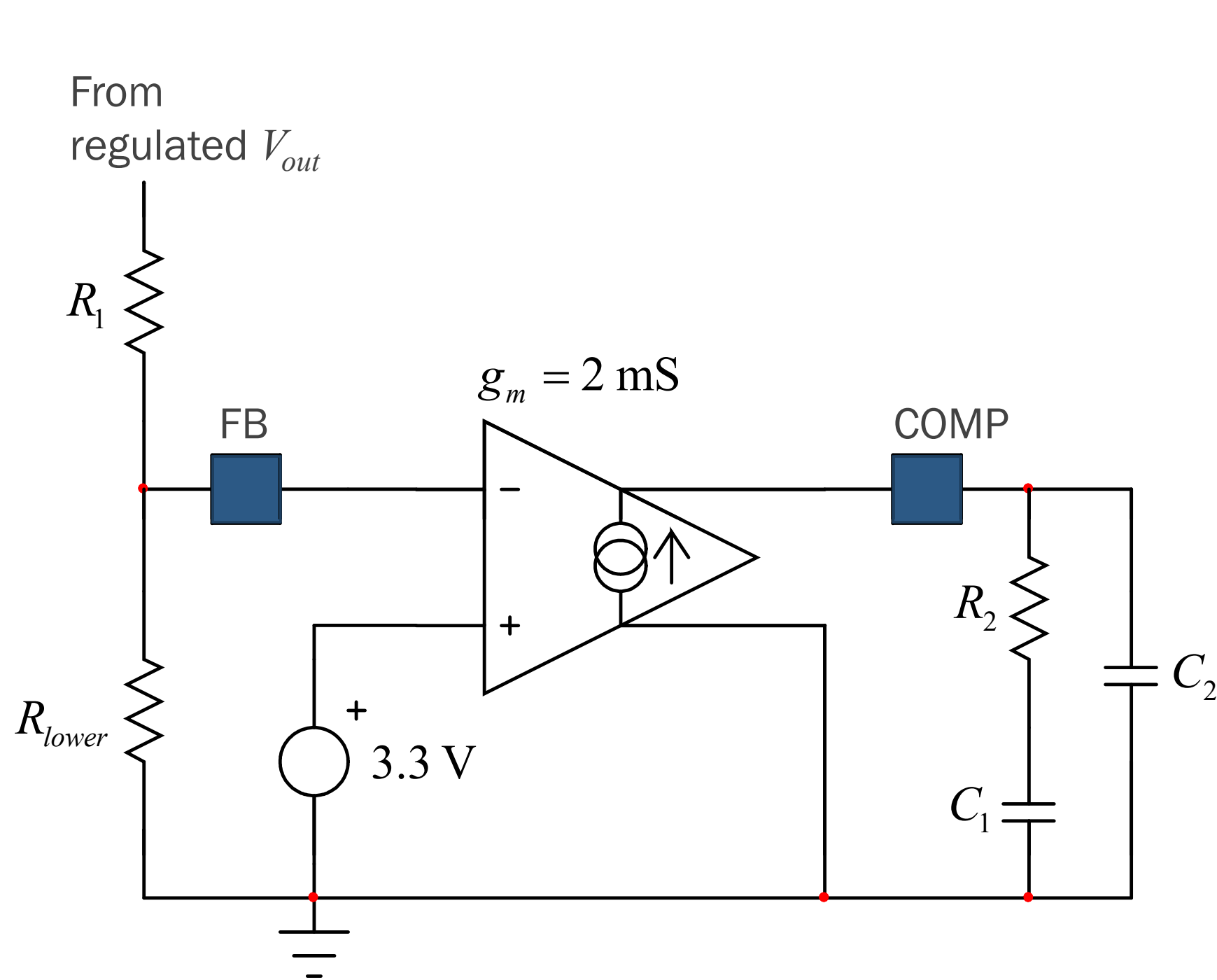

$$G(s) = -G_0 \frac{1 + \frac{\omega_z}{s}}{1 + \frac{s}{\omega_p}} \quad \omega_z = \frac{1}{R_2 C_1}$$

$$\omega_p = \frac{1}{R_2 \left( \frac{C_1 C_2}{C_1 + C_2} \right)} \quad G_0 = \frac{R_2 C_1}{C_1 + C_2} \frac{g_m R_{lower}}{R_{lower} + R_1}$$

Select  $R_2$  to compensate gain/attenuation at  $f_c$




$$R_2 = \frac{G_{10} f_p}{f_p - f_z} \frac{R_{lower} + R_1}{g_m R_1} \frac{\sqrt{1 + \left( \frac{f}{f_p} \right)^2}}{\sqrt{1 + \left( \frac{f_z}{f} \right)^2}}$$


C. Basso, *Designing Control Loops for Linear and Switching Power Supplies*, Artech House 2012
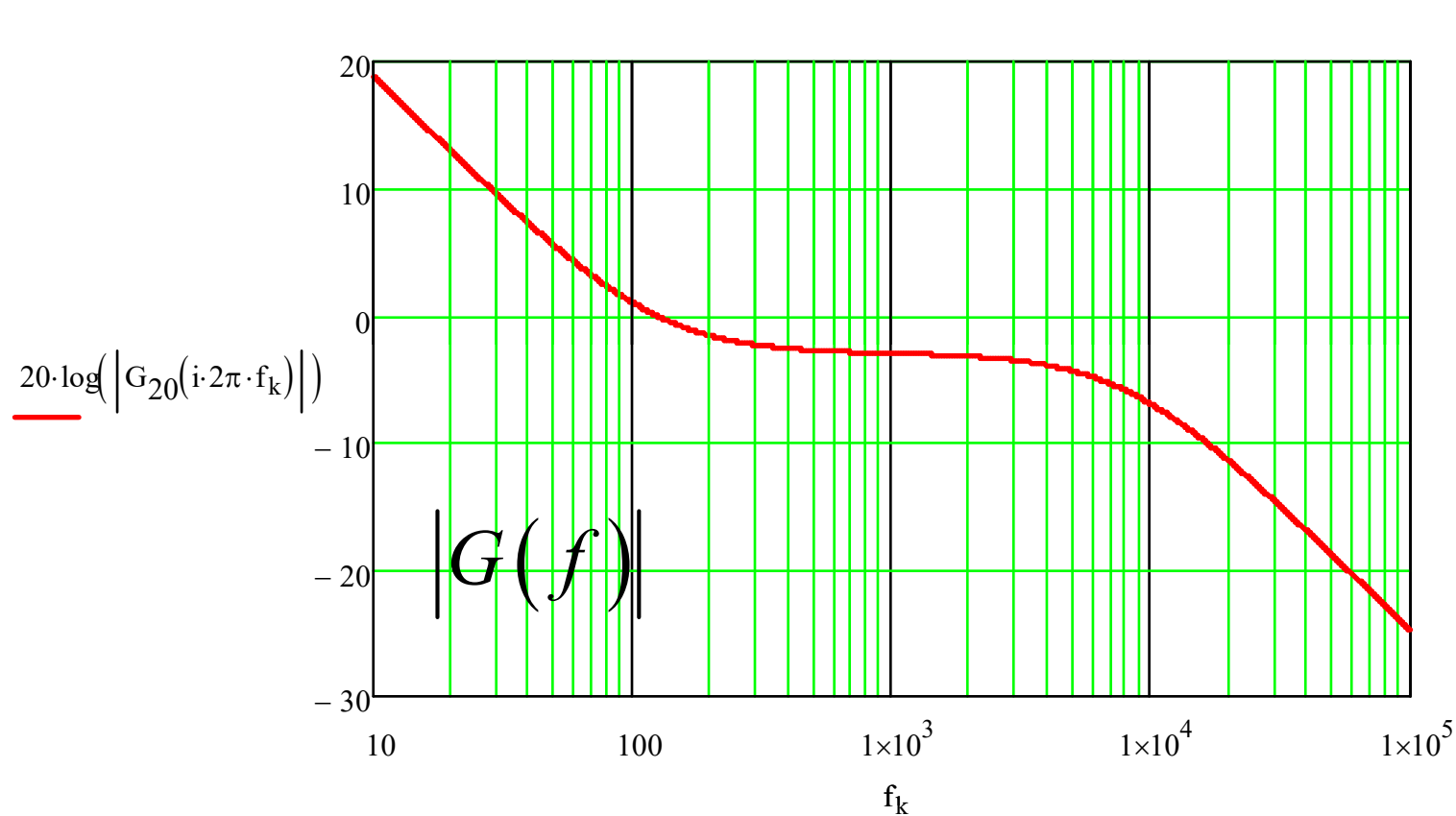
# Dynamic Response of the Type-2 Compensator

The phase response is boosted between the zero and the pole. The peak occurs at the selected crossover frequency.





Plot the loop gain

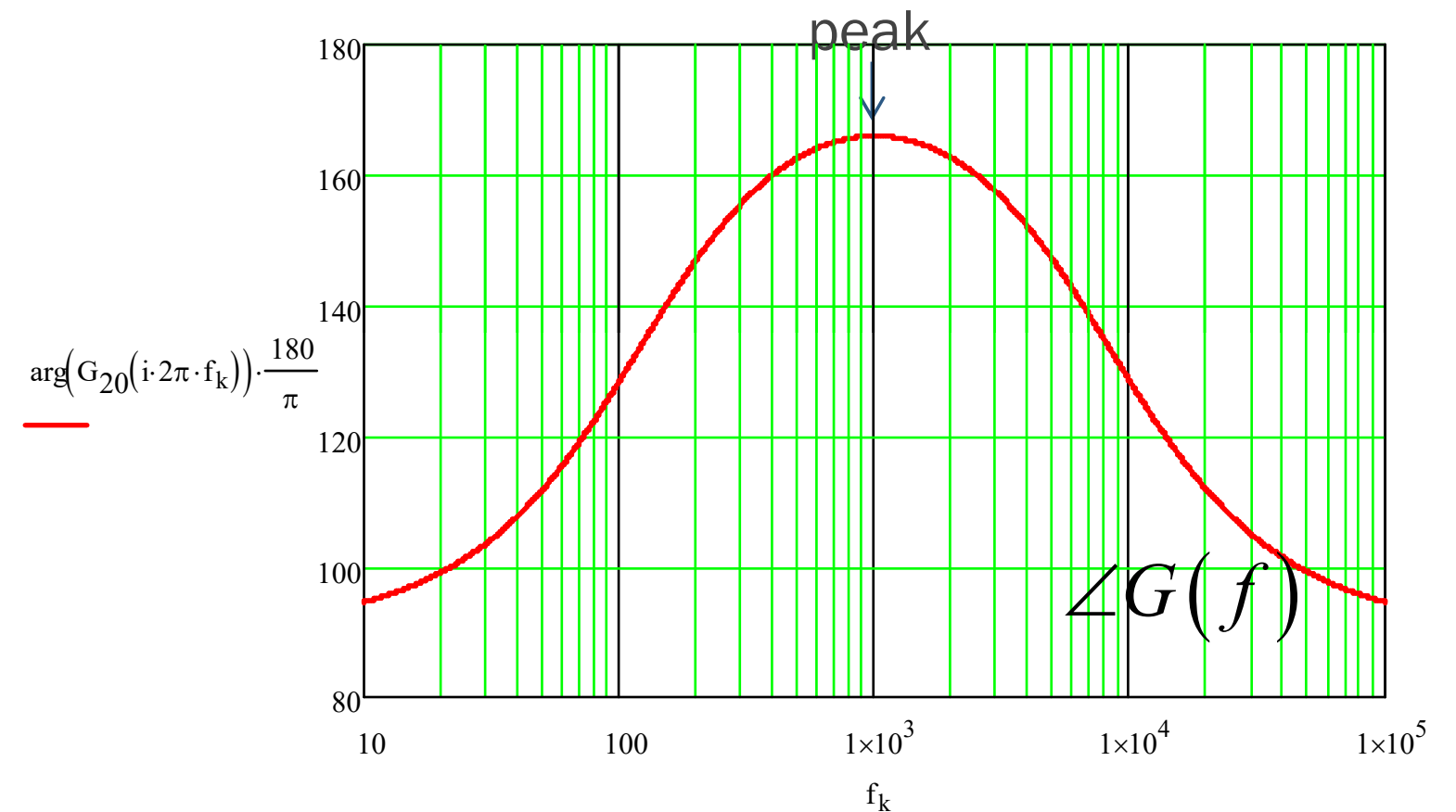

# Plot the Compensated Loop Gain



The loop gain is obtained by cascading the plant transfer function with the compensator transfer function

$$T(s) = H(s)C(s)G(s)$$

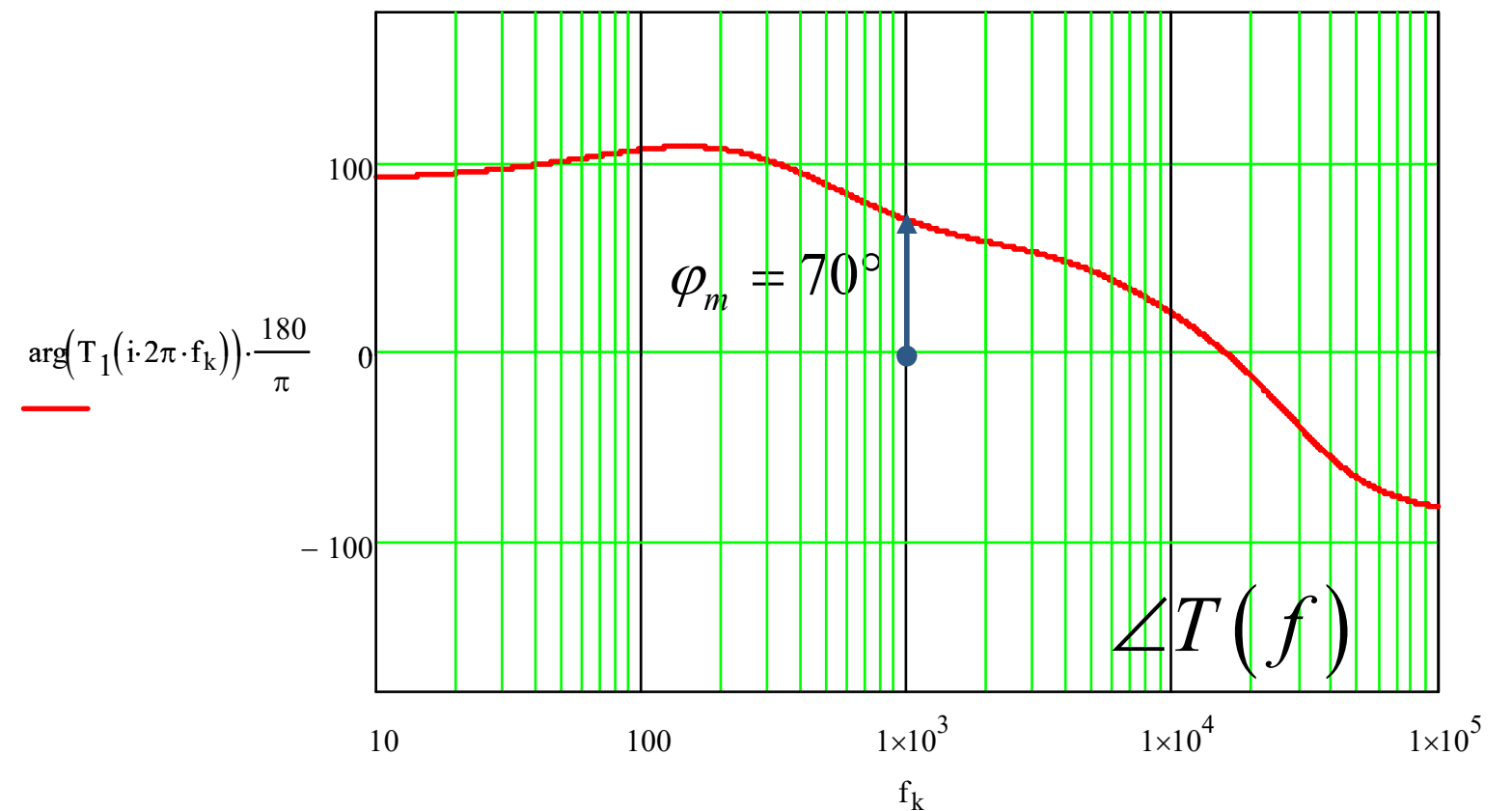
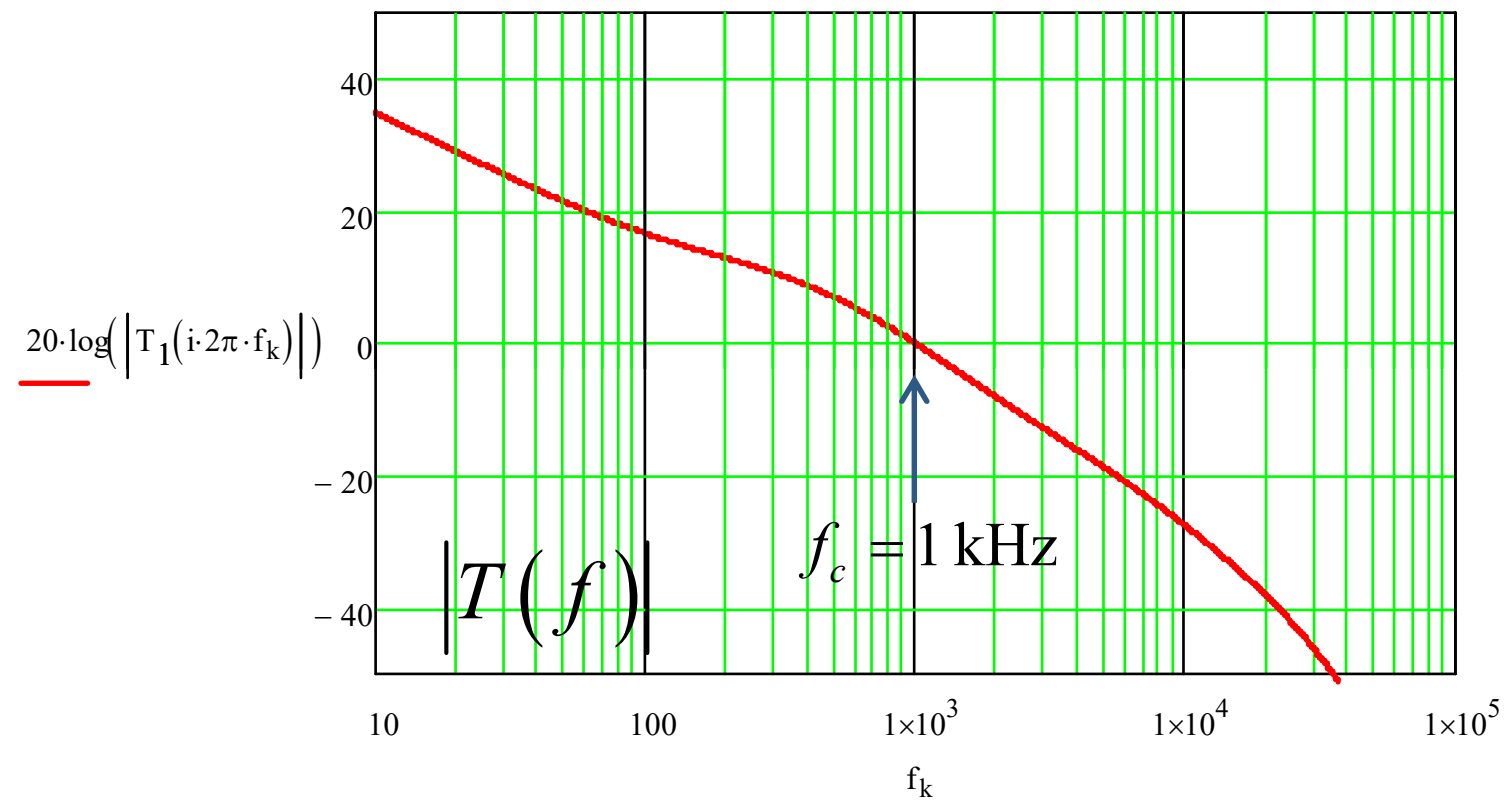




# Simulate with SIMPLIS®

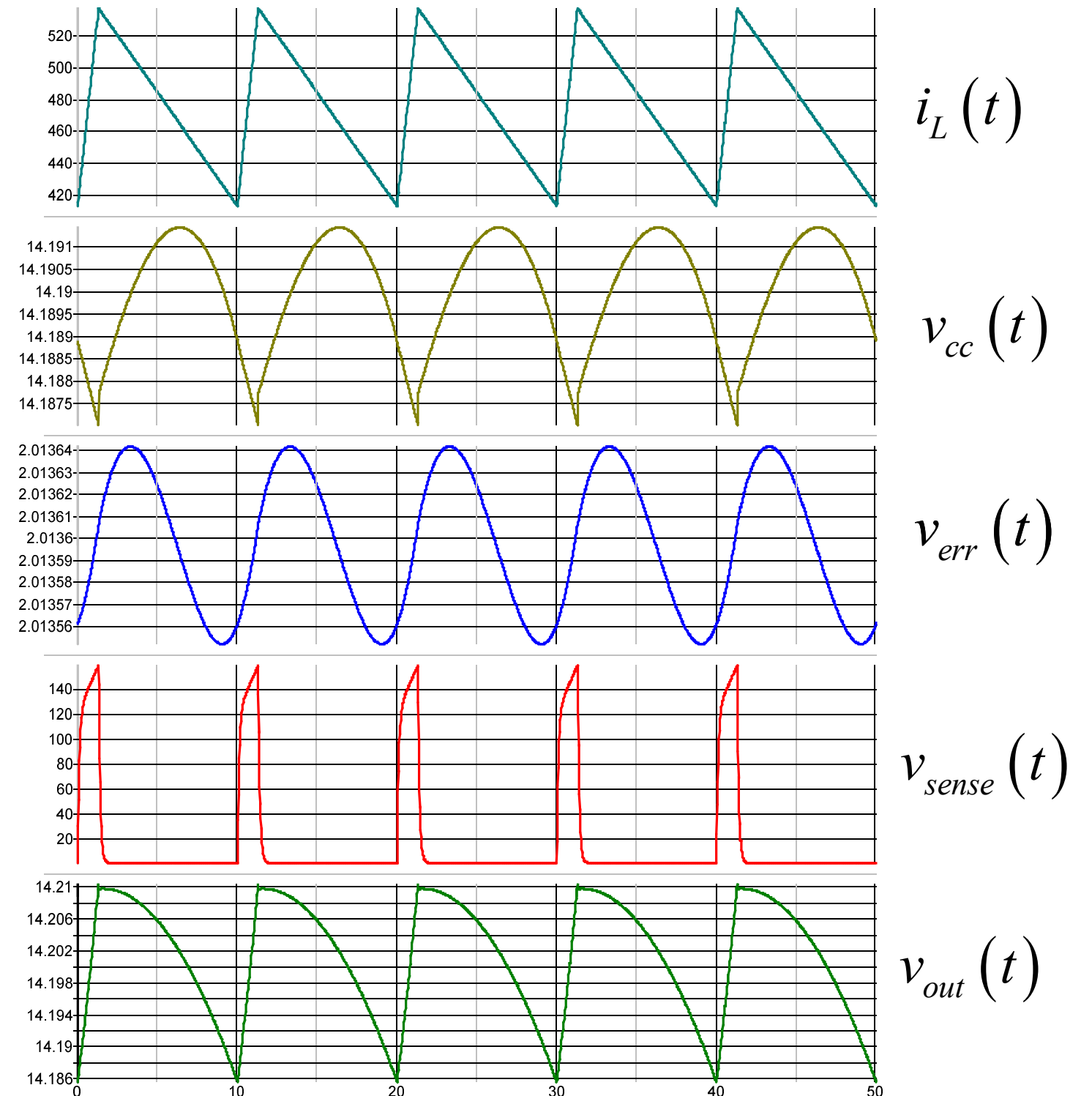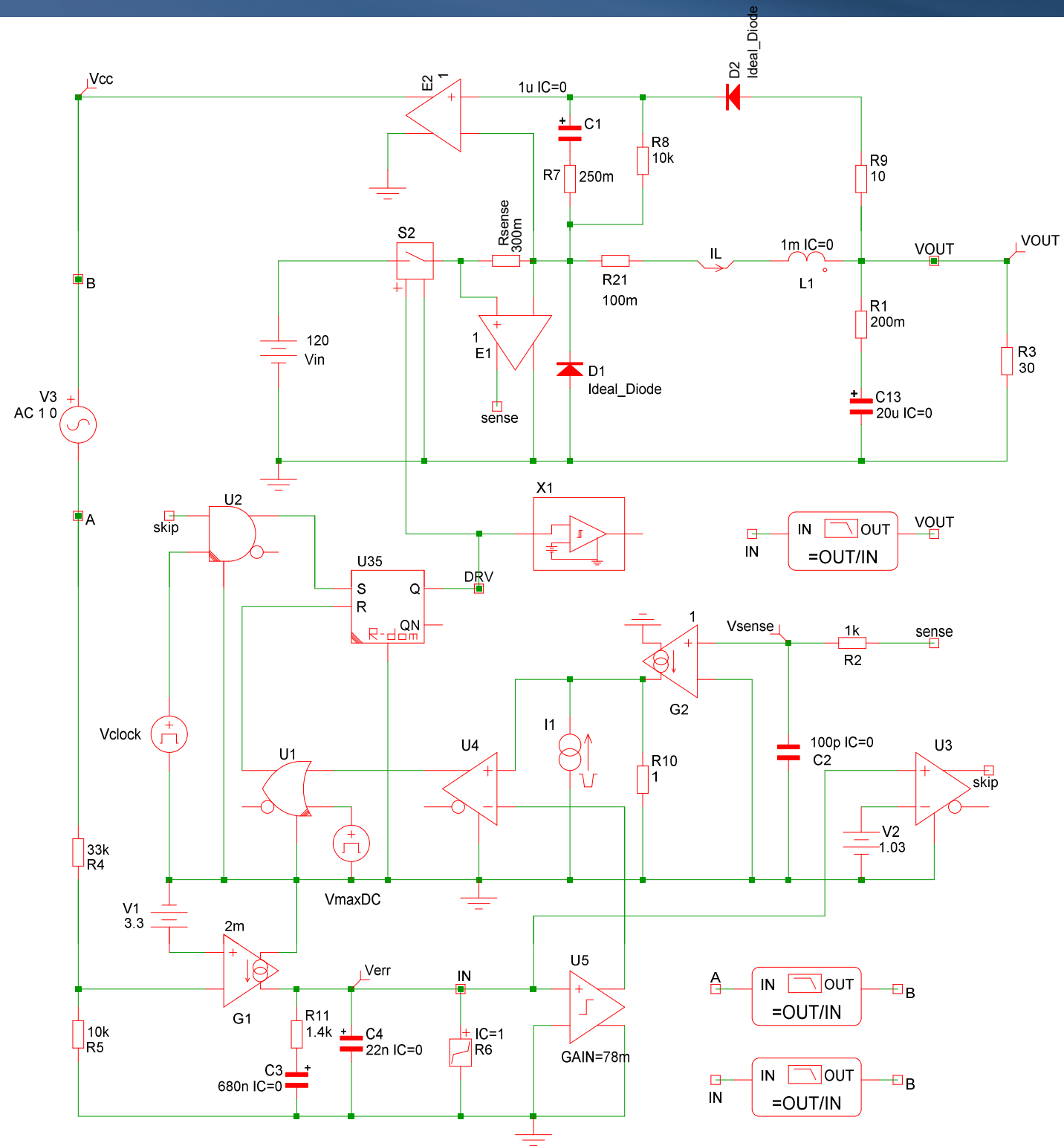

# Check Plant and Loop Gains

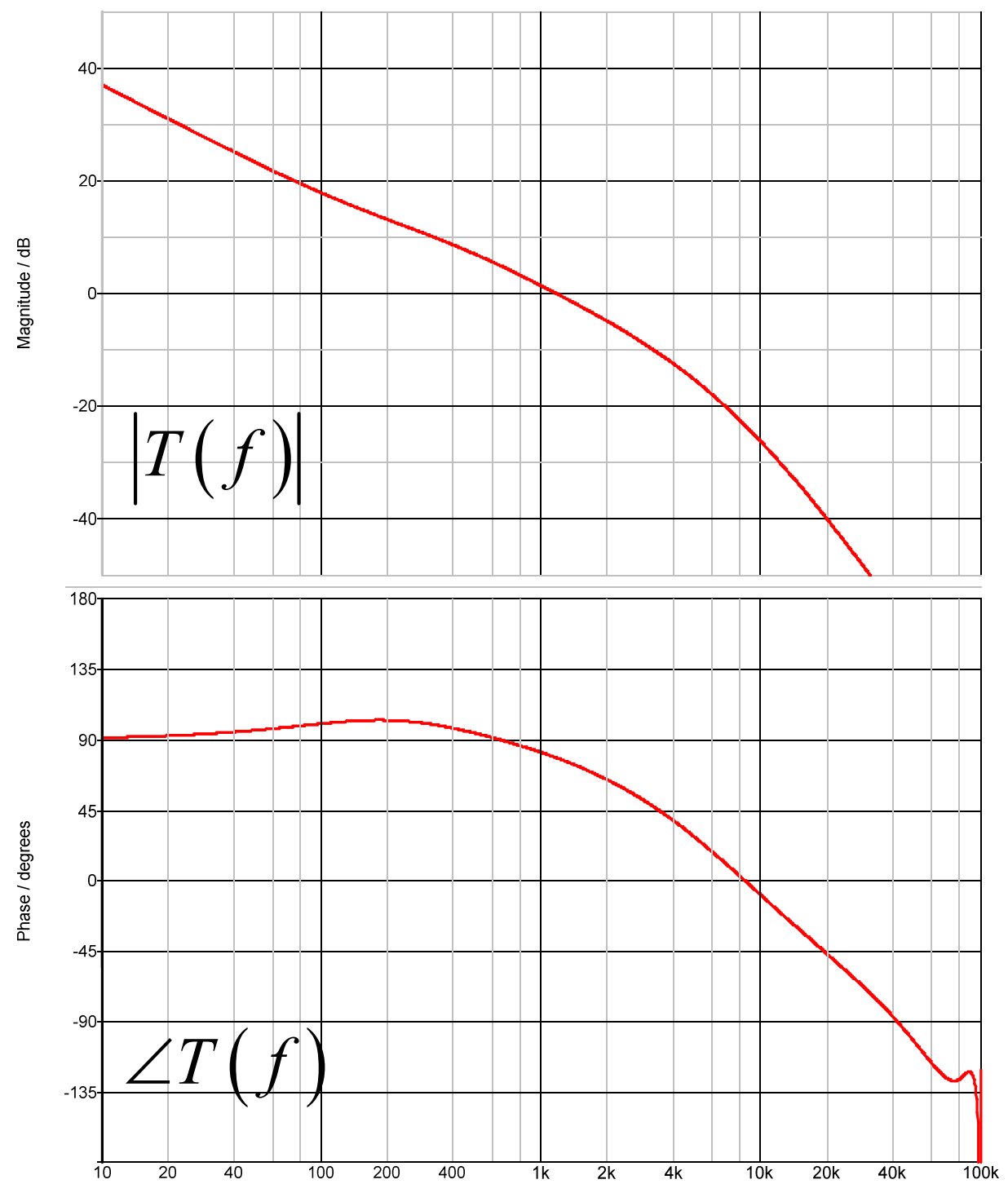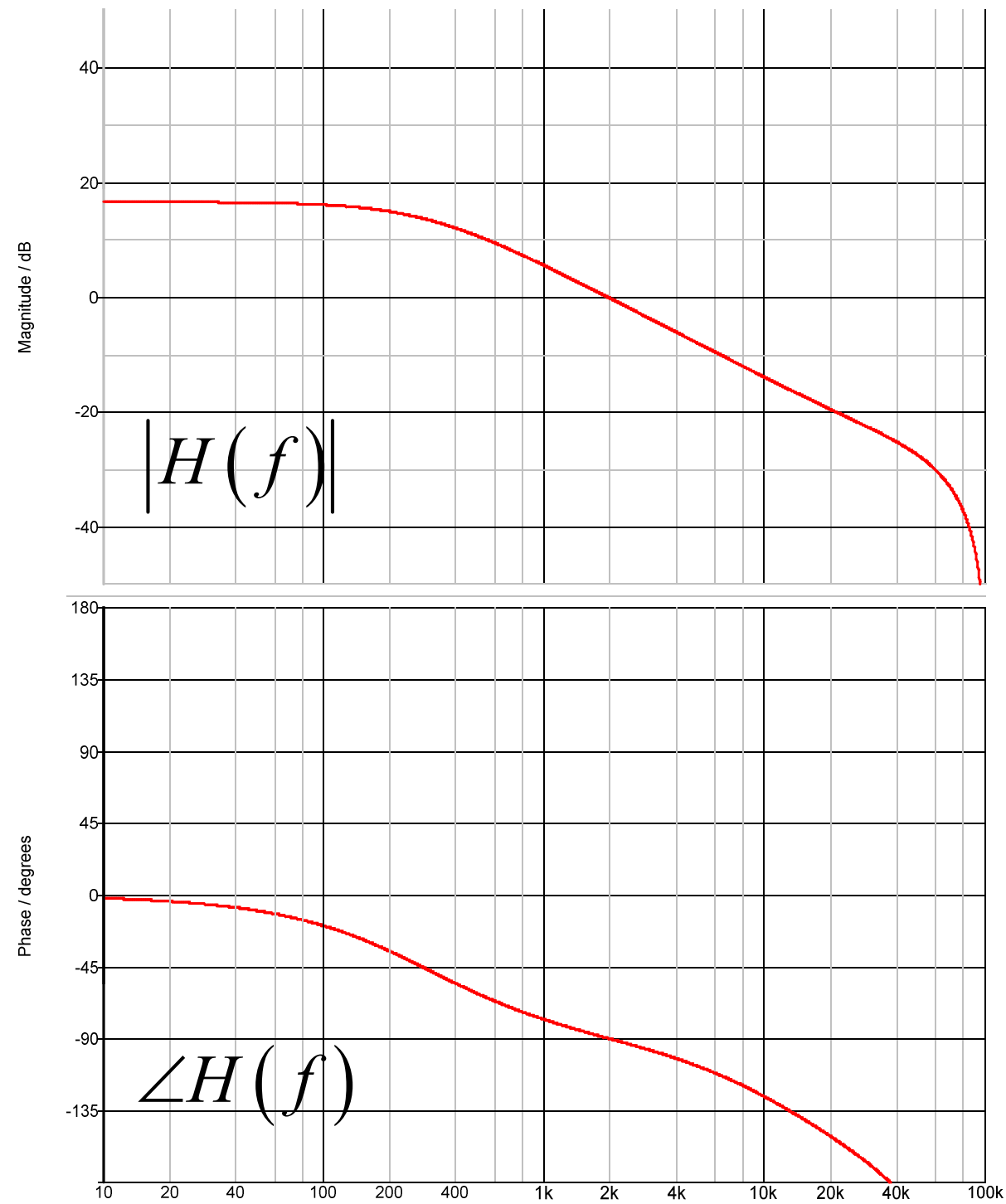

# Conclusion

❑ The compensation of the NCP1060 in a CCM-operated buck converter is done via a few steps

1. Determine the control-to-output transfer function (with Mathcad<sup>®</sup> or SIMPLIS<sup>®</sup>)
2. Extract the magnitude and phase at the selected crossover frequency
3. Build a type-2 compensator with the built-in OTA
4. Check the complete loop gain  $T(s)$  at different operating conditions
5. Sweep all parasitics (ESRs, capacitor etc.) and check there is always a sufficiently-high phase margin

