



安森美半导体
ON Semiconductor[®]


补偿PFC段

Compensating PFC Stages

议程 Agenda

- 简介 Introduction
- 导出小信号模型 Deriving a small-signal model
 - 一般方法 General method
 - 实际案例：NCP1605驱动PFC段 Practical example: NCP1605-driven PFC stages
- 补偿环路 Compensating the loop
 - 第2类补偿 Type-2 compensation
 - 交流线路及功率电平影响 Influence of the line and power level
 - 计算补偿 Computing the compensation
 - 实际案例 Practical example
- 总结 Summary

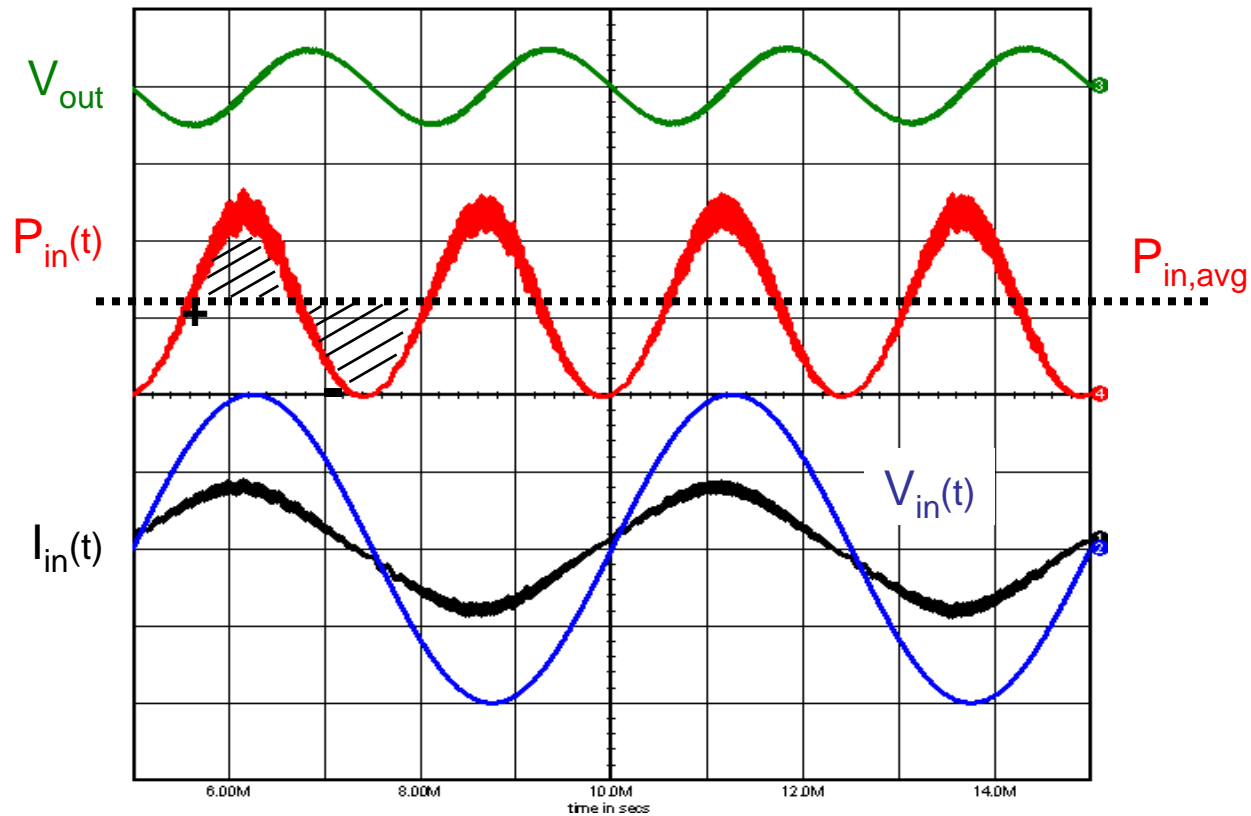输出电压低频纹波 Output Voltage Low Frequency Ripple



- ❑ 负载功率需求仅匹配平均值 The load power demand is matched in average only
- ❑ PFC功能本质上会有**低频纹波** A **low frequency ripple** is inherent to the PFC function

PFC段是低频工作系统

PFC Stages are Slow Systems...

- ❑ 必须滤除输出纹波，防止电流失真
The output ripple must be filtered to avoid current distortion.
- ❑ 在实际工作,环路频率会选择在20 Hz范围,这是非常低
In practice, the loop frequency is selected in the range of 20 Hz, which is very low.
- ❑ 即使带宽低,环路也必须作补偿!
Even if the bandwidth is low, the loop must be compensated!

议程 Agenda

□ 简介 Introduction

□ 导出小信号模型 Deriving a small-signal model

- 一般方法 General method
- 实际案例：NCP1605驱动PFC段 Practical example: NCP1605-driven PFC stages


□ 补偿环路 Compensating the loop

- 第2类补偿 Type-2 compensation
- 交流线路及功率电平影响 Influence of the line and power level
- 计算补偿 Computing the compensation
- 实际案例 Practical example

□ 总结 Summary

PFC段简化表现 A Simple Representation

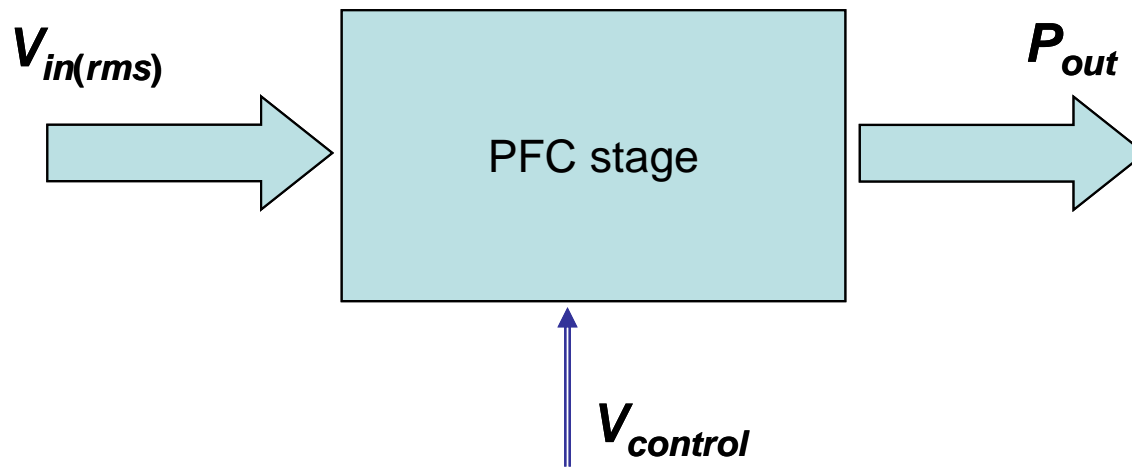- 将PFC段视作一个系统，在输入均方根(rms)电压及控制信号
的条件下提供功率 We will consider the PFC stage as a system delivering a power under an input rms
voltage and a control signal




- 忽略具体的功率处理问题 Details of the power processing are ignored:
 - 工作模式(CrM, CCM, 电压或电流模式...) Operation mode (CrM, CCM, Voltage or Current mode...)
 - 能效100%，仅考虑正弦信号的平均功率部分 100% efficiency, only the average power contribution
of the sinusoidal signals is considered

PFC段简化大信号模型 A Simple Large Signal Model

- 将PFC段表现为电流源， 传送能量到大电容及负载

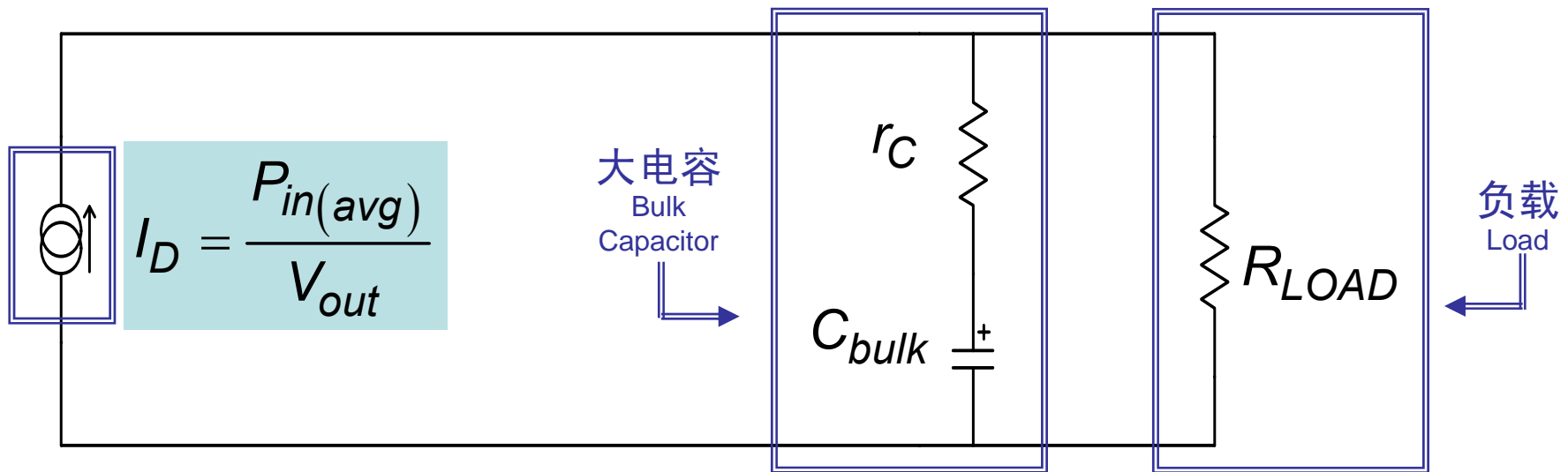Let's represent the PFC stage as a current source delivering the power to the bulk capacitor and the load



- $P_{in(avg)}$ 取决于 $V_{control}$ (永远)、 $V_{in(rms)}$ (缺少前馈时) 及 V_{out} (有时)

$P_{in(avg)}$ depends on $V_{control}$ (always), on $V_{in(rms)}$ (in the absence of feedforward) and sometimes on V_{out}

- 3种可能的干扰源: $V_{control}$ 、 V_{out} 及 $V_{in(rms)}$

3 possible sources of perturbations: $V_{control}$, V_{out} and $V_{in(rms)}$


NCP1605

□ 频率钳位临界导电模式(FCCrM) Frequency Clamped Critical Conduction Mode (FCCrM)

□ 主PFC关键特性 Key features for a master PFC:

- 高压电流源，待机模式软跳周期 High voltage current source, Soft-Skip™ during standby mode
- 提供“pfcOK”信号，动态响应增强器 “pfcOK” signal, dynamic response enhancer
- 多种保护特性，便于设计坚固的PFC段 Bunch of protections for rugged PFC stages

□ 市场：大功率交流适配器、液晶电视 Markets: high power ac adapters, LCD TVs

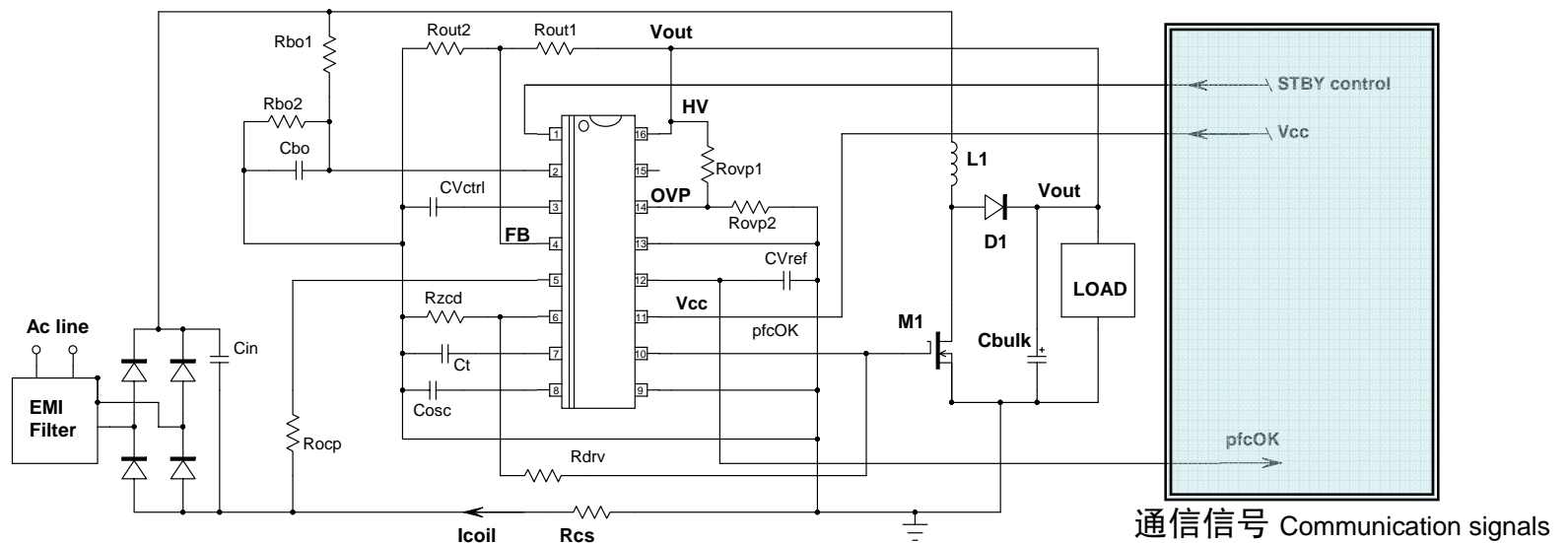

NCP1605-跟随升压 NCP1605 – Follower Boost

□ 电压模式工作：电路藉调制MOSFET导通时间来调节功率电平

Voltage mode operation: the circuit adjusts the power level by modulating the MOSFET conduction time

□ 时序电容的充电电流与反馈方波、并因此与 $(V_{out})^2$ 成正比 The charge current of the timing capacitor is proportional to the FB square and hence to $(V_{out})^2$:

$$I_{charge} = I_t \cdot \left(\frac{V_{out}}{V_{out,nom}} \right)^2$$

其中 where :

- $V_{out,nom}$ 是输出稳压电压 $v_{out,nom}$ is the V_{out} regulation voltage
- I_t 是370 μ A电流源 I_t is a 370- μ A current source


□ 导通时间与 $(V_{out})^2$ 成反比，支持跟随升压功能 The on-time is inversely proportional to $(V_{out})^2$ allowing the Follower boost function:

$$t_{on} = \frac{C_t \cdot V_{ton}}{I_t} \cdot \left(\frac{V_{out,nom}}{V_{out}} \right)^2$$

NCP1605-功率表达式 NCP1605 - Power Expression

- 控制信号是 V_F 先向下偏置、然后除以3所得到的 V_{REGUL} ，用于脉宽调制(PWM)部分

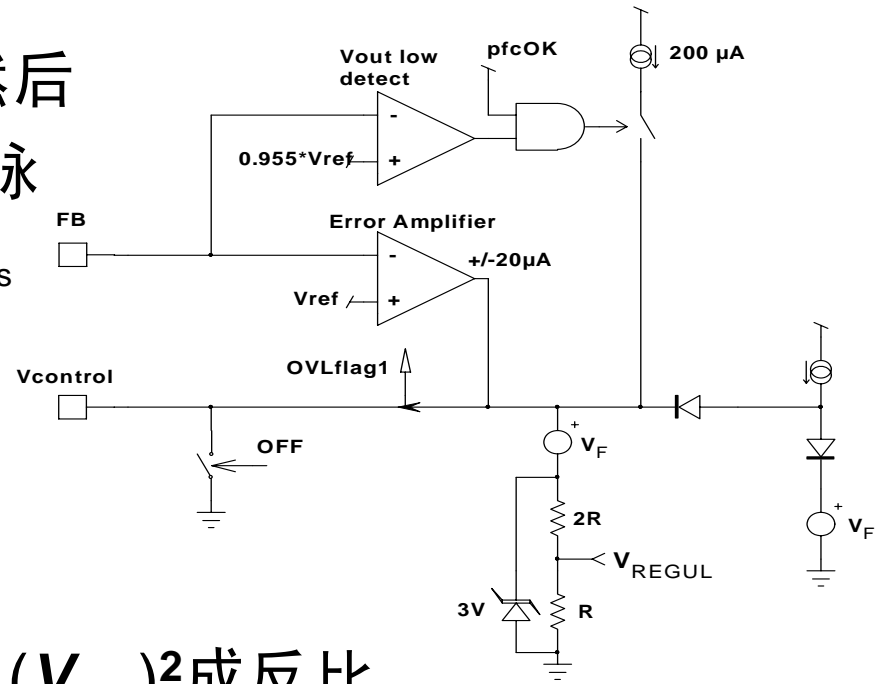The control signal is V_F offset down and divided by 3 to form V_{REGUL} used in the PWM section



- 故由于跟随升压功能，功率与 $(V_{out})^2$ 成反比

Hence due to the follower boost function, the power is inversely dependent on $(V_{out})^2$:


$$P_{in(avg)} = \frac{C_t \cdot V_{in(rms)}^2}{2 \cdot L \cdot I_t} \cdot \left(\frac{V_{out,nom}}{V_{out}} \right)^2 \cdot \frac{(V_{control} - V_F)}{3}$$

NCP1605-大信号模型

NCP1605 - Large Signal Model

□ 将PFC段表现为电流源， 传送能量到大电容及负载

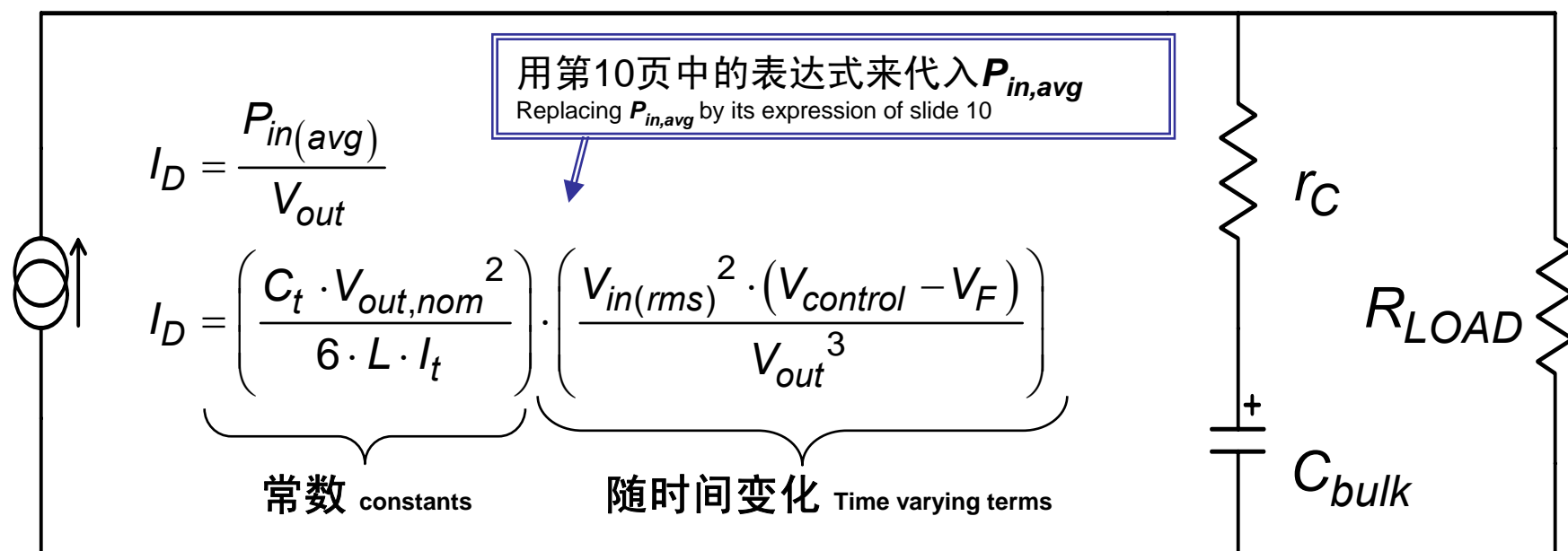Let's represent the PFC stage as a current source delivering the power to the bulk capacitor and the load:



□ 3种干扰源: $V_{CONTROL}$ 、 V_{out} 及 $V_{in(rms)}$

3 sources of perturbations: $V_{CONTROL}$, V_{out} and $V_{in(rms)}$.

小信号模型 Small Signal Model

- 大信号模型是非线性，因为 I_D 由 $V_{control}$ 、 $V_{in,rms}$ 及 V_{out} 的乘法及除法运算而构成

A large signal model is nonlinear because I_D is formed of the multiplication and division of $V_{control}$, $V_{in,rms}$ and V_{out}

- 这个模型需要线性化，评估每个变量的交流成分

This model needs to be linearized to assess the ac contribution of each variable

- 这模型在静态工作点(直流点)附近扰动及线性化

The model is perturbed and linearized around a quiescent operating point (dc point)

考虑直流值附近的变量


Considering Variations Around the Dc Value...

❑ 忽略交流线的微扰(假定为常量) Let's omit the perturbations of the line magnitude (assumed constant)

❑ 考虑 V_{out} 及 $V_{control}$ 直流值附近的小变量 Let's consider small variations around the dc values for V_{out} and $V_{control}$:


❑ 然后我们获得 We then obtain:
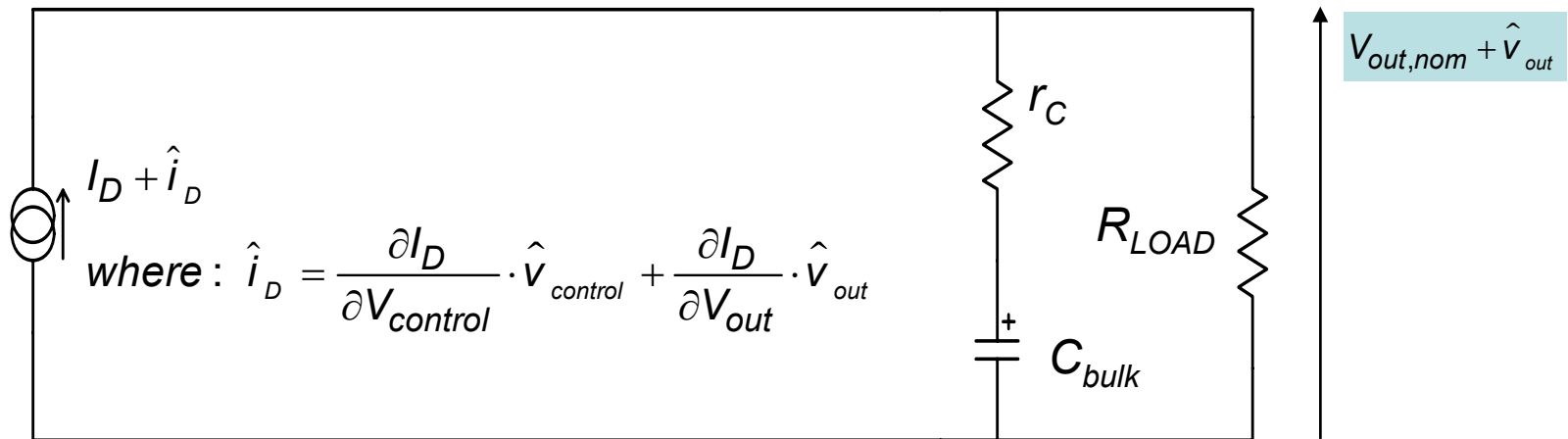
$$\hat{i}_D = \frac{\partial I_D}{\partial V_{control}} \cdot \hat{v}_{CONTROL} + \frac{\partial I_D}{\partial V_{out}} \cdot \hat{v}_{out}$$



导出小信号模型 Deriving a Small Signal Model...

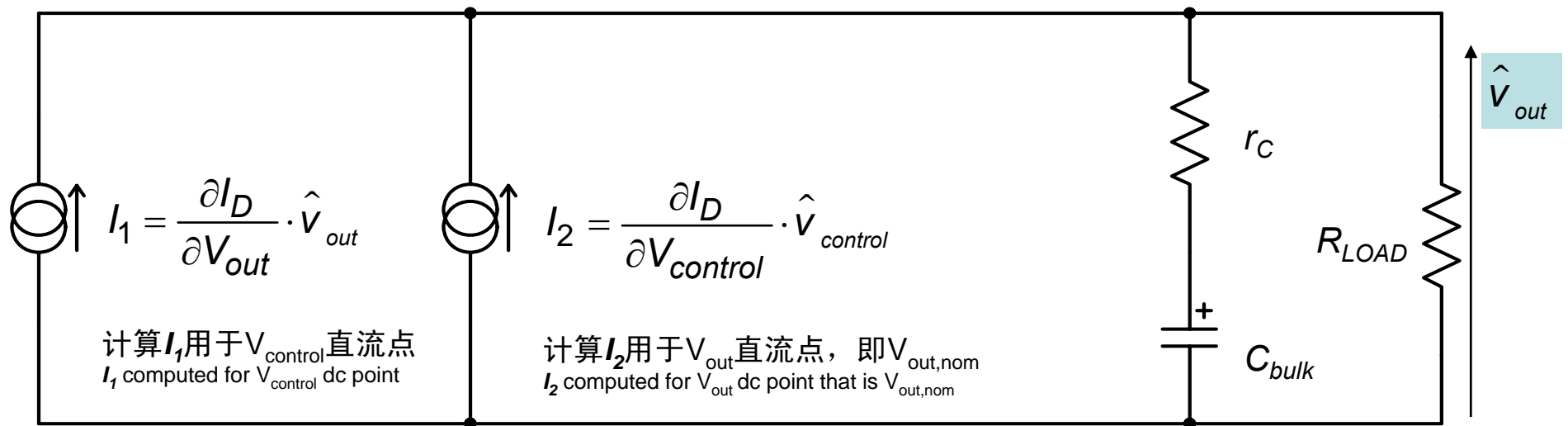- 直流部分可以去除 The dc portion can be eliminated
- 在直流点计算偏导数，即 The partial derivatives are to be computed at the dc point that is for:
 - $V_{control}$ 是控制信号直流值，用于所考虑的工作点 that is the control signal dc value for the considered working point
 - $V_{out,nom}$ 是额定(直流)输出电压 that is the nominal (dc) output voltage
- 用等式替代导数，我们就获得 Replacing the derivations by their expression, we obtain:



输出电压干扰成分 Contribution of the V_{out} Perturbations

□ 取决于控制器原理 Depending on the controller scheme

$$I_D = \frac{P_{in,avg}}{V_{out}} = \frac{f(V_{in(rms)}, V_{control})}{(V_{out})^{n+1}} \quad \text{where } n = 0, 1 \text{ or } 2$$

- $n=0$ 对应NCP1607 for NCP1607
- $n=1$ 对应NCP1654(预测型CCM PFC, 当 $P_{in,avg} \propto \frac{V_{control} \cdot V_{in,rms}}{V_{out}}$)
 $n=1$ for NCP1654 (predictive CCM PFC for which)
- $n=2$ 对应NCP1605(跟随升压-见第10页)
 $n=2$ for NCP1605 (follower boost – see slide 10)


□ 在直流点 At the dc point $V_{out} = V_{out,nom}$ and $\frac{P_{in(avg)}}{(V_{out,nom})^2} = \frac{1}{R_{LOAD}}$

□ 最后得到 Finally:

$$I_1 = \frac{\partial I_D}{\partial V_{out}} \cdot \hat{V}_{out} = - \frac{(n+1) \cdot f(V_{in(rms)}, V_{control})}{(V_{out})^{n+2}} \Bigg|_{V_{out}=V_{out,nom}} \cdot \hat{V}_{out} = - \frac{(n+1) \cdot P_{in(avg)}}{(V_{out,nom})^2} \cdot \hat{V}_{out} = - \frac{(n+1)}{R_{LOAD}} \cdot \hat{V}_{out}$$

简化为2个电阻型负载 2 Resistors...

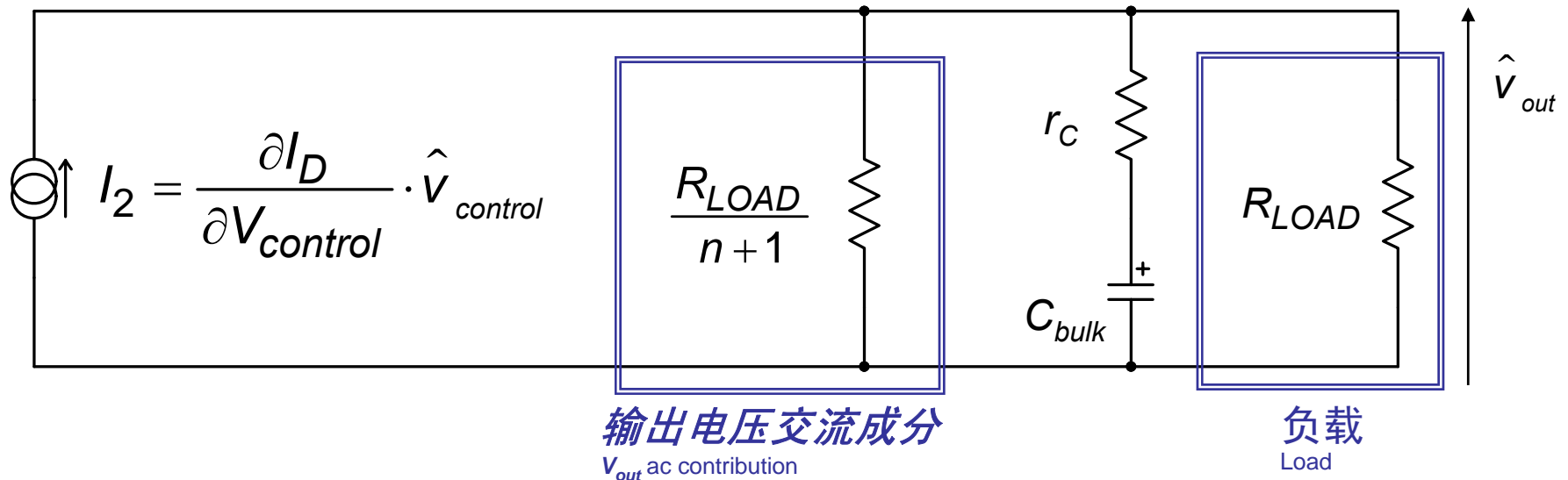因此，能简化小信号模型，如下图所示 Hence, the small signal model can be simplified as follows:




注意： Noting that: $\frac{R_{LOAD}}{n+1} \square R_{LOAD} = \frac{R_{LOAD}}{n+2}$

这模型还能进一步简化 the model can be further simplified

最终获得 Finally...

□ 小信号模型 The small signal model is:
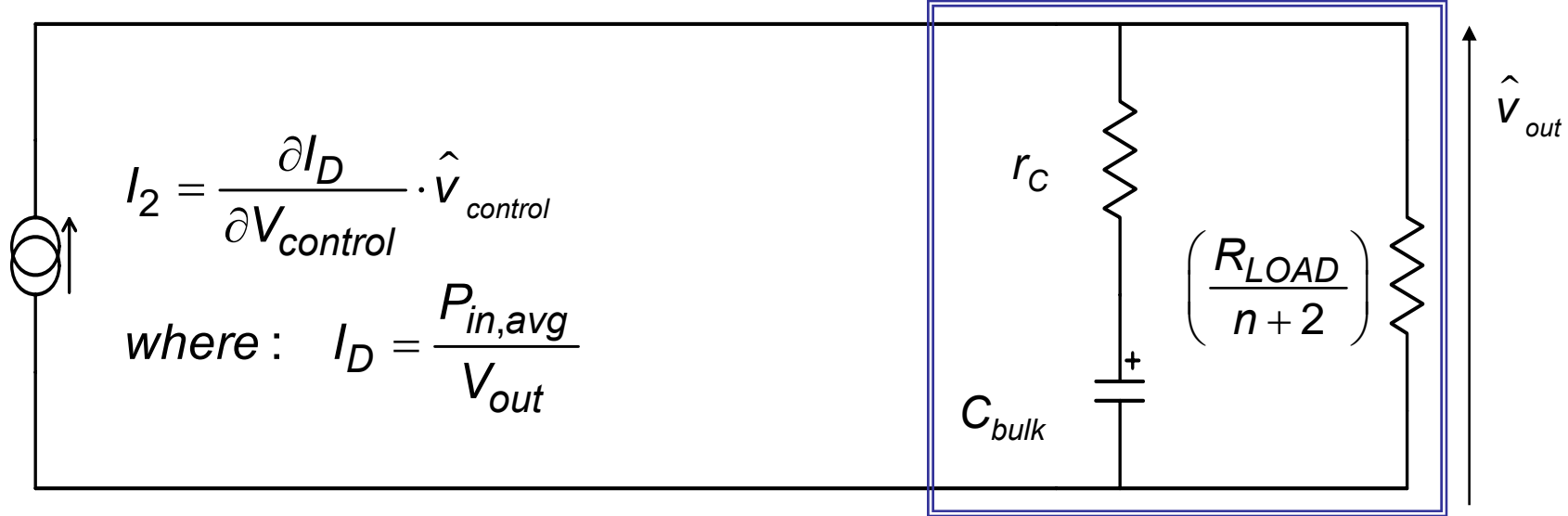
$$Z(s) = \frac{R_{LOAD}}{n+2} \cdot \frac{1+s \cdot r_C \cdot C_{bulk}}{1+s \left(\frac{R_{LOAD} \cdot C_{bulk}}{n+2} \right)}$$



□ 传递函数 The transfer function is:

$$\frac{\hat{V}_{out}}{\hat{V}_{control}} = \frac{R_{LOAD}}{n+2} \cdot \left(\frac{\partial I_D}{\partial V_{control}} \right) \cdot \frac{1+s \cdot r_C \cdot C_{bulk}}{1+s \left(\frac{R_{LOAD} \cdot C_{bulk}}{n+2} \right)}$$



NCP1605示例 NCP1605 Example

□ 大信号模型表示为 The large signal model instructed that:

$$I_D = \frac{P_{in(avg)}}{V_{out}} = \left(\frac{C_t \cdot V_{out,nom}^2}{6 \cdot L \cdot I_t} \right) \cdot \left(\frac{V_{in(rms)}^2 \cdot (V_{control} - V_F)}{V_{out}^3} \right)$$

□ 因此 Hence:

$$n = 2$$


$$\frac{\partial I_D}{\partial V_{control}} = \frac{C_t \cdot (V_{in(rms)})^2}{6 \cdot L \cdot I_t \cdot V_{out,nom}}$$

$(V_{out})^{n+1}$ term

NCP1605-小信号模型

NCP1605 - Small Signal Model

□ 最终获得 Finally:

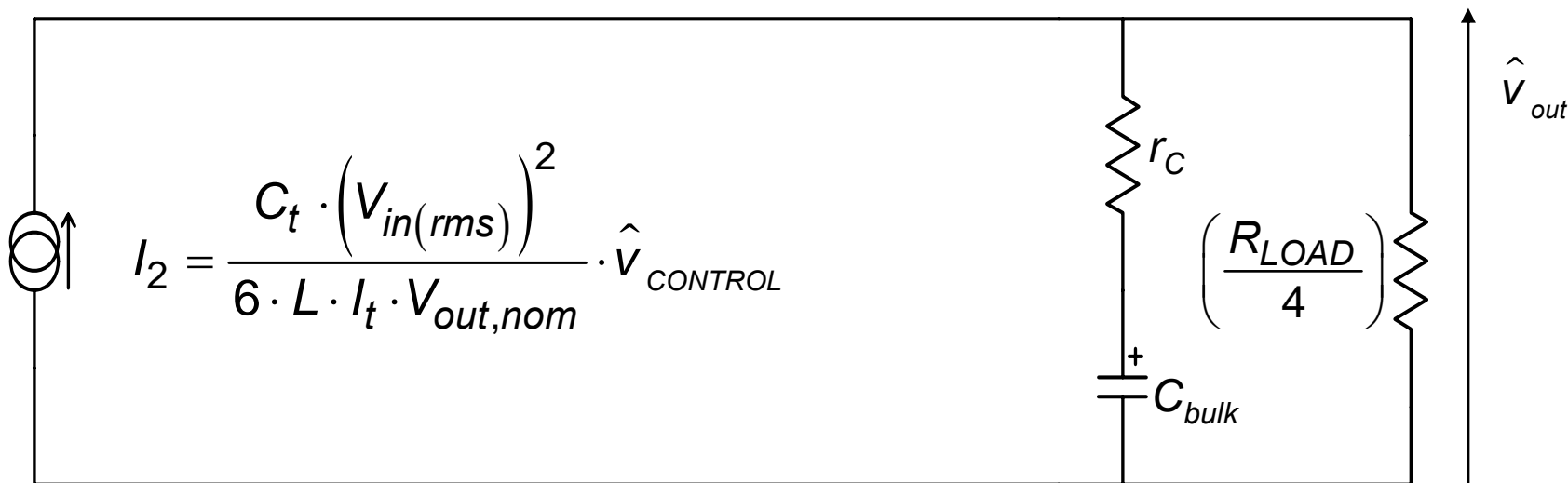


□ 传递函数是 The transfer function is:

$$\frac{\hat{V}_{out}}{\hat{V}_{CONTROL}} = \frac{R_{LOAD} \cdot C_t \cdot (V_{in(rms)})^2}{24 \cdot L \cdot I_t \cdot V_{out,nom}} \cdot \frac{1 + s \cdot r_C \cdot C_{bulk}}{1 + s \cdot \left(\frac{R_{LOAD} \cdot C_{bulk}}{4}\right)}$$

电源段特性描述-波特图

Power stage characteristic – Bode Plots

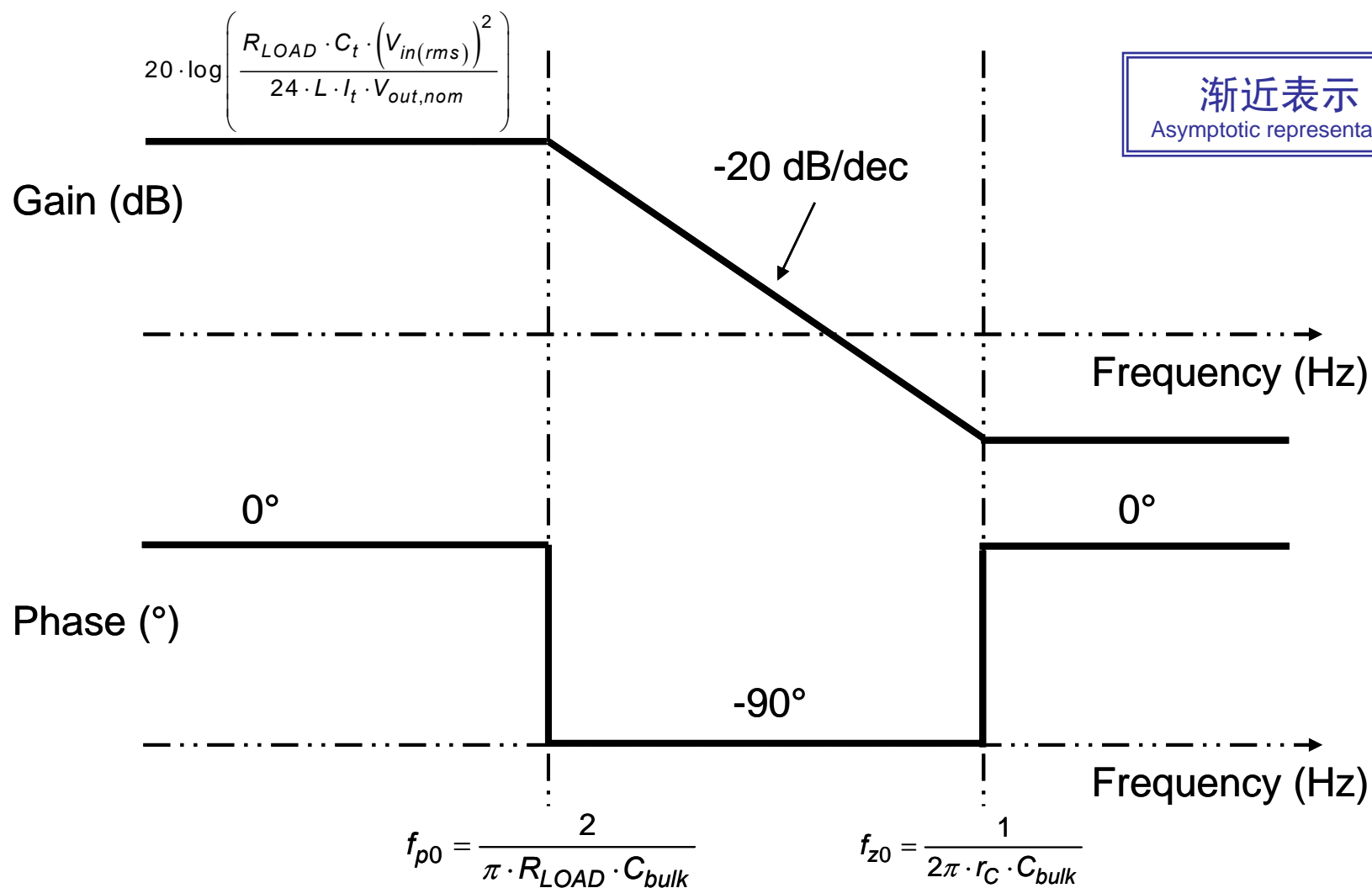

议程 Agenda

□ 简介 Introduction

□ 导出小信号模型 Deriving a small-signal model

- 一般方法 General method
- 实际案例：NCP1605驱动PFC段 Practical example: NCP1605-driven PFC stages

□ 补偿环路 Compensating the loop

- 第2类补偿 Type-2 compensation
- 交流线路及功率电平影响 Influence of the line and power level
- 计算补偿 Computing the compensation
- 实际案例 Practical example

□ 总结 Summary


补偿相位提升 Compensation Phase Boost

- ❑ 由大电容等效串联电阻(ESR)导致的零点太高，难以提供一些相位余量。忽略不计。 The zero brought by the bulk capacitor ESR is too high to bring some phase margin. It is ignored.
- ❑ PFC环路开路本质上会导致 -360° 的相移 The PFC open loop inherently causes a -360° phase shift:
 - 电源段极点 Power stage pole $\rightarrow -90^\circ$
 - 倒置误差放大器 Error amplifier inversion $\rightarrow -180^\circ$
 - 补偿原极点 Compensation origin pole $\rightarrow -90^\circ$
- ❑ 补偿必须提供一些相位提升 The compensation must then provide some phase boost
- ❑ 推荐第2类补偿 A type-2 compensation is recommended

第2类补偿 Type-2 Compensation

□NCP1605集成了传导误差变压器(OTA)

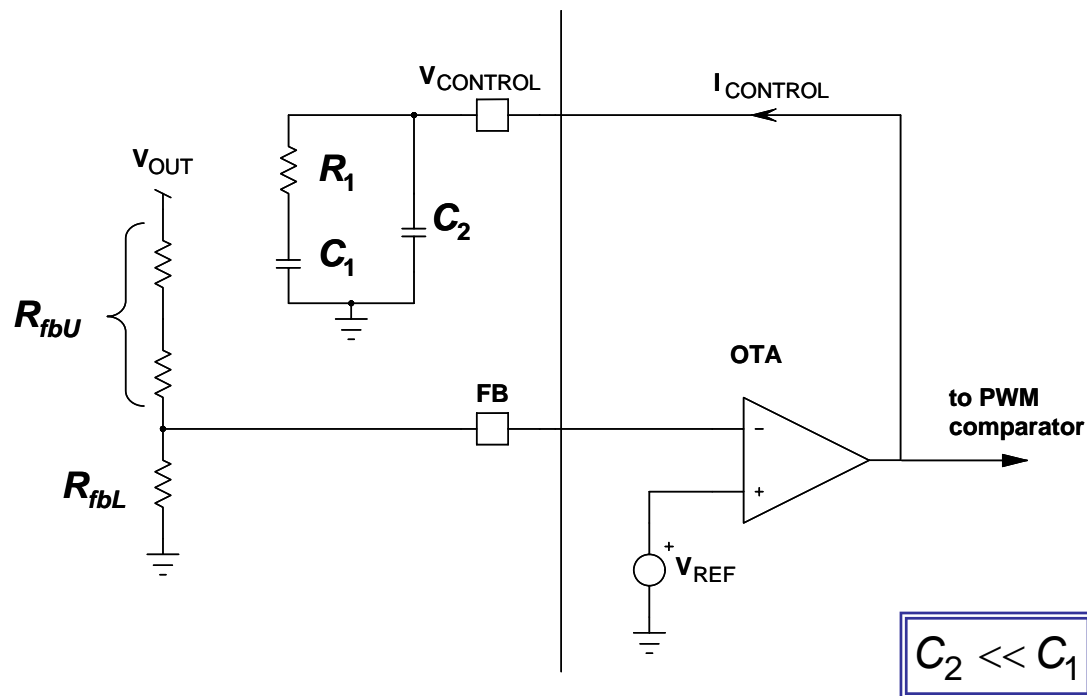The NCP1605 embeds a transconductance error amplifier (OTA)



$$f_{z1} = \frac{1}{2\pi \cdot R_1 \cdot C_1}$$

$$f_{p2} = \frac{1}{2\pi \cdot R_1 \cdot C_2}$$

$$f_{p1} = \frac{1}{2\pi \cdot R_0 \cdot C_1}$$

pole at the origin

$$R_0 = \frac{V_{out,nom}}{V_{ref} \cdot G_{EA}}$$

– R_{fbU} 阻抗对补偿没有直接影响


No direct influence of the R_{fbU} impedance on the compensation

–仅反馈比例因数有影响

Only the feedback scale factor interferes

- V_{ref} is the reference voltage (generally 2.5 V in ON semi devices)
- G_{EA} is the OTA (200- μ S transconductance gain for NCP1605, NCP1654 and NCP1631)

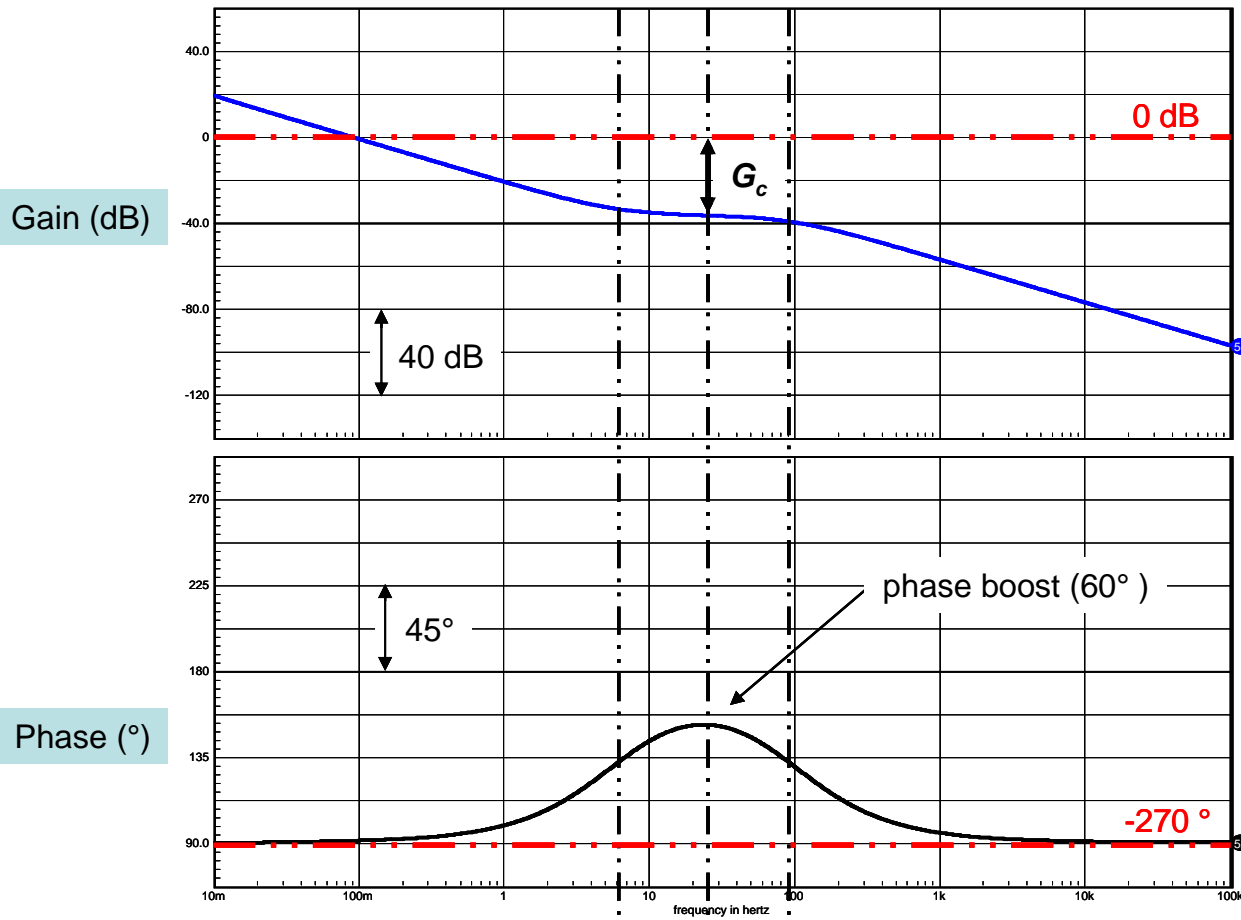第2类补偿特性示例 Type-2 Characteristic - Example



f_{z1} : compensation zero (6 Hz)

f_{p2} : high frequency pole (90 Hz)

$$\sqrt{f_{z1} \cdot f_{p2}}$$

□ f_{p2} 和 f_{z1} 确定相位提升幅度及位置(频率) f_{p2} and f_{z1} set the phase boost magnitude and location (frequency)

□ 相位提升峰值为: The phase boost peaks at: $(f_{phB} = \sqrt{f_{z1} \cdot f_{p2}})$ 即27 Hz that is 27 Hz


□ 相位提升为 The phase boost is: $\tan^{-1}\left(\frac{f_{phB}}{f_z}\right) - \tan^{-1}\left(\frac{f_{phB}}{f_p}\right)$

□ 原极点 f_{p1} 以相位提升频率调节增益 G_c The origin pole f_{p1} adjusts the gain G_c at the phase boost frequency



在交越频率相位提升

Phase Boost at the Crossover Frequency

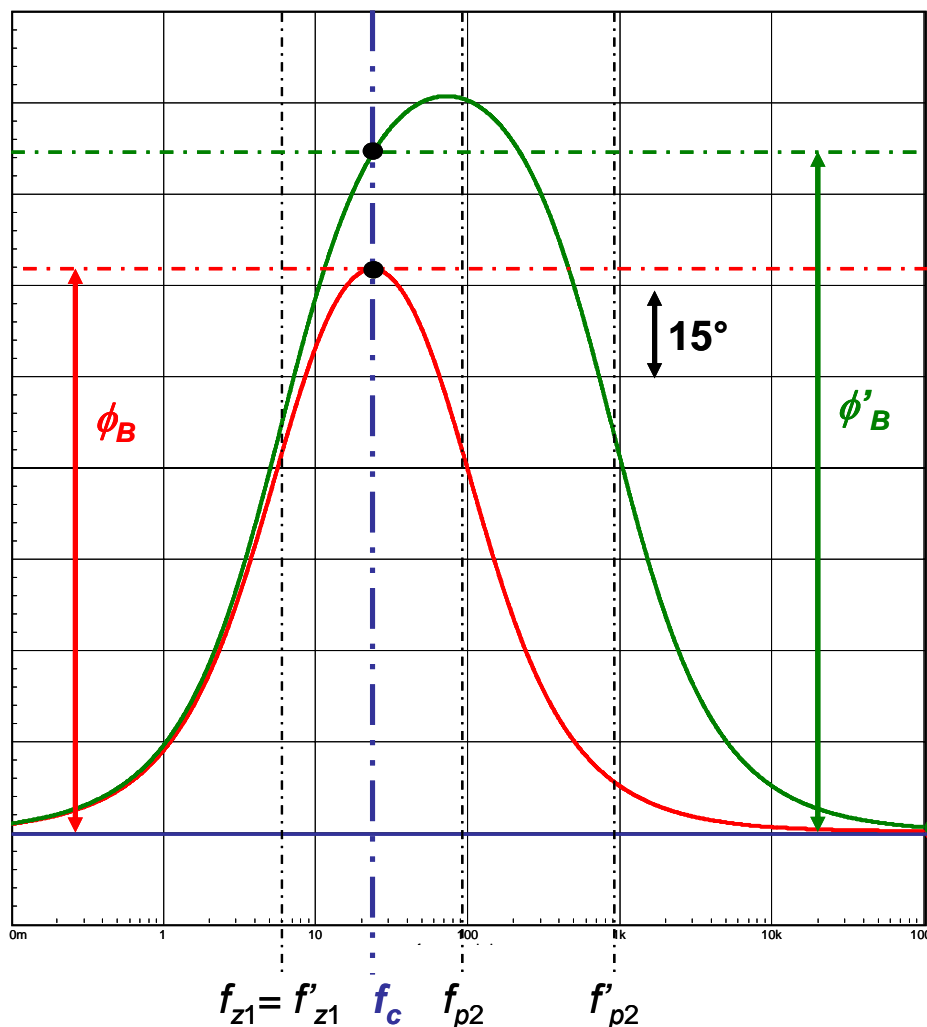

$$\phi_B = \tan^{-1} \left(\frac{f_c}{f_{z1}} \right) - \tan^{-1} \left(\frac{f_c}{f_{p2}} \right)$$

□ f_{z1} 越低和/或 f_{p2} 越高, 相位提升就越高(最大值为 90°)

The lower f_{z1} and/or the higher f_{p2} , the higher the phase boost (max. value: 90°)

□ 假定PFC电源段极点远低于交越频率(f_c), 相位提升就等于相位余量($\phi_m = \phi_B$)


Assuming the PFC power stage pole is well below the crossover frequency (f_c), the phase boost equates the phase margin ($\phi_m = \phi_B$)

-270°

□ 将相位增益目标定在 45° 与 75° 之间

Target a phase boost between 45° and 75°

增益考虑因素 Gain Considerations

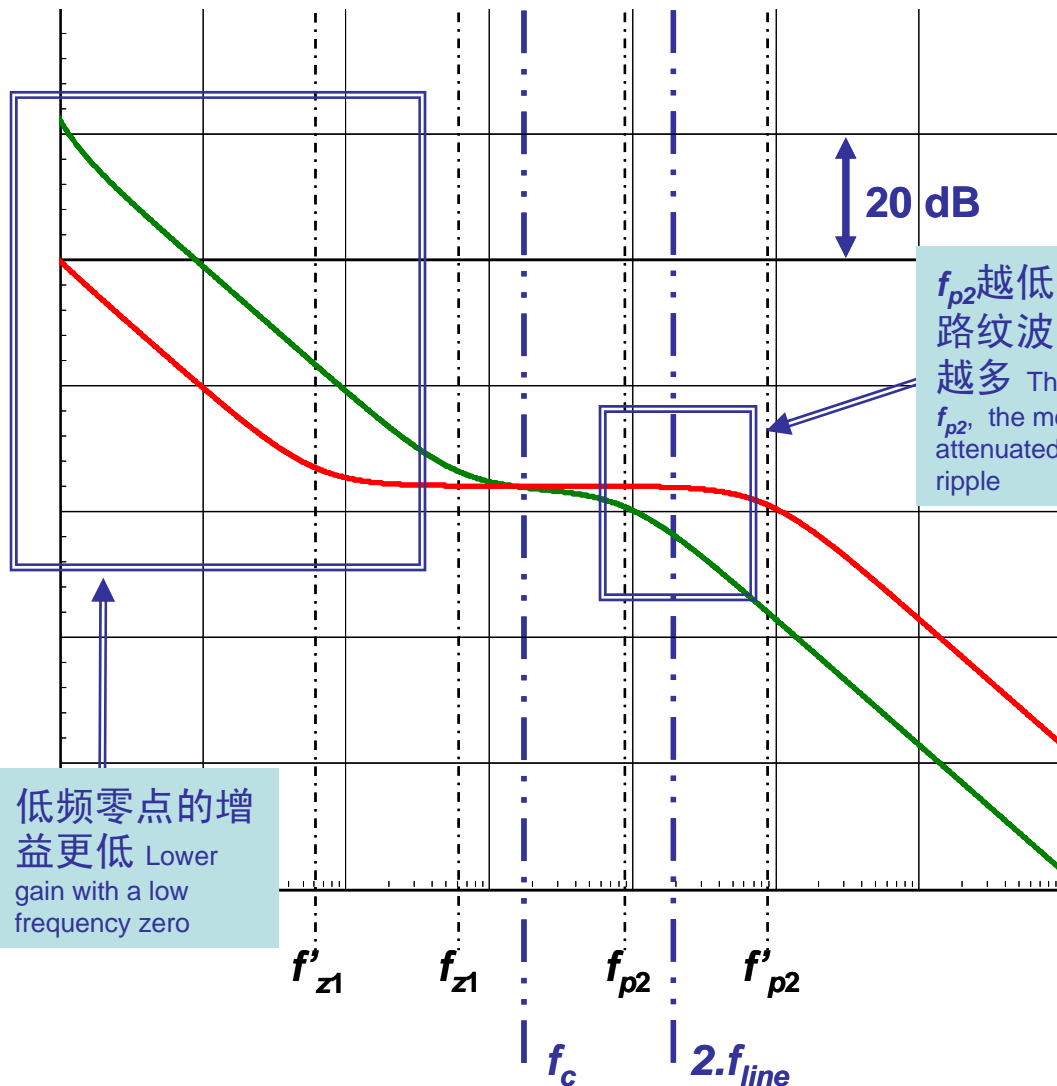

- ❑ 红色迹线中，零点与极点频率之间的距离增加 In the red trace, the distance between the zero and the pole frequencies is increased
- ❑ 两种特性迹线在交越频率处产生的衰减相同 Both characteristics generate the same attenuation at the crossover frequency
- ❑ f_{z1} 频率越低，低频区域中的增益就越低 The lower the f_{z1} frequency, the lower the gain in the low frequency region
- ❑ f_{p2} 越高， $(2 \cdot f_{line})$ 纹波抑制就越低 The higher f_{p2} , the lower the $(2 \cdot f_{line})$ ripple rejection

第2类补偿器小结

Type-2 Compensator - Summary

□ 零点不应置于太低的频率(不损及低频增益)

The zero should not be placed at a too low frequency (not to penalize the low-frequency gain)

□ 高频极点必须置于低至足以使交流线路纹波衰减的频率

The high frequency pole must be placed at a frequency low enough to attenuate the line ripple

□ 相位提升(及相位余量)取决于零点及高频极点位置

The phase boost (and phase margin) depends on the zero and high-frequency pole locations

□ 原极点设为在目标交越频率迫使开环增益为零

The origin pole is set to force the open loop gain to zero at the targeted crossover frequency

议程 Agenda

□ 简介 Introduction

□ 导出小信号模型 Deriving a small-signal model

- 一般方法 General method
- 实际案例：NCP1605驱动的PFC段 Practical example: NCP1605-driven PFC stages

□ 补偿环路 Compensating the loop

- 第2类补偿 Type-2 compensation
- 交流线路及功率电平影响 Influence of the line and power level
- 计算补偿 Computing the compensation
- 实际案例 Practical example

□ 总结 Summary

是否要全范围补偿?

Compensating for the Full Range?...

- 静态增益取决于负载，而如果没有前馈，取决于交流线路幅度
The static gain depends on the load and if there is no feedforward, on the line magnitude

$$G_{static(dB)} = 20 \cdot \log \left(\frac{R_{LOAD}}{n+2} \cdot \left(\frac{\partial I_D}{\partial V_{control}} \right) \right) = 20 \cdot \log \left(\frac{R_{LOAD} \cdot C_t \cdot (V_{in(rms)})^2}{24 \cdot L \cdot I_t \cdot V_{out,nom}} \right) \quad (\text{NCP1605})$$

- 电源段极点以负载的函数而变化 The power stage pole varies as a function of the load:


$$f_{p0} = \frac{n+2}{2\pi \cdot R_{LOAD} \cdot C_{bulk}} = \frac{2}{\pi \cdot R_{LOAD} \cdot C_{bulk}} \quad (\text{NCP1605})$$

- 在关闭环路时最坏情况如何? What is the worst case when closing the loop?

负载对开环图的影响

Load Influence on the Open Loop Plots

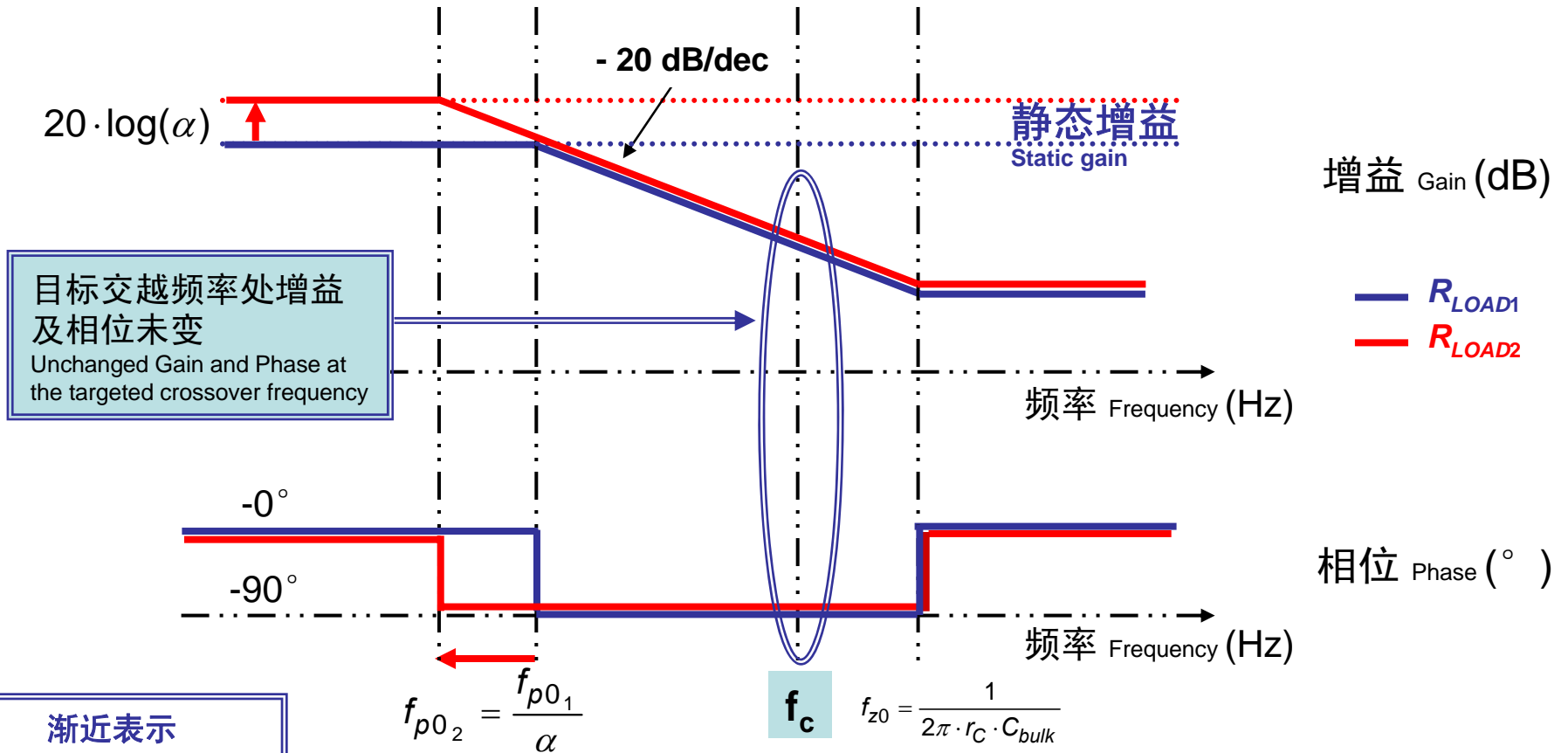□ 增加负载电阻 Let's increase R_{LOAD} ($R_{LOAD2} = \alpha \cdot R_{LOAD1}$ with $\alpha > 1$)




f_c 及 Φ_m 不受影响! f_c and ϕ_m are not affected!

交流线路对开环图的影响

Line Influence on the Open Loop Plots

□ 无前反馈(如NCP1607), 及 $V_{in(rms)2} = \beta \cdot V_{in(rms)1}$ with $\beta > 1$)

No feedforward (e.g. NCP1607) and

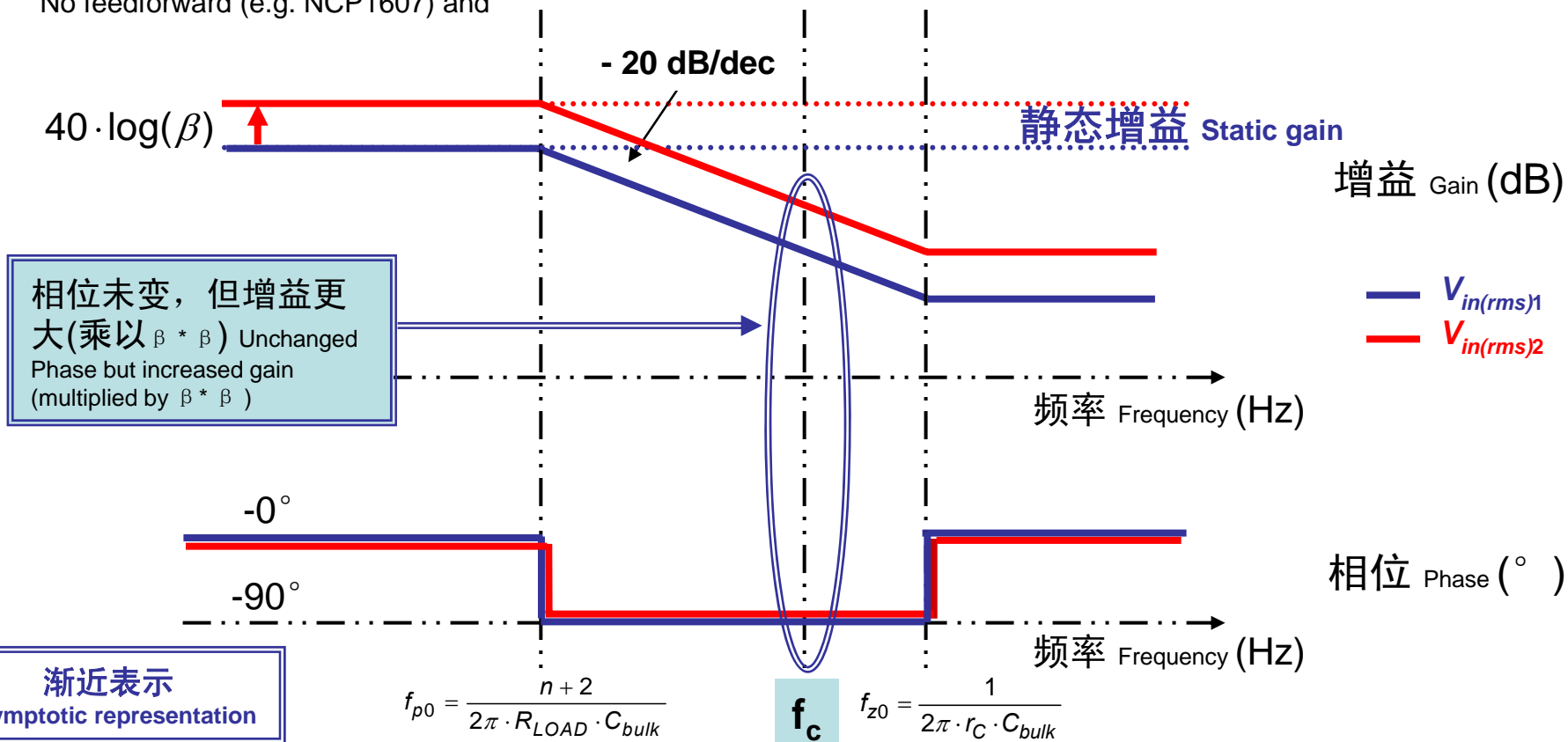

环路交越频率乘以 β^2 The loop crossover frequency is β^2 increased

负载及交流线路考虑因素

Load and Line Considerations

□ 满载时补偿 Compensate at full load

– 与较轻负载时交越频率相同 Same crossover frequency at lighter loads

– 优化设定了零点频率(不处于太低频率) The zero frequency is set optimally (not at a too low frequency)

□ 在高交流线路输入时补偿 Compensate at high line

– 交流高线路输入是最坏情况，因为没有前馈，静态增益正比于 $(V_{in(rms)})^2$

High line is the worst case as in the absence of feedforward, the static gain is proportional to

– 即可得到 This leads to:

$$(f_c)_{HL} = \left(\frac{(V_{in(rms)})_{HL}}{(V_{in(rms)})_{LL}} \right)^2 \cdot (f_c)_{LL}$$

其中，HL代表最高线路输入，LL代表最低线路输入 Where HL stands for Highest Line and LL for Lowest Line

– 在通用主电源应用中，高线路交越频率是低线路交越频率的9倍 In universal mains applications, the high-line crossover frequency is 9 times higher than the low-line one:

$$(f_c)_{HL} = \left(\frac{265}{90} \right)^2 \cdot (f_c)_{LL} \cong 9 \cdot (f_c)_{LL}$$

交越频率选择

Crossover Frequency Selection

□ 没有前馈的条件下, $(f_c)_{HL} \leq f_{line}$ 是个好选择 In the absence of feedforward, $(f_c)_{HL} \leq f_{line}$ is a good option

□ 有前馈时, 应该选择 $(f_c)_{HL} \leq \frac{f_{line}}{2}$, 获得更好的低频纹波衰减 With feedforward, $(f_c)_{HL} \leq \frac{f_{line}}{2}$ is rather selected for a better attenuation of the low frequency ripple

□ 确保在交流线路输入范围下, PFC升压极点在满载时保持低于交越频率!

Get sure that on the line range, the PFC boost pole remains lower than the crossover frequency at full load!

$$f_{p0} \leq (f_c)_{LL}$$

□ 否则, 就增大大电容 If not, increase C_{bulk}

议程 Agenda

□ 简介 Introduction

□ 导出小信号模型 Deriving a small-signal model

- 一般方法 General method
- 实际案例：NCP1605驱动PFC段 Practical example: NCP1605-driven PFC stages

□ 补偿环路 Compensating the loop

- 第2类补偿 Type-2 compensation
- 交流线路及功率电平影响 Influence of the line and power level
- 计算补偿 Computing the compensation
- 实际案例 Practical example

□ 总结 Summary

补偿技术

Compensation Techniques

□存在几种技术 Several techniques exist:

▪手动设置, “k因数”(Venable).....manual placement, “k factor” (Venable)...

+ 系统化 Systematic

- PFC升压增益将在 f_c 频率计算 The PFC boost gain is to be computed at f_c

-零点及高极点位置没有灵活性 No flexibility in the zero and high pole locations

$$f_c = k \cdot f_{z1} = \frac{f_{p2}}{k}$$


▪极点和零点消除 Pole and zero cancellation:

✓设置补偿零点, 这样它就消除电源段极点 Place the compensation zero so that it cancels the power stage pole:

✓迫使极点位于原点, 从而在($f = f_c$)时消除PFC升压增益 Force the pole at the origin to cancel the PFC boost gain when ($f = f_c$)

✓以高频极点调节相位余量 Adjust the phase margin with the high frequency pole

极点和零点消除 Pole and Zero Cancellation...

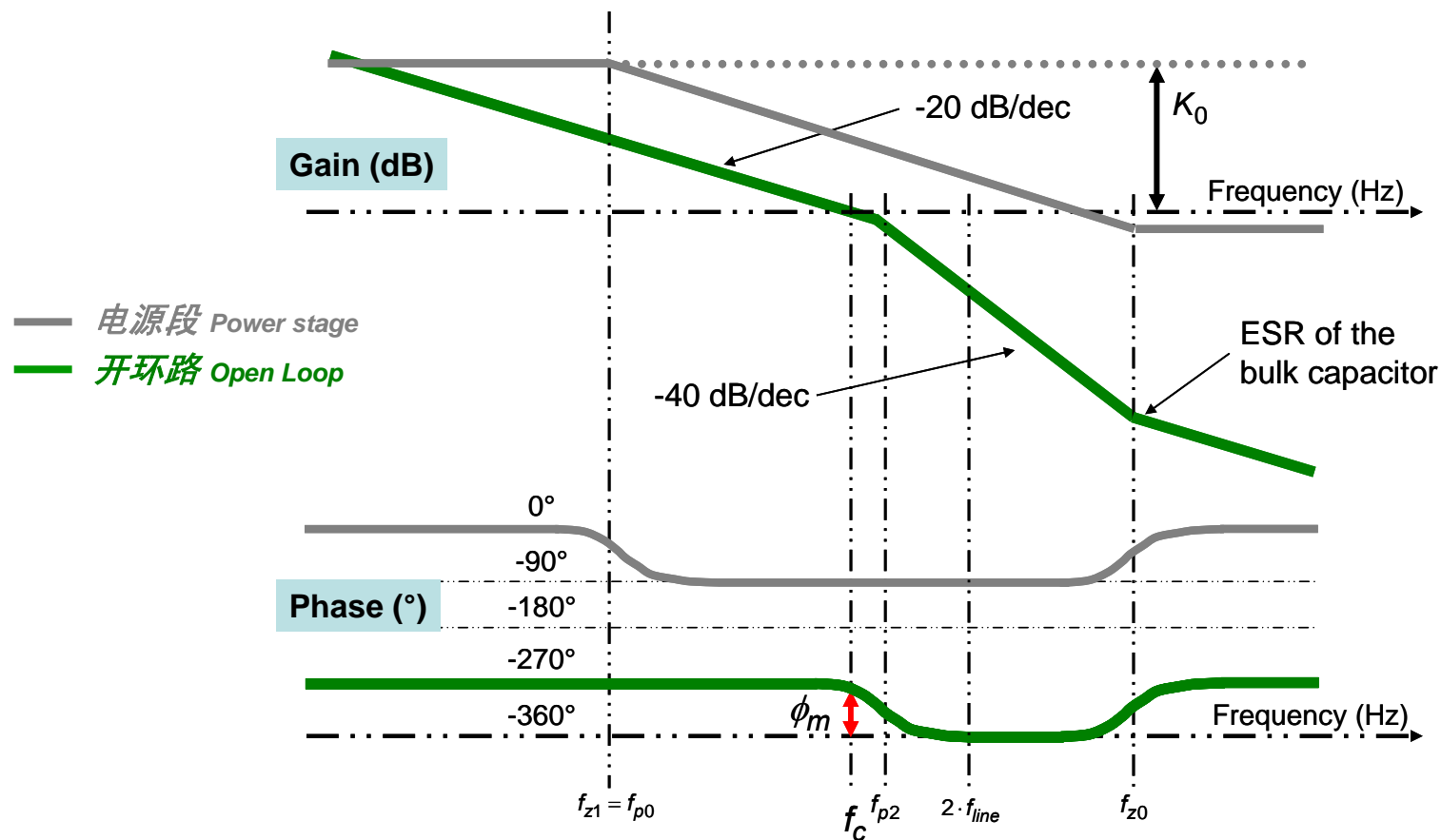

- f_{p2} 越高, 相位余量越大 The higher f_{p2} , the larger the phase margin
- f_{p2} 越低, 低频纹波抑制越佳 The lower f_{p2} , the better the rejection of the low frequency ripple
- $\phi_m = 45^\circ$ 若 if $f_{p2} = f_c$

极点和零点设置 Poles and Zero Placement

□ 针对满载、高线路输入来设计补偿

Design the compensation for full load, high line:

$$R_{LOAD} = R_{LOAD(min)}$$

□ 恰当设置原极点以消除 f_c 时的静态

增益 K_0 Place the origin pole to cancel K_0 , the static gain at f_c :

$$f_{p0} = \frac{f_c}{K_0} \quad \text{for } R_{LOAD} = R_{LOAD(min)}$$

where:
$$\hat{V}_{out} = K_0 \cdot \frac{1 + s \cdot r_C \cdot C_{bulk}}{1 + s \cdot \left(\frac{R_{LOAD(min)} \cdot C_{bulk}}{n + 2} \right)}$$

□ 恰当设置零点，消除PFC升压极点

Place the zero so that it cancels the PFC boost pole

$$(f_{z1} = f_{p0}) \quad \text{for } R_{LOAD} = R_{LOAD(min)}$$

□ 恰当设置 f_{p2} ，获得目标相位余量

Place f_{p2} to obtain the targeted phase margin:

$$f_{p2} = \frac{f_c}{\tan(90^\circ - \phi_m)}$$

示例 Example

❑ 宽范围主电源，基于NCP1605的150 W应用 A wide mains, 150-W application driven by the NCP1605

❑ $V_{out,nom} = 390 \text{ V}$

❑ $(V_{in(rms)})_{LL} = 90 \text{ V}$

❑ $(V_{in(rms)})_{HL} = 265 \text{ V}$

❑ $L = 150 \mu\text{H}$

❑ $C_t = 4.7 \text{ nF}$

❑ $C_{bulk} = 100 \mu\text{F}$

❑ $r_C = 500 \text{ m}\Omega$ (ESR)

❑ $f_c = 50 \text{ Hz}$

and $F_m = 60^\circ$

@ high line (265 V)

$$\frac{\hat{V}_{out}}{\hat{V}_{CONTROL}} = K_0 \cdot \frac{1 + s \cdot r_C \cdot C_{bulk}}{1 + s \cdot \left(\frac{R_{LOAD} \cdot C_{bulk}}{4} \right)} \quad \text{where: } K_0 = \frac{R_{LOAD} \cdot C_t \cdot (V_{in(rms)})^2}{24 \cdot L \cdot I_t \cdot V_{out,nom}}$$

$$R_{LOAD(min)} = \frac{(V_{out,nom})^2}{(P_{out})_{max}} = \frac{390^2}{150} \cong 1 \text{ k}\Omega$$

$$R_0 = \frac{V_{out,nom}}{V_{ref} \cdot G_{EA}} = \frac{390}{2.5 \cdot 200 \cdot 10^{-6}} = 780 \text{ k}\Omega \quad (\text{OTA})$$

$$C_1 = \frac{K_{0(min)}}{2\pi \cdot f_c \cdot R_0} = \frac{R_{LOAD(min)} \cdot C_t \cdot (V_{in(rms)})_{HL}^2}{2\pi \cdot f_c \cdot R_0 \cdot 24 \cdot L \cdot I_t \cdot V_{out,nom}} = \frac{10^3 \cdot 4.7 \cdot 10^{-9} \cdot 265^2}{2\pi \cdot 50 \cdot 780 \text{ k} \cdot 24 \cdot 150 \mu \cdot 370 \mu \cdot 390} \cong 2.59 \mu\text{F} \implies 2.2 \mu\text{F}$$


$$R_1 = \frac{R_{LOAD(min)} \cdot C_{bulk}}{(n+2) \cdot C_1} = \frac{10^3 \cdot 100 \cdot 10^{-6}}{(2+2) \cdot 2.2 \cdot 10^{-6}} \cong 11.36 \text{ k}\Omega \implies 12 \text{ k}\Omega$$

$$C_2 = \frac{\tan(90^\circ - \phi_m)}{2\pi \cdot f_c \cdot R_1} = \frac{\tan(90^\circ - 60^\circ)}{2\pi \cdot 50 \cdot 12 \cdot 10^3} \cong 153 \text{ nF} \implies 150 \text{ nF}$$


$$f_{p1} = \frac{1}{2\pi \cdot R_0 \cdot C_1} = 93 \text{ mHz} \quad f_{z1} = \frac{1}{2\pi \cdot R_1 \cdot C_1} = 6 \text{ Hz} \quad f_{z2} = \frac{1}{2\pi \cdot R_1 \cdot C_2} = 88 \text{ Hz}$$

仿真验证 Simulation Validation

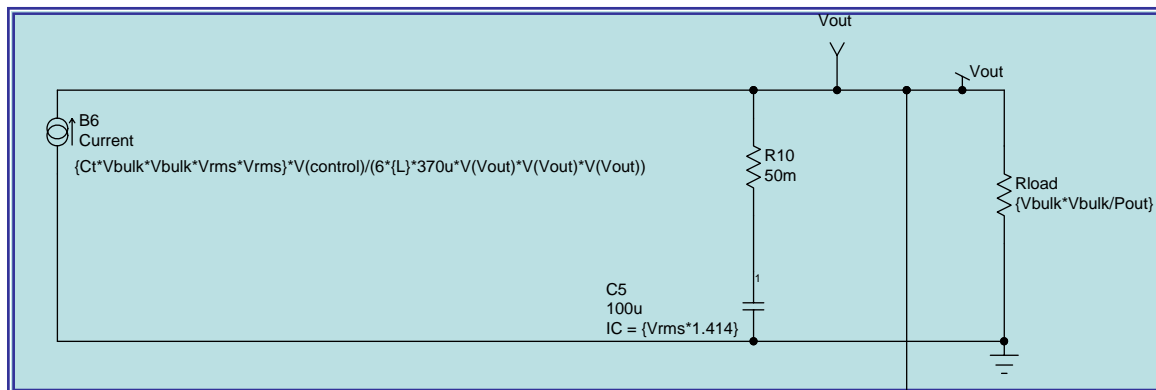
□ 仿真电路基于大信号模型 The simulation circuit is based on the large signal model:



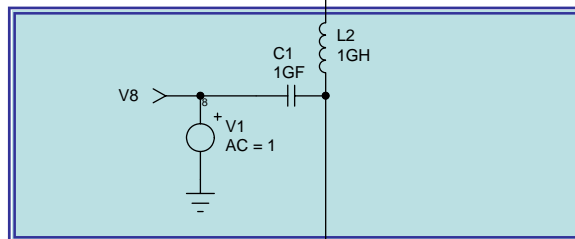← 采用NCP1605的PFC段的大信号模型 Large signal model of the NCP1605-driven PFC stage




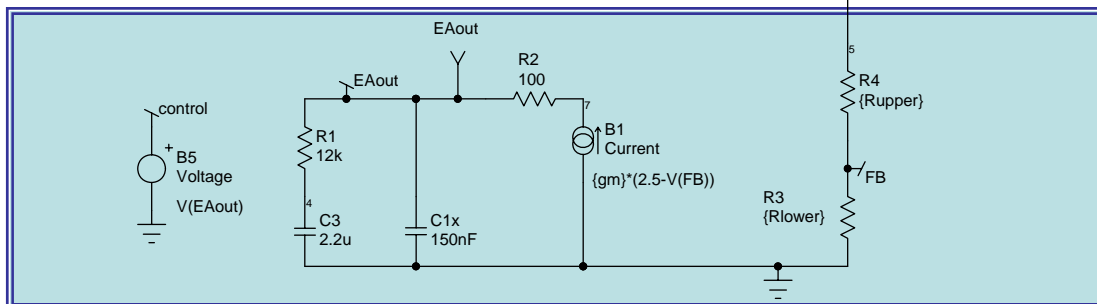← 交流干扰的产生及抑制 Generation and injection of the ac perturbation




← 反馈及稳压电路(含第2类补偿) Feedback and regulation circuit (including type-2 compensation)

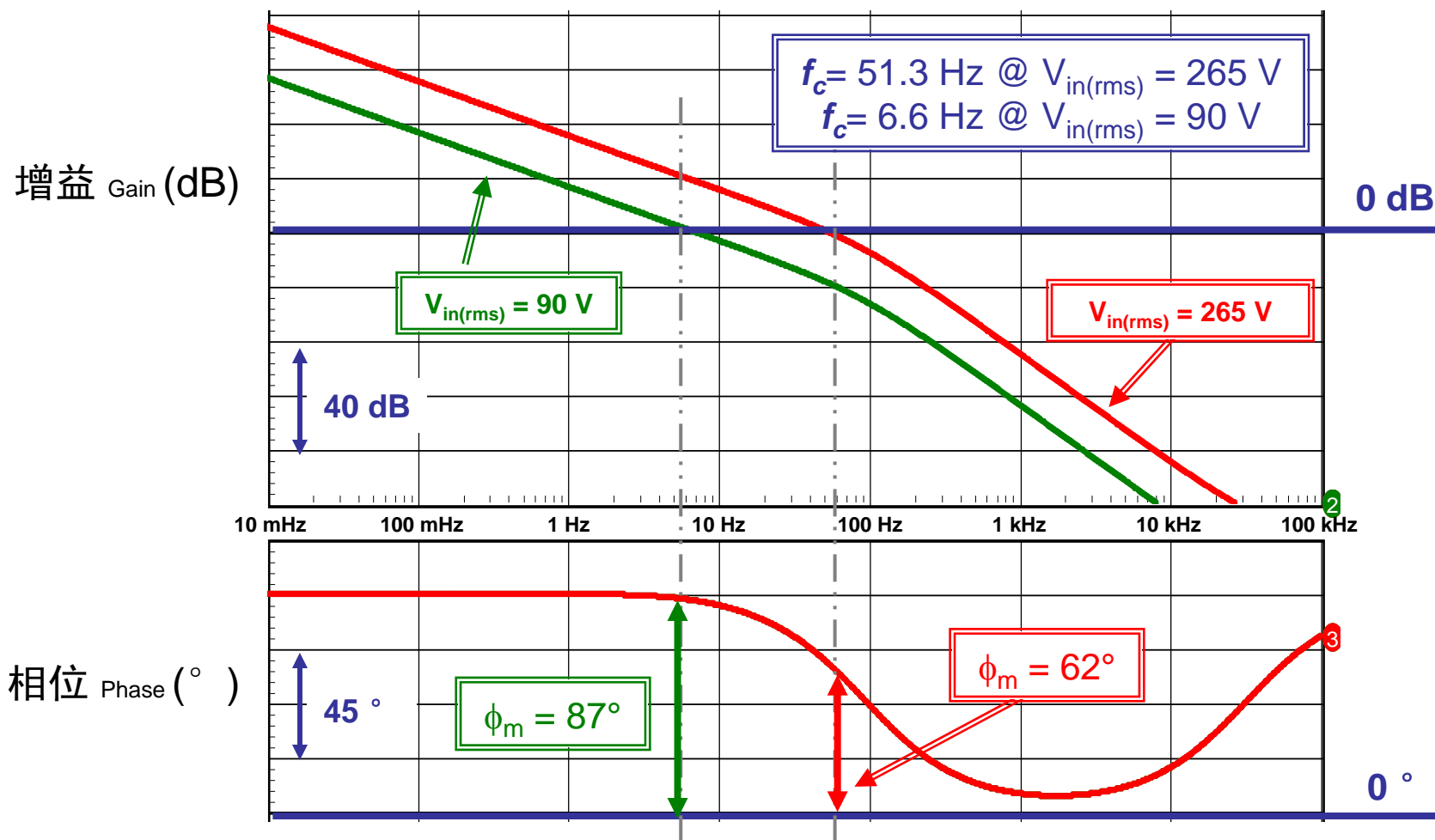环路开路特性-满载 Open Loop Characteristic – Full Load




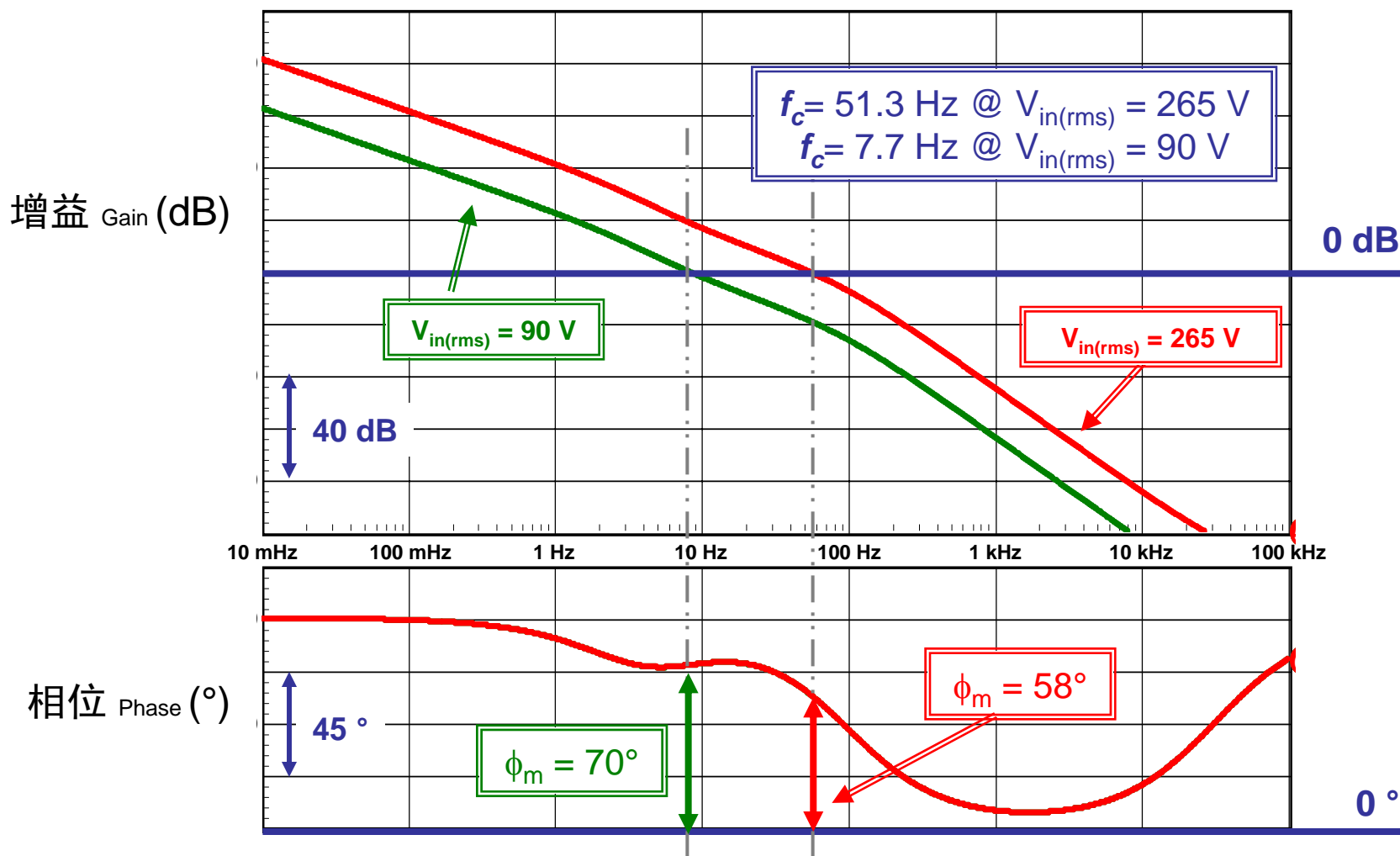环路开路特性-中等负载 Open Loop Characteristic – Mid Load



满载实验结果 Experimental Results at Full Load


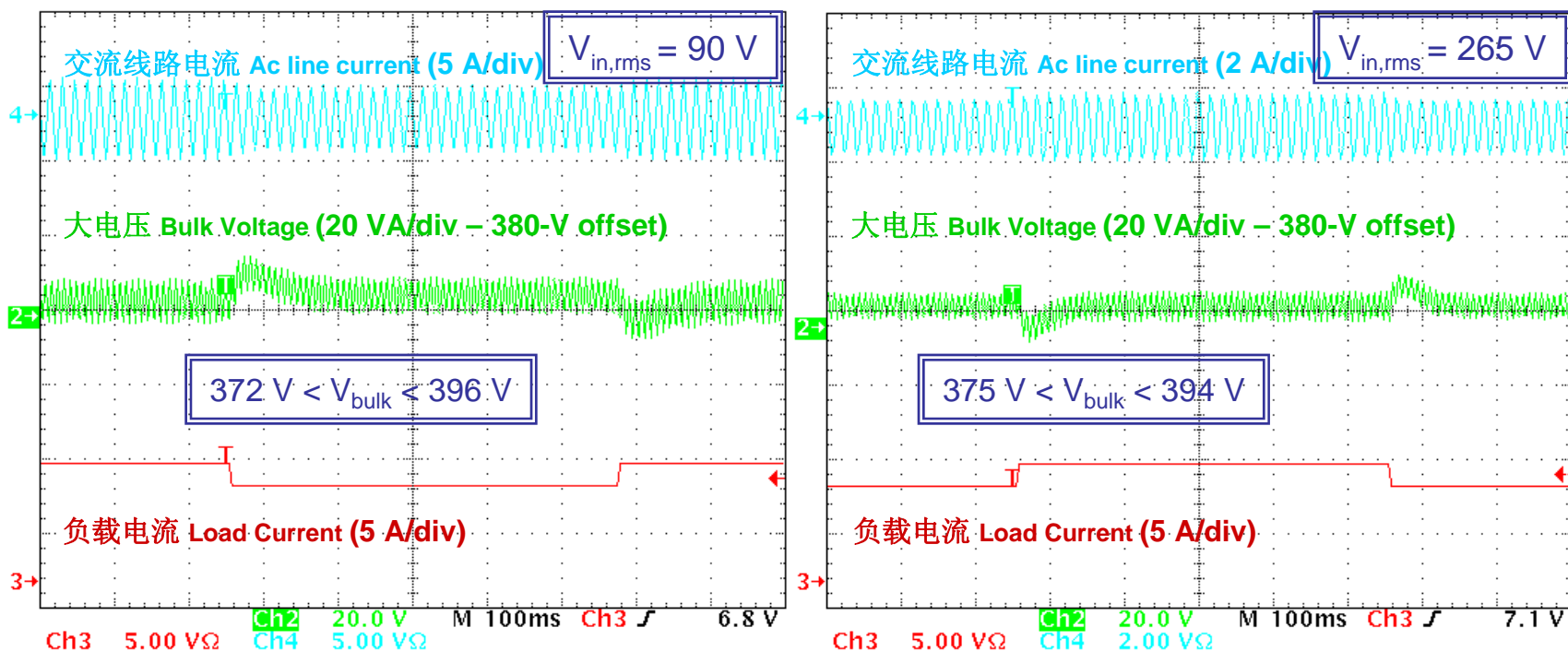
- ❑ PFC段负载为19 V/7 A A 19-V / 7-A loads the PFC stage
- ❑ 下行转换器电流在6.3 A与7.7 A之间摆动($\pm 10\%$), 并带有2 A/ μs 的斜坡
The downstream converter swings between 6.3 A and 7.7 A ($\pm 10\%$) with a 2-A/ μs slope



- ❑ 高线路输入、较大带宽降低 V_{bulk} 漂移, 加速输出电压恢复 The high-line, larger bandwidth reduces the V_{bulk} deviations and speeds-up the output voltage recovery

中等负载实验结果 Experimental Results at Medium Load

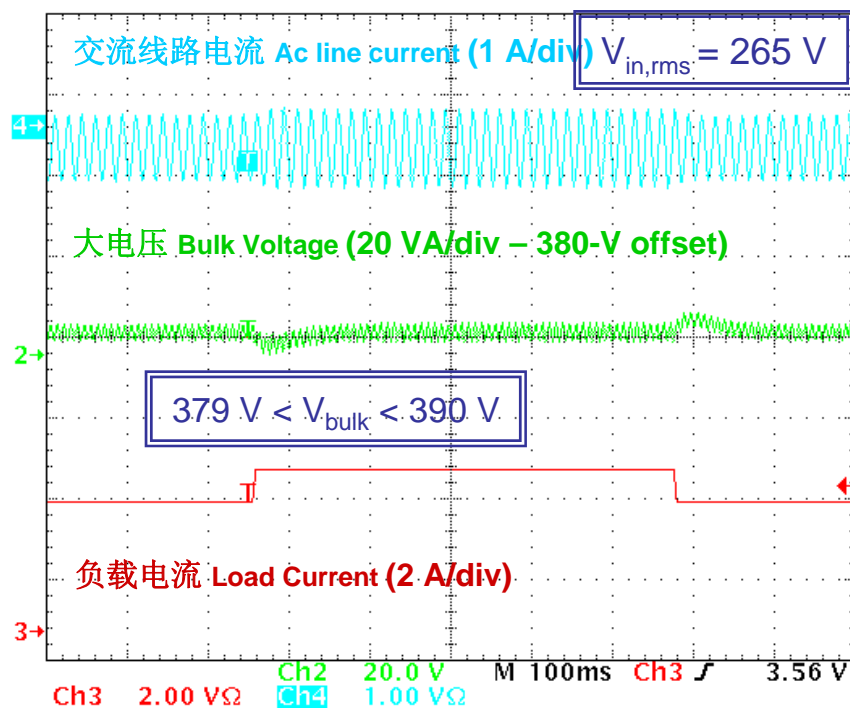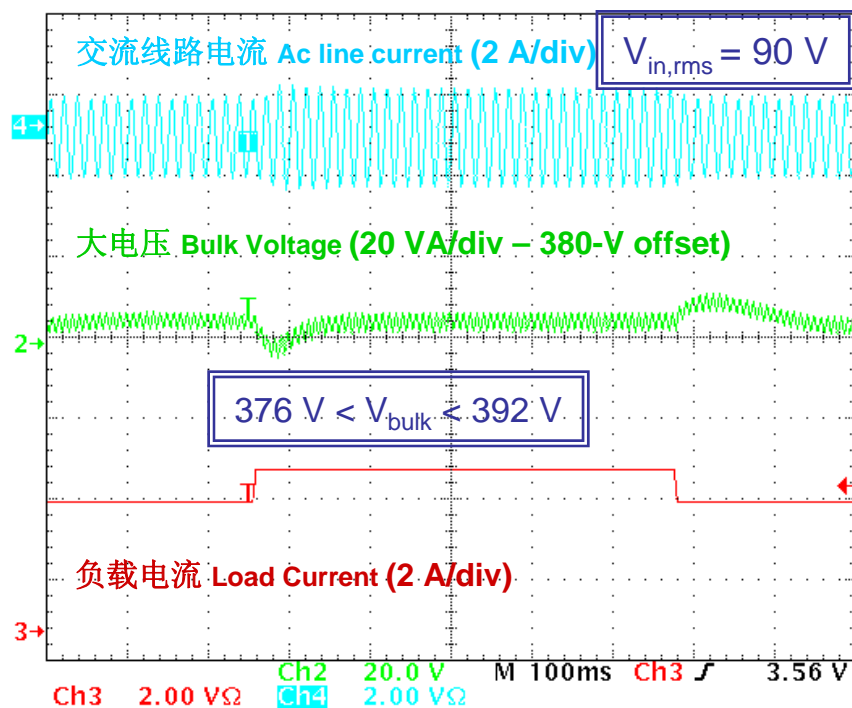
- ❑ PFC段负载为19 V/7 A A 19-V / 7-A loads the PFC stage
- ❑ 下行转换器电流在3.1 A与3.9 A之间摆动($\pm 10\%$), 并带有2 A/ μs 的斜坡
The downstream converter swings between 3.1 A and 3.9 A ($\pm 10\%$) with a 2-A/ μs slope



- ❑ 电路仍然呈现一阶响应 The circuit still exhibits a first order response

陡然负载改变 Abrupt Load Changes

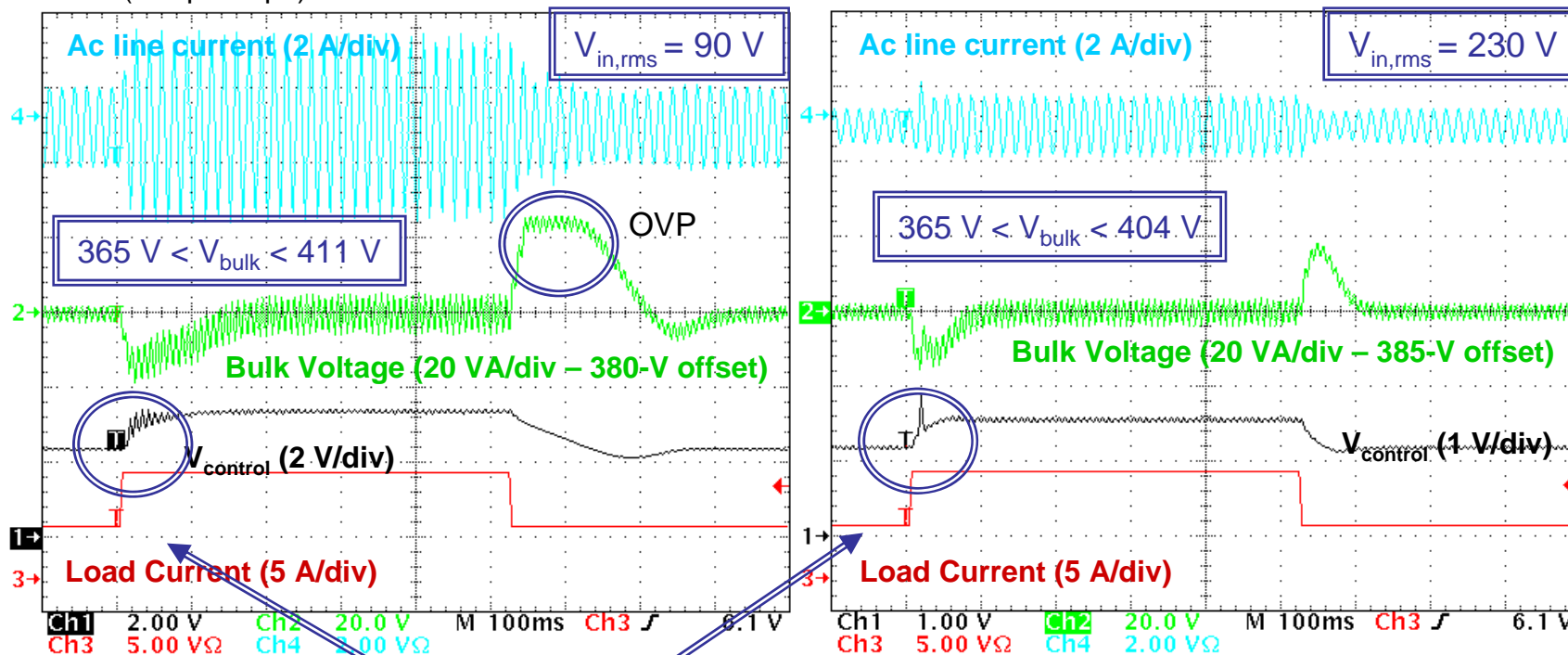- ❑ PFC段负载为19 V/7 A A 19-V / 7-A loads the PFC stage
- ❑ 下行转换器电流在7.0 A至3.5 A间摆(2 A/ μ s斜坡) The downstream converter swings from 7.0 A to 3.5 A (2-A/ μ s slope)



NCP1605(FCCrM)、NCP1654(CCM)和NCP1631(交错式)中应用了动态响应增强器，在出现较大欠冲时加速环路反应速度 The dynamic response enhancer speeds-up the loop reaction in case of a large undershoot Implemented in NCP1605 (FCCrM), NCP1654 (CCM) and NCP1631 (Interleaved)

- ❑ 动态响应增强器减少低交流线路输入时的欠冲 The dynamic response enhancer reduces the undershoot at low line

议程 Agenda

□ 简介 Introduction

□ 导出小信号模型 Deriving a small-signal model

- 一般方法 General method
- 实际案例：NCP1605驱动PFC段 Practical example: NCP1605-driven PFC stages

□ 补偿环路 Compensating the loop

- 第2类补偿 Type-2 compensation
- 交流线路及功率电平影响 Influence of the line and power level
- 计算补偿 Computing the compensation
- 实际案例 Practical example

□ 总结 Summary

总结 Summary

- ❑ 以基于NCP1605的PFC为例，阐述了PFC补偿的一般考虑因素
General considerations were illustrated by the case of NCP1605-driven PFC stages
- ❑ 能够轻易导出升压PFC的小信号模型
A small signal model of PFC boosts can be easily derived
- ❑ 建议的方法与PFC工作模式无关
The proposed method is independent of the operating mode
- ❑ 推荐第2类补偿 A type-2 compensation is recommended
- ❑ 如果没有应用前反馈，环路带宽和相位余量跟线路幅度的函数变化
If no feed-forward is implemented, the loop bandwidth and phase margin vary as a function of the line magnitude
- ❑ 交越频率不跟随负载的函数而变化
The crossover frequency does not vary as a function of the load
- ❑ 即使PFC段为电源馈电(负阻抗)，也能使用电阻型负载-参见备份资料
A resistive load can be used for the computation even if the PFC stage feeds a power supply (negative impedance) – See back-up

For More Information

- ❑ View the extensive portfolio of power management products from ON Semiconductor at www.onsemi.com
- ❑ View reference designs, design notes, and other material supporting the design of highly efficient power supplies at www.onsemi.com/powersupplies