



CM-LLC Power Stage Dynamic Response

Christophe Basso – Technical Fellow
IEEE Senior Member


ON Semiconductor[®]



The Basic Blocks of a Closed-Loop CM-LLC Converter

- ❑ Before applying a compensation strategy to any converter, you need its control-to-output transfer function
- ❑ $H(s)$ for a CM-LLC converter cannot be obtained mathematically using a simple model
- You need to either build a prototype on the bench or use a piece wise linear simulator like SIMPLIS®

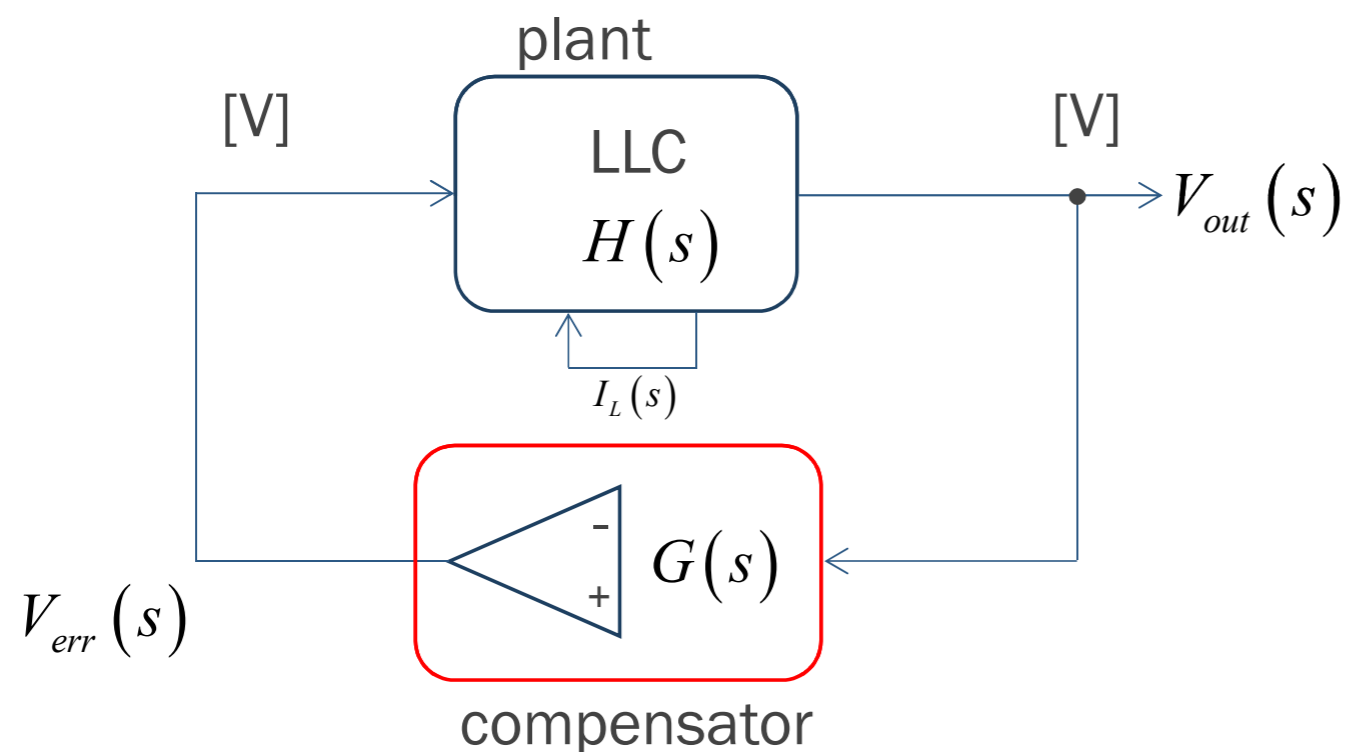The basic blocks assembly for the CM-LLC is as below:




$$T(s) = G(s)H(s)$$


- The compensator delivers a control voltage proportional to input/output operating conditions. The voltage sets the resonating tank current setpoint. It is a current-mode-control type.
- The plant is the LLC power stage, including the resonating elements and the transformer. The power transfer depends on the operating frequency.
- The compensator is where you apply the compensation strategy to cross over at a certain frequency with a given phase margin.

Basic Principles of Operation of the CM-LLC Converter

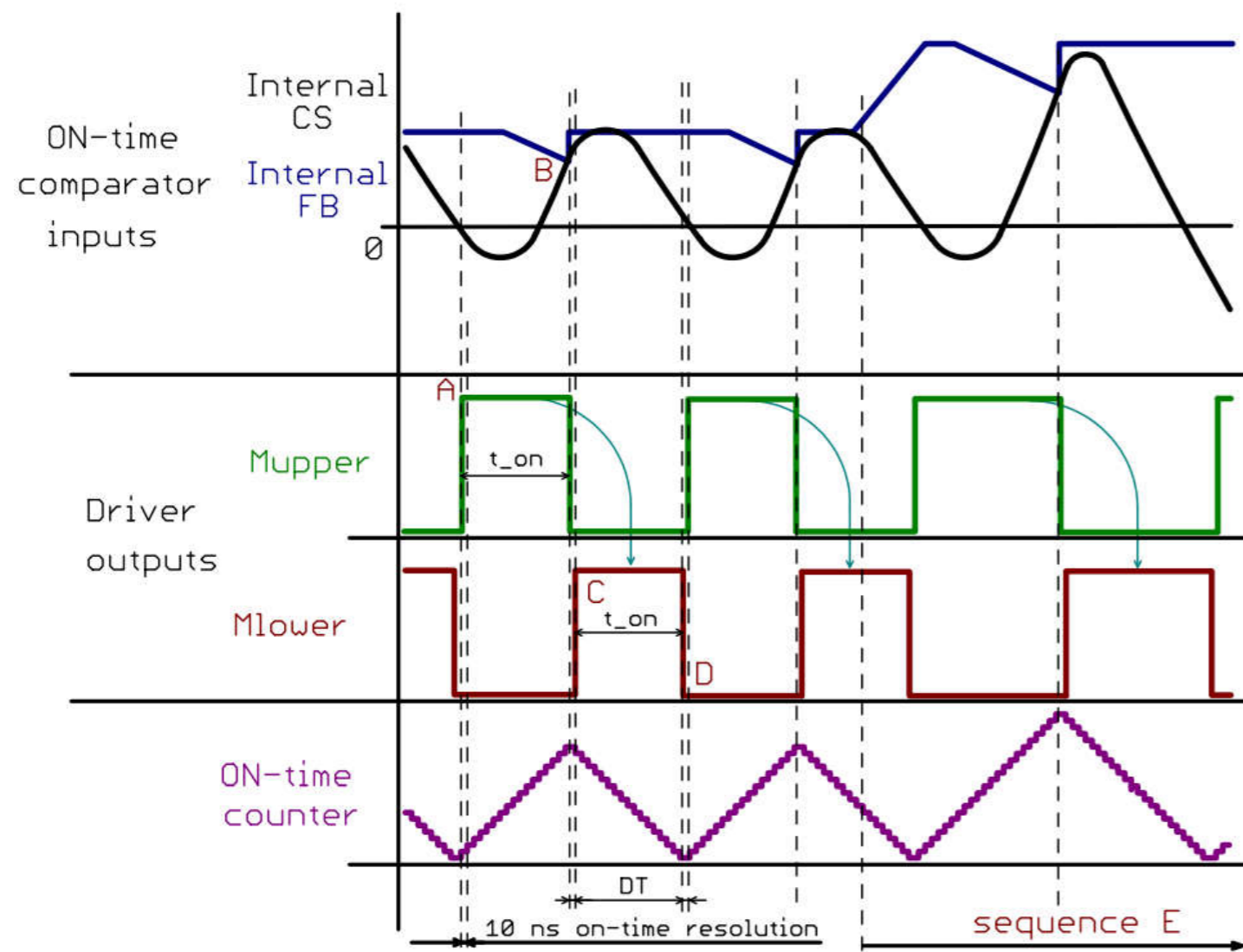
- ❑ This CM-LLC operates in a free-running mode: the switching frequency is not internally fixed
 - The on-time is set by the peak current setpoint while the off-time precisely replicates its duration
 - The circuit ensures a 50% duty ratio square wave whose frequency depends on the peak current setpoint.



NCP1399 data-sheet

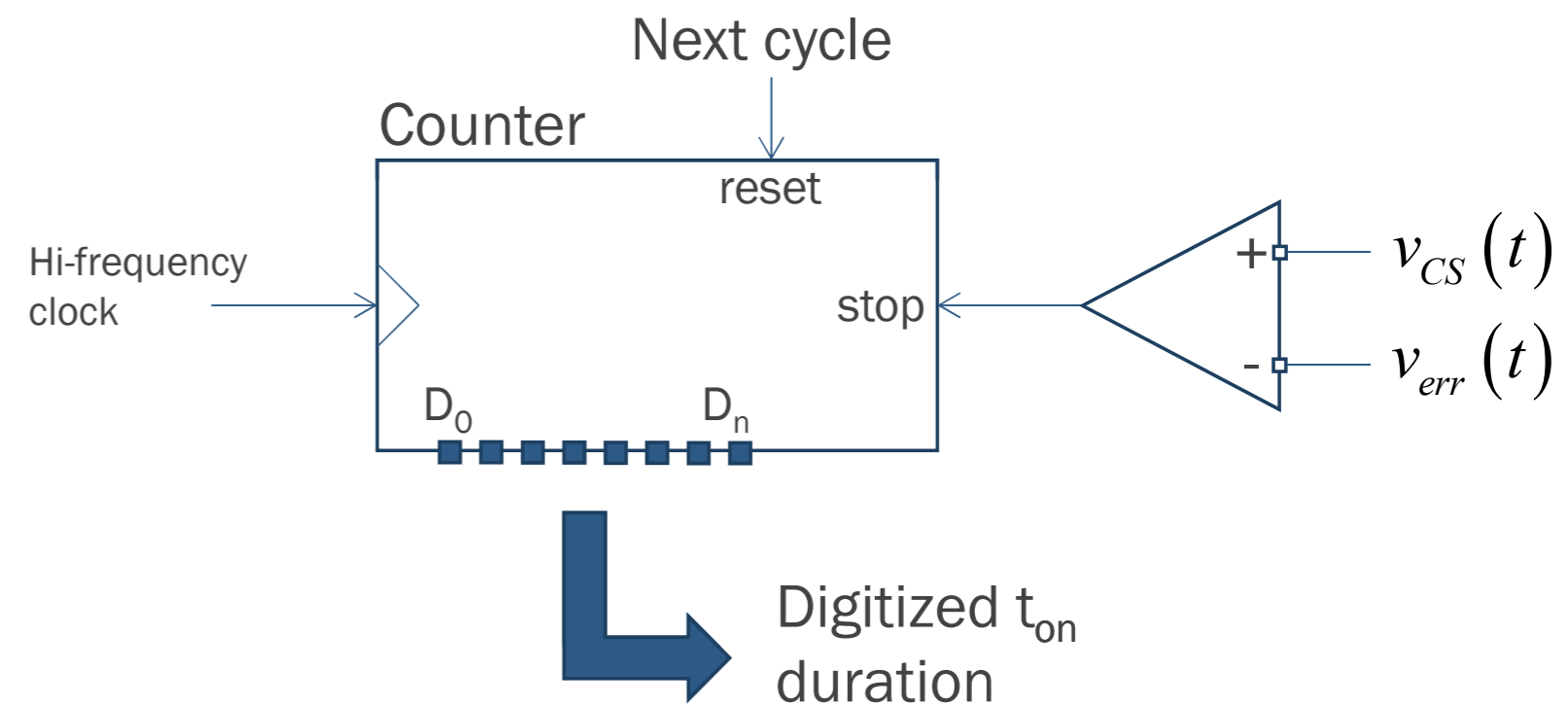

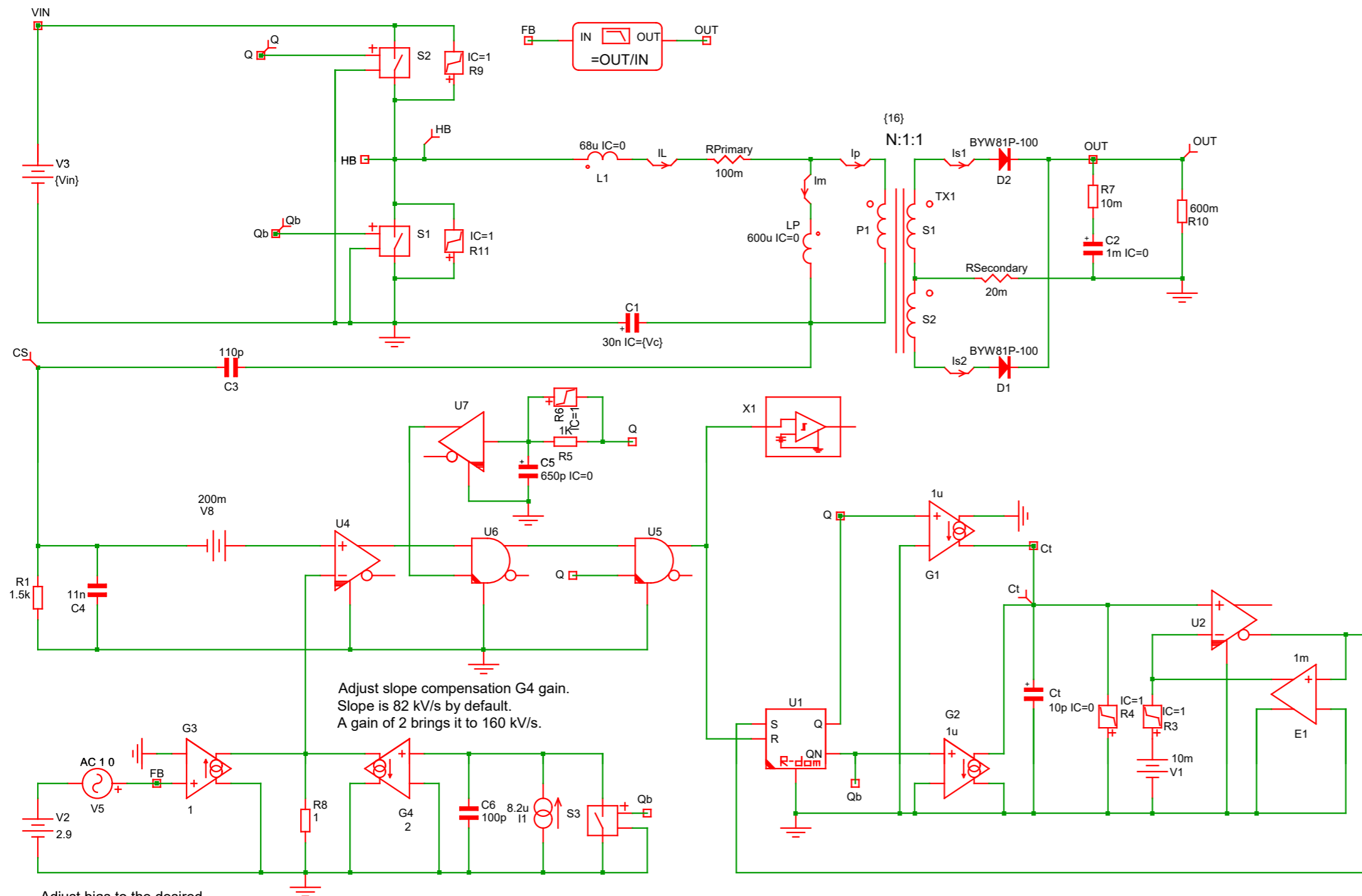Application Circuit Working with Elements




Adjust bias to the desired Vout level. Here, a 2.9-V bias gives 12 V/20 A.

□ This is a 12-V/20-A LLC converter as described in the NCP1399 landing page: <https://www.onsemi.com/pub/Collateral/EVBUM2342-D.PDF>

Ok with demo version




Obtaining Steady-State Waveforms

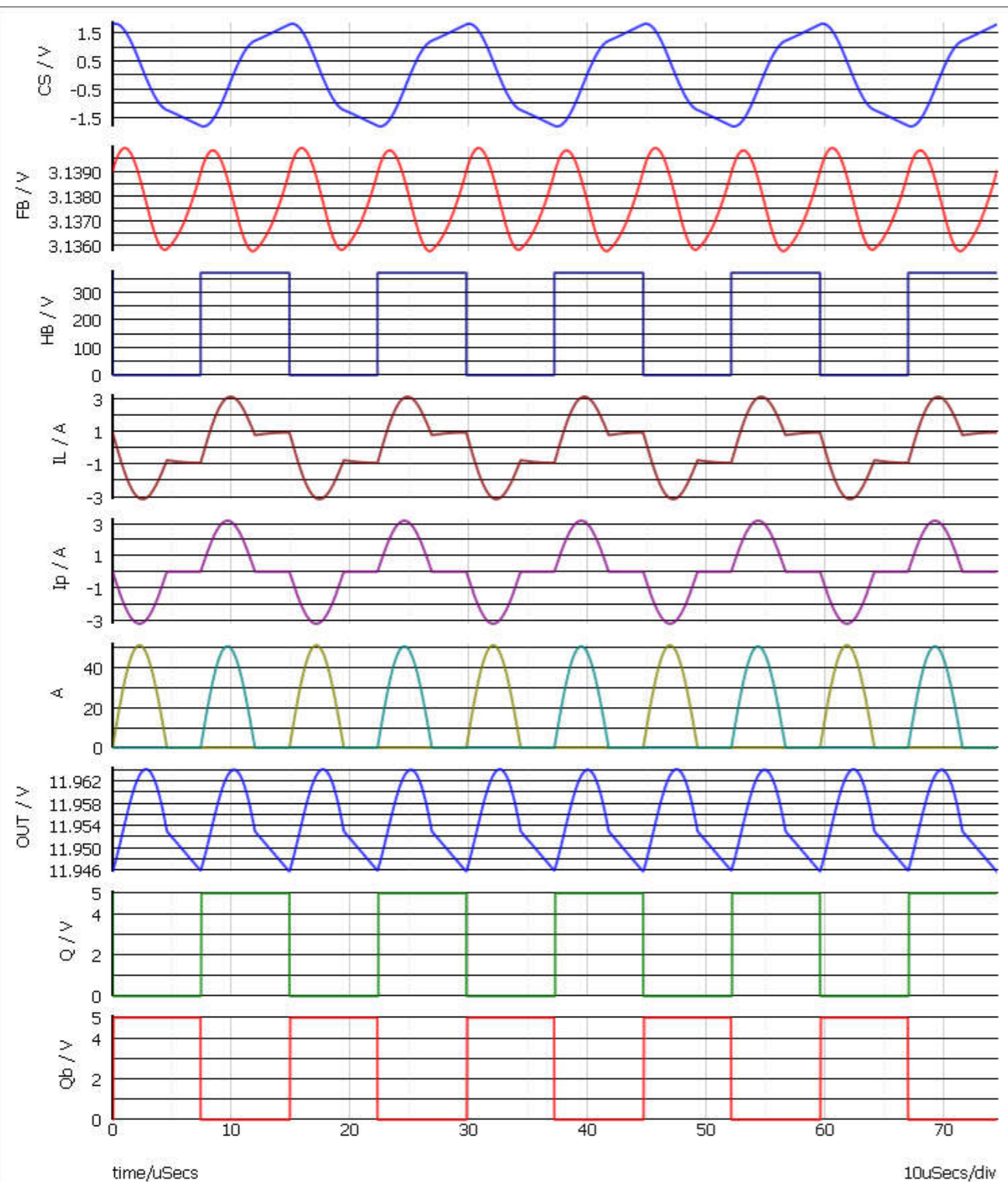



$$V_{in} = 400 \text{ V}$$

- You can check the waveforms at steady-state operation and assess peak and rms values.

$$V_{in} = 370 \text{ V}$$

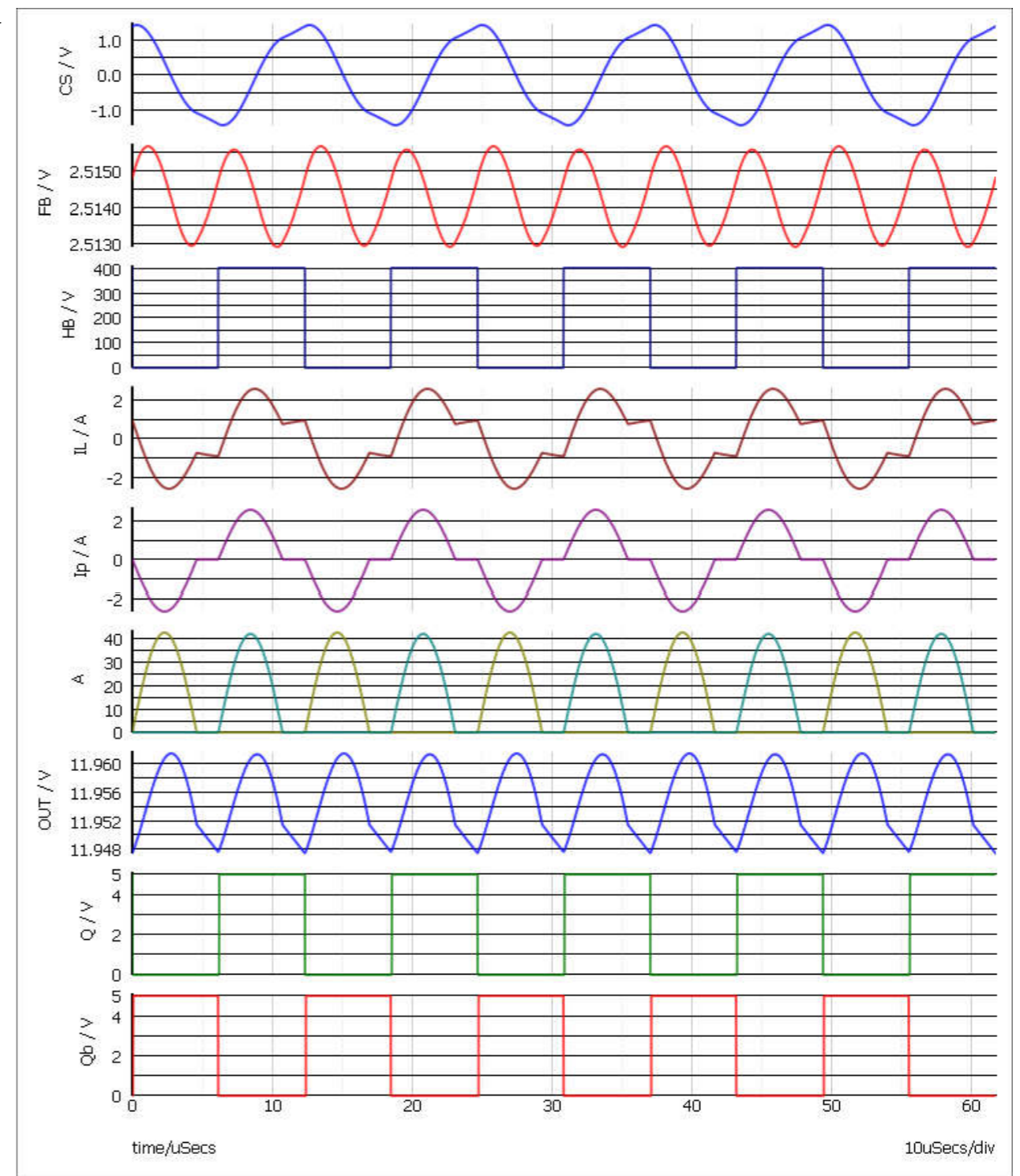

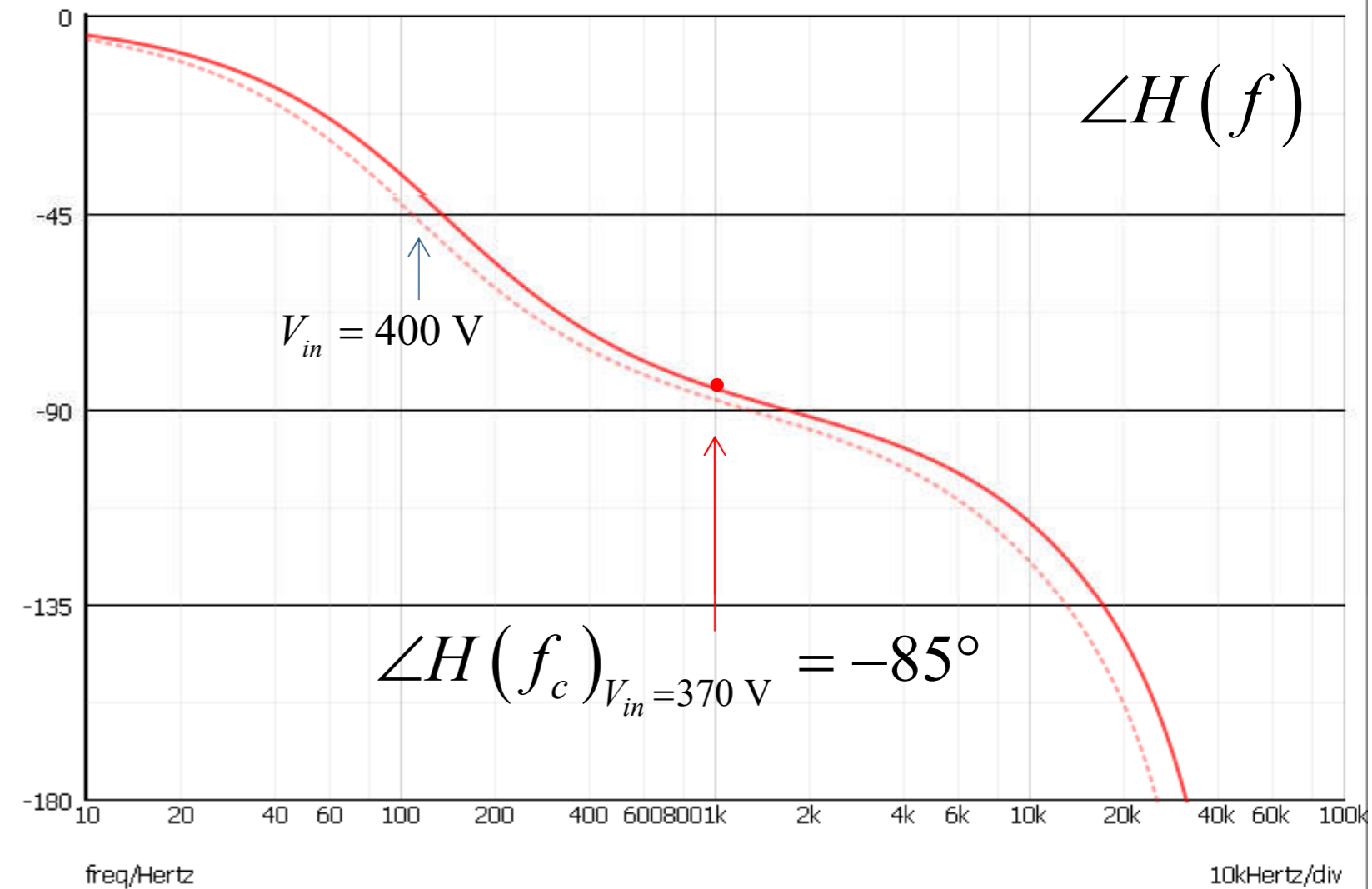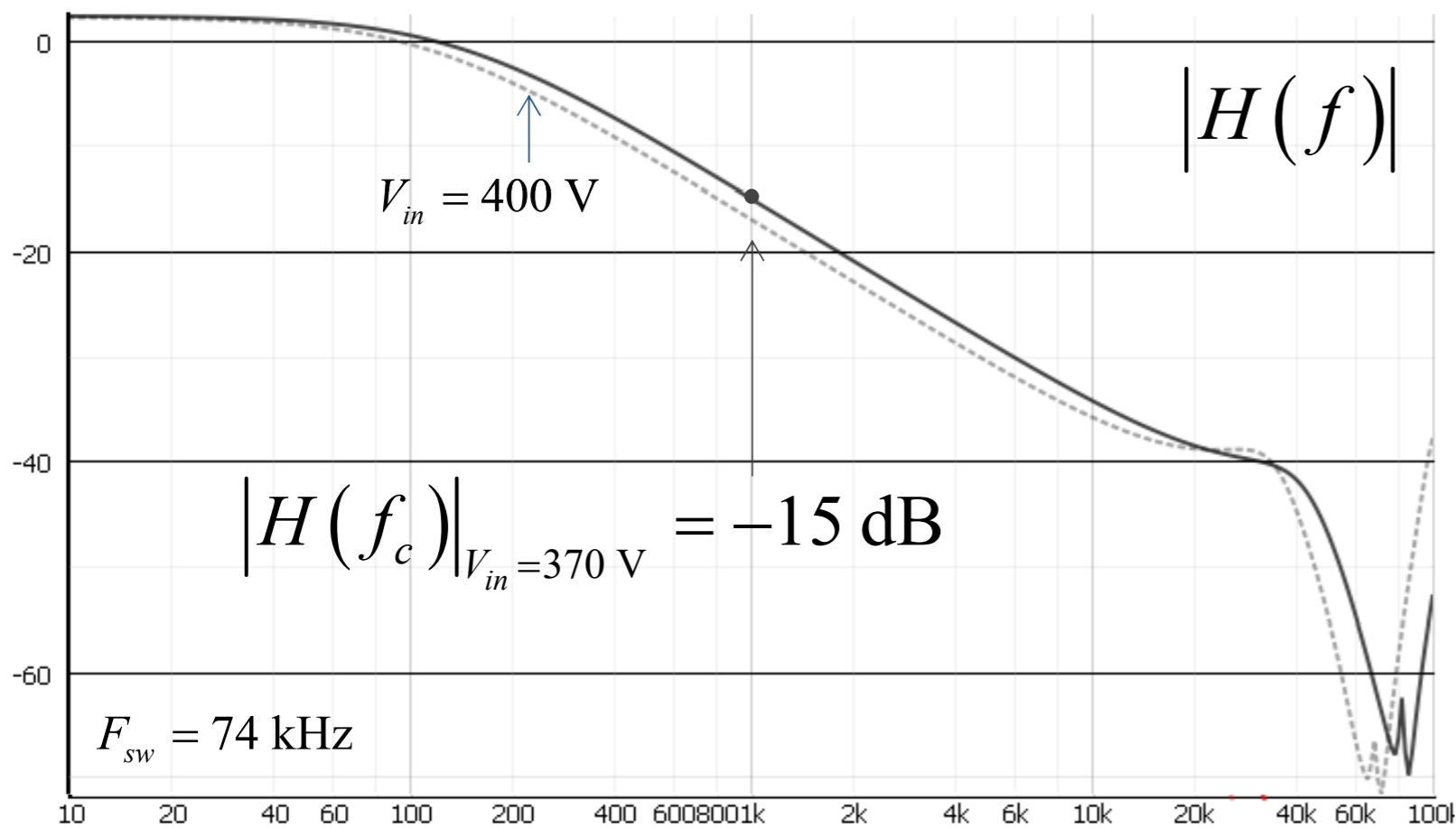Check Response at Different Input Voltages




- One benefit of the CM operation is the 1st-order response.
- The control-to-output transfer function remains the same from 370 V dc to 400 V dc.




For a 1-kHz crossover frequency, a simple type-2 compensator will do!

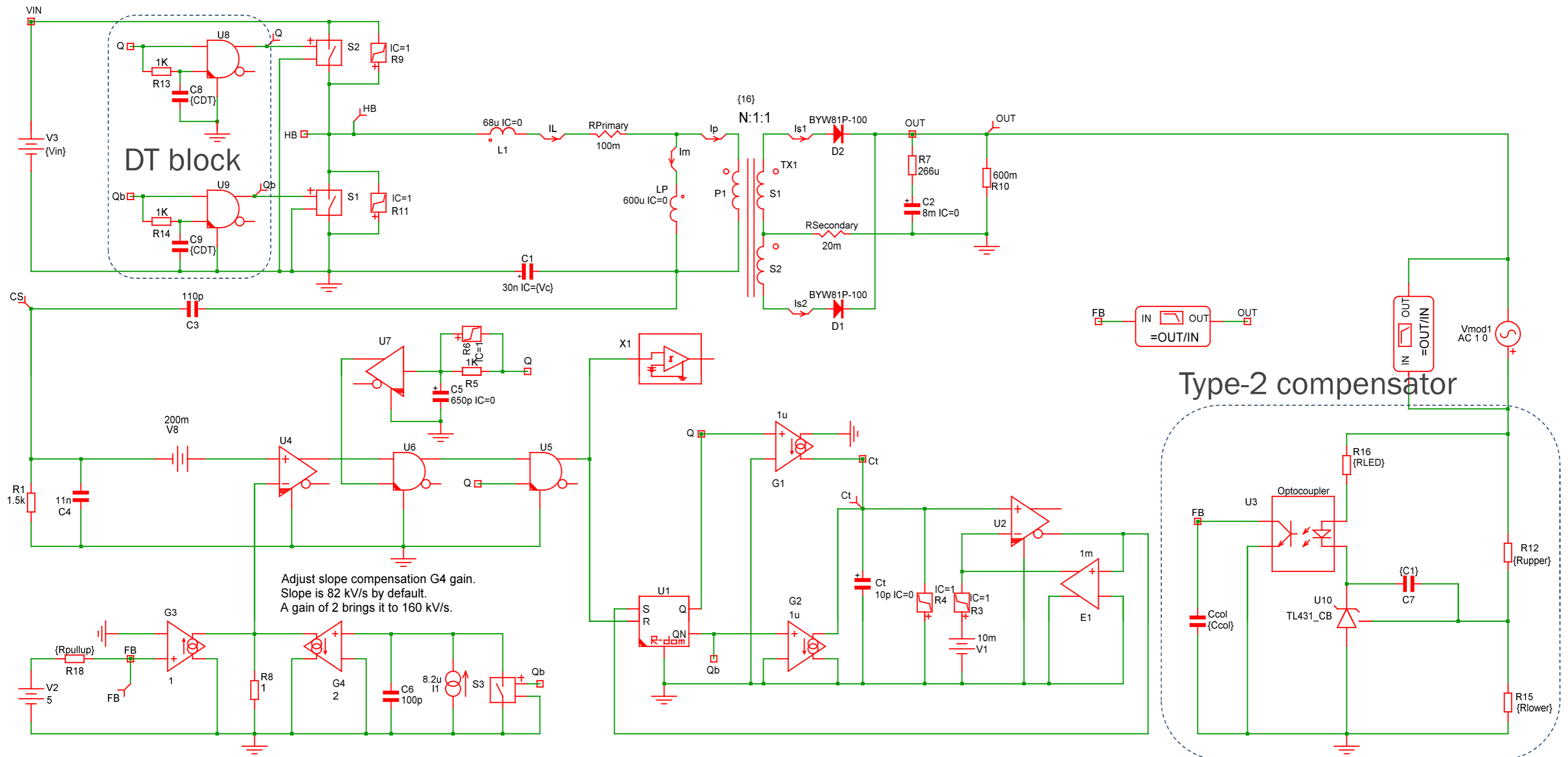Now Include Dead Time and Loop with Full Version



Type 2 Compensator with Optocoupler

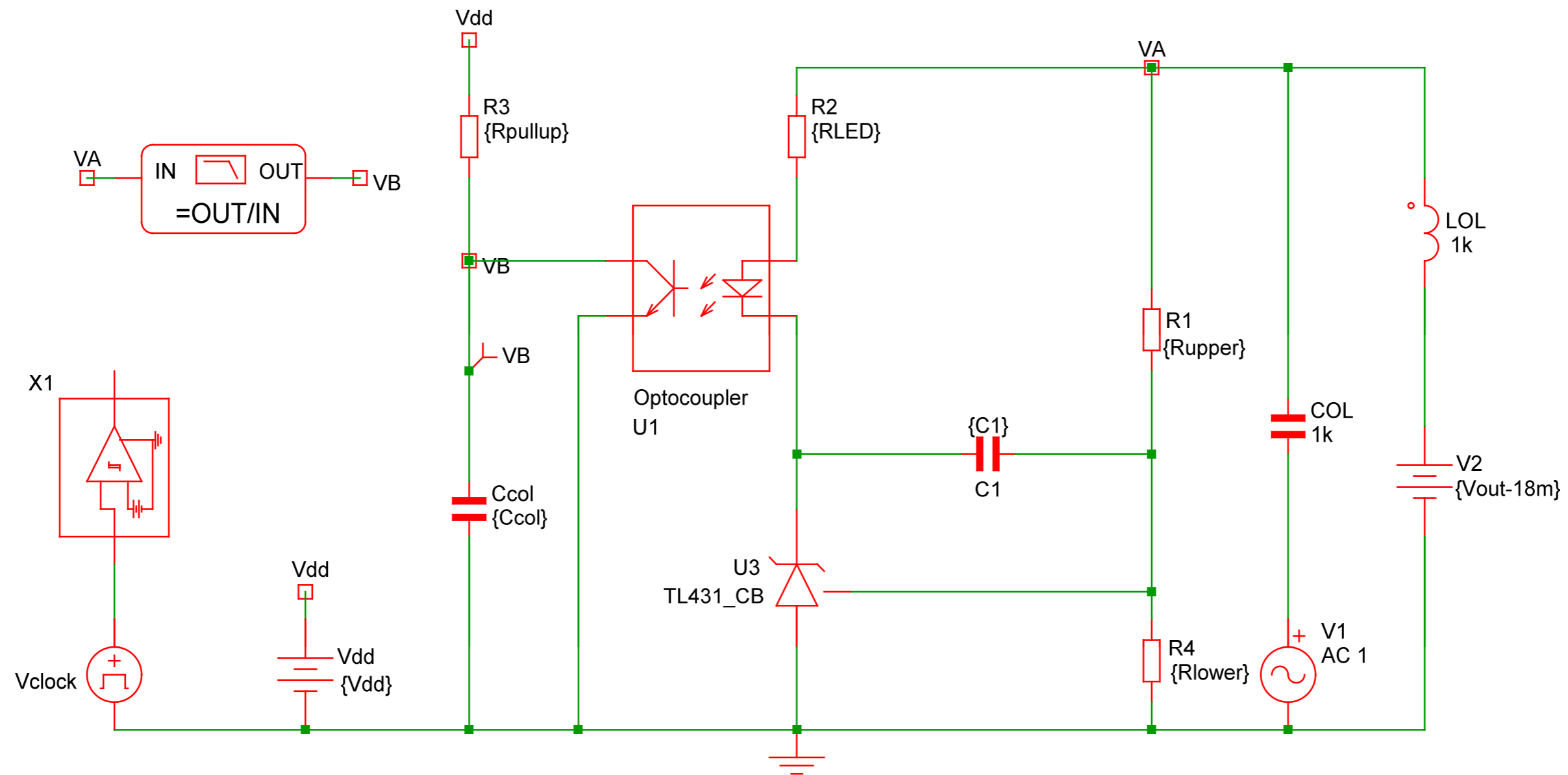- The component values are calculated by SIMPLIS[®] to meet the needed gain and phase boost





Component Calculations for the Type 2

```


41
22 .GLOBALVAR Vin=370 * the input source voltage *
23 .GLOBALVAR Vc=Vin/2 * pre-charged resonating capacitor *
24 .GLOBALVAR DT=50n * select HB deadtime *
25 .GLOBALVAR CDT=DT/(1k*0.693) * calculate DT capacitor *
26
27 .GLOBALVAR Gfc=-18 * magnitude at crossover *
28 .GLOBALVAR PFC=-87 *plant phase at crossover *
29 .GLOBALVAR PM=70 * phase margin goal *
30 .GLOBALVAR boost=pm-(pfc)-90 * required boost *
31 *
32 * Enter Design Goals Information Here *
33 *
34 .GLOBALVAR fc=1k * targetted crossover *
35 *
36 * Pole-zero calculations *
37 *
38 .GLOBALVAR k=tan((boost/2+45)*pi/180)
39 .GLOBALVAR fp=k*fc
40 .GLOBALVAR fz=fc/k
41 *
42 * Enter the Values for Vout and Bridge Bias Current *
43 *
44 .GLOBALVAR Vout=12
45 .GLOBALVAR Ibias=250u
46 .GLOBALVAR Vref1=2.5
47 .GLOBALVAR Rlower=Vref1/Ibias
48 .GLOBALVAR Rupper=(Vout-Vref1)/Ibias
49 .GLOBALVAR Rpullup=18k
50 *
51 * Optocoupler specifications *
52 *
53 .GLOBALVAR Fopto=15k
54 .GLOBALVAR Copto=1/(2*pi*Fopto*Rpullup)
55 .GLOBALVAR CTR=0.3
56 *
57 .GLOBALVAR VL=0.2
58 .GLOBALVAR VCESat=0.3
59 .GLOBALVAR Vdd=5
60 .GLOBALVAR Vf=1
61 .GLOBALVAR A=Vout-Vf-VL
62 .GLOBALVAR B=Vdd-VCESat
63 .GLOBALVAR Rmax=(A/B)*Rpullup*CTR
64 *
65 * Do not edit the below lines *
66 *
67 .GLOBALVAR G=10^(-Gfc/20)
68 .GLOBALVAR RLED=CTR*Rpullup/G * watch for internal LED rd contribution for low RLED *
69 .GLOBALVAR C1=1/(2*pi*fz*Rupper)
70 .GLOBALVAR C2=1/(2*pi*fp*Rpullup)
71 .GLOBALVAR Ccol=C2-Copto
72 *
73
74 .simulator DEFAULT
75

```

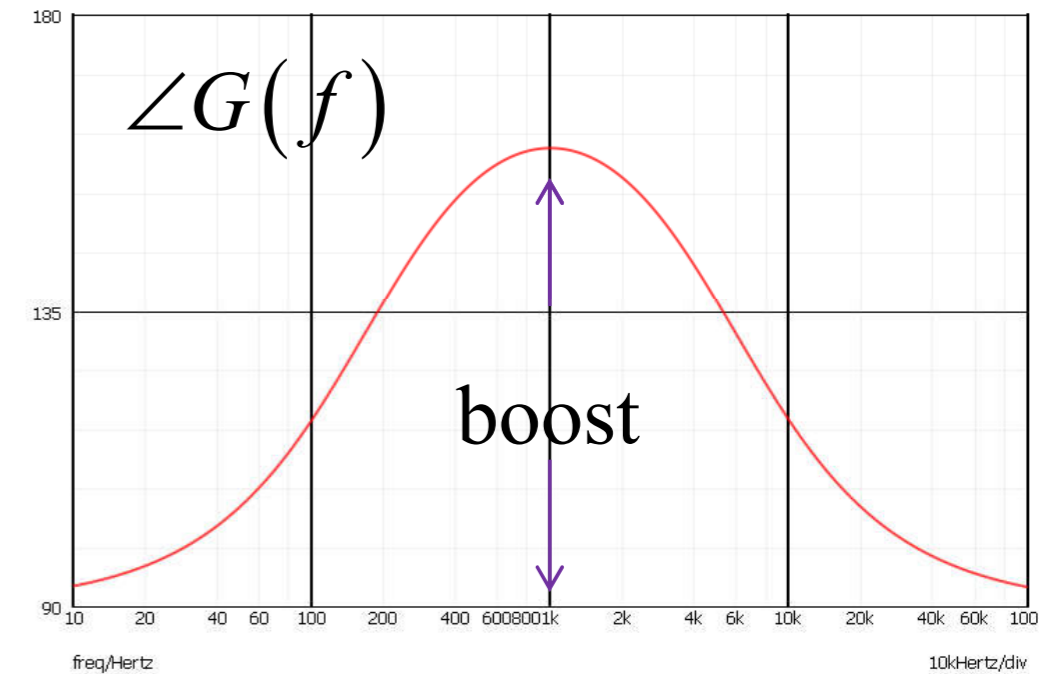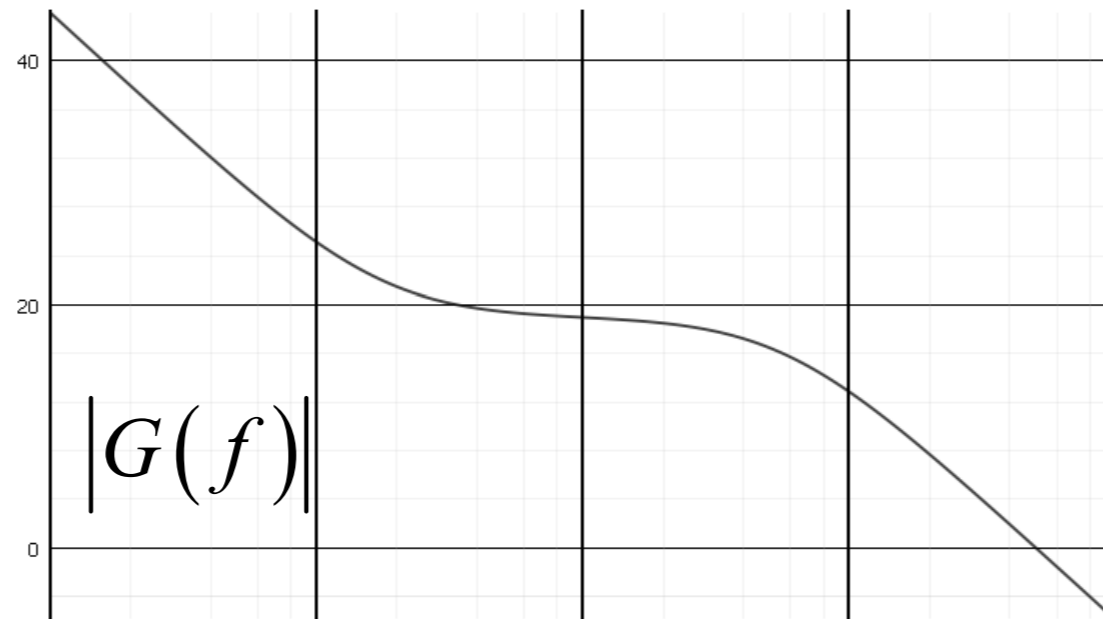Power stage magnitude at f_c
 Power stage phase at f_c
 Wanted phase margin




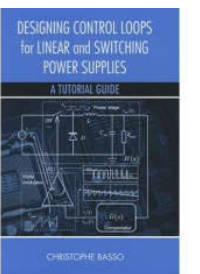Type 1, 2 and 3 design details can be found in C. Basso, *Designing Control Loops for Linear and Switching Power Supplies*, Artech House 2012




Compensated Loop Gain

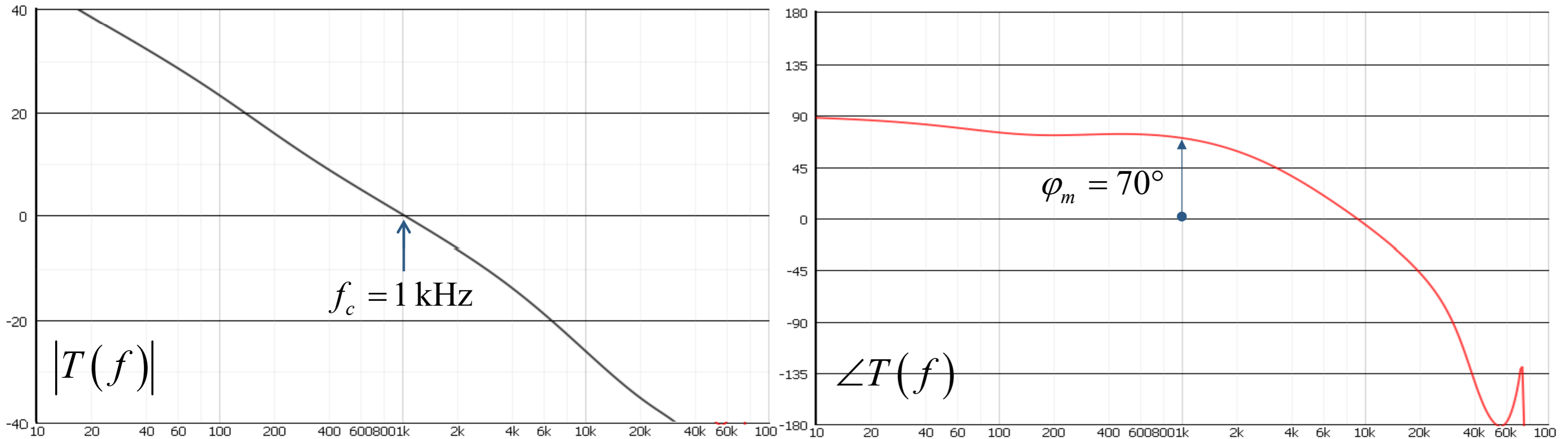- Plot the loop gain to check crossover frequency and phase margin at this point



A 1-kHz crossover frequency is obtained with a 70° phase margin.

Compensated Transient Response

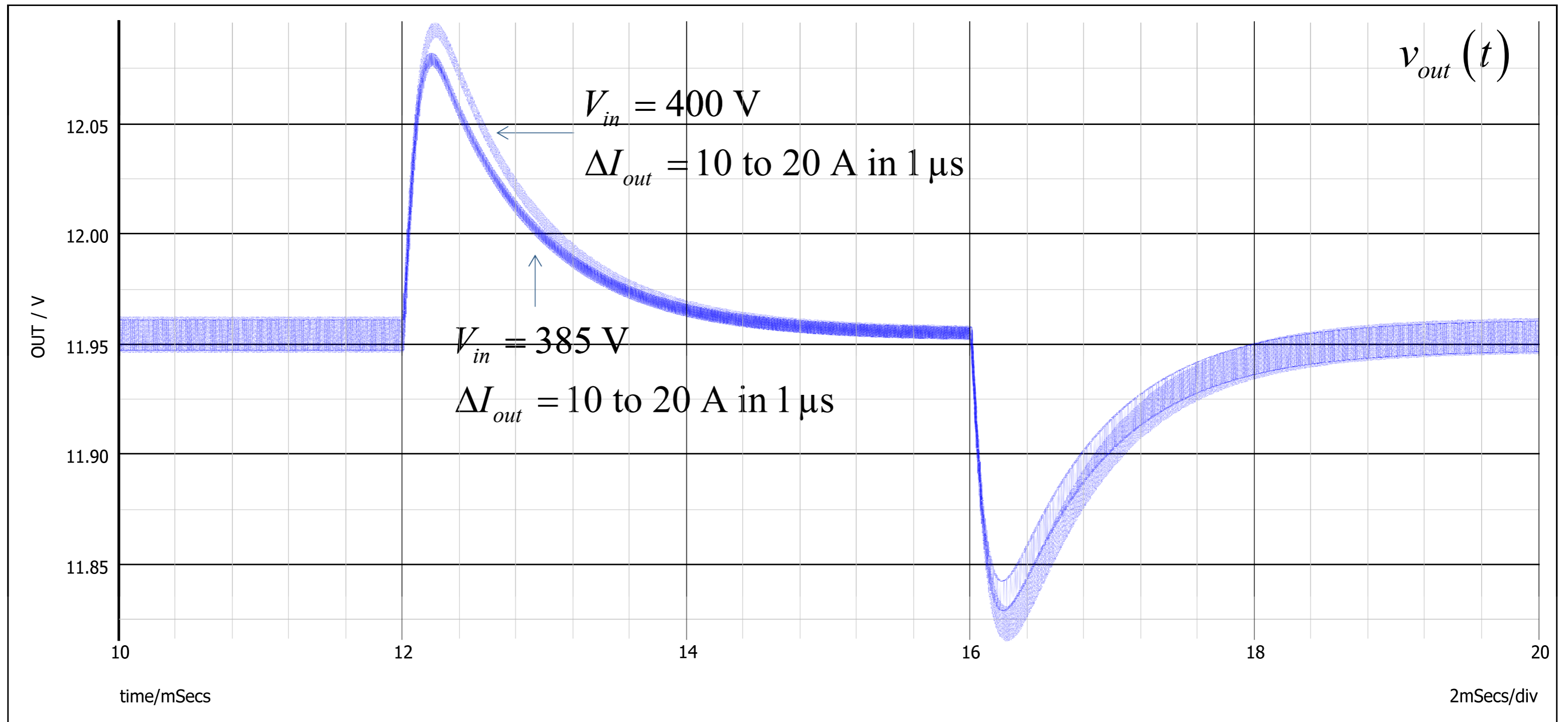

Conclusion

- The compensation of a CM-LLC-based power converter is done via a few steps
 1. Determine the control-to-output transfer function with SIMPLIS[®]
 2. Extract the magnitude and phase at the selected crossover frequency
 3. Build a type-2 compensator with an op-amp or a TL431 and an optocoupler
 4. Make sure the optocoupler is well characterized for its CTR and lo-freq. pole
 5. Check the complete loop gain $T(s)$ at different operating conditions
 6. Sweep all parasitics (ESRs, capacitor etc.) and check there is always a sufficiently-high phase margin
 7. Check load-step response is within design goals in all conditions

