



ON Semiconductor®

Design of a QR Adapter with Improved Efficiency and Low Standby Power

Agenda

1. Quasi-Resonance (QR) Generalities
2. The Valley Lockout Technique
3. The NCP1379/1380
4. Step by Step Design Procedure
5. Performances of a 60 W Adapter Featuring Valley Lockout




Agenda

 
1. Quasi-Resonance (QR) Generalities
2. The Valley Lockout Technique
3. The NCP1379/1380
4. Step by Step Design Procedure
5. Performances of a 60 W Adapter Featuring Valley Lockout

What is Quasi-Square Wave Resonance ?

- MOSFET turns on when $V_{DS}(t)$ reaches its minimum value.
 - Minimizes switching losses
 - Improves the EMI signature





MOSFET turns on in first valley

 

MOSFET turns on in second valley


Quasi-Resonance Operation

 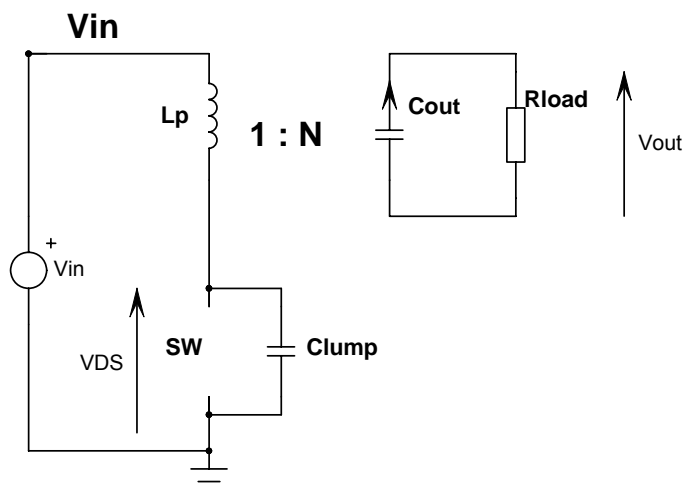- In DCM, V_{DS} must drop from $(V_{in} + V_{reflect})$ to V_{in}
- Because of L_p - C_{lump} network \rightarrow oscillations appear
- Oscillation half period: $t_x = \pi \sqrt{L_p C_{lump}}$



A Need to Limit the Switching Frequency


 
- In a self-oscillating QR, F_{sw} increases as the load decreases



Higher losses at light load if F_{sw} is not limited

- 2 methods to limit F_{sw} :
 - Frequency clamp with frequency foldback
 - Changing valley with valley lockout

Frequency Clamp in QR Converters

  

- ❑ In light load, frequency increases and hits clamp
 - Multiple valley jumps
 - Jumps occur at audible range
 - Creates signal instability

Agenda



1. Quasi-Resonance (QR) Generalities
- 2. The Valley Lockout Technique**
3. The NCP1379/1380
4. Step by Step Design Procedure
5. Performances of a 60 W Adapter Featuring Valley Lockout

The Valley Lockout

- As the load decreases, the controller changes valley (1st to 4th valley in NCP1380)
- The controller stays locked in a valley until the output power changes significantly.




 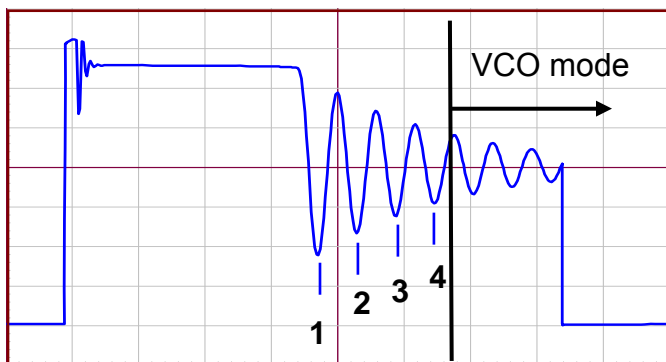- No valley jumping noise
- Natural switching frequency limitation



The Valley Lockout

 - FB comparators select the valley and pass the information to a counter.
- The hysteresis of FB comparators locks the valley.
- 2 possible operating set points for a given FB voltage.



→ V_{FB} increases (P_{OUT} increases)

← V_{FB} decreases (P_{OUT} decreases)

Agenda

1. Quasi-Resonance (QR) Generalities
2. The Valley Lockout Technique
- 3. The NCP1379/1380**
4. Step by Step Design Procedure
5. Performances of a 60 W Adapter Featuring Valley Lockout




NCP1379/1380 Features

- Operating modes:
 - QR current-mode with valley lockout for noise immunity
 - VCO mode in light load for improved efficiency

- Protections

- Over power protection
- Soft-start
- Short circuit protection
- Over voltage protection
- Over temperature protection
- Brown-Out



□ Mass production: Q4 2009

 

QR Mode with Valley Lockout

- **Operating principle:**

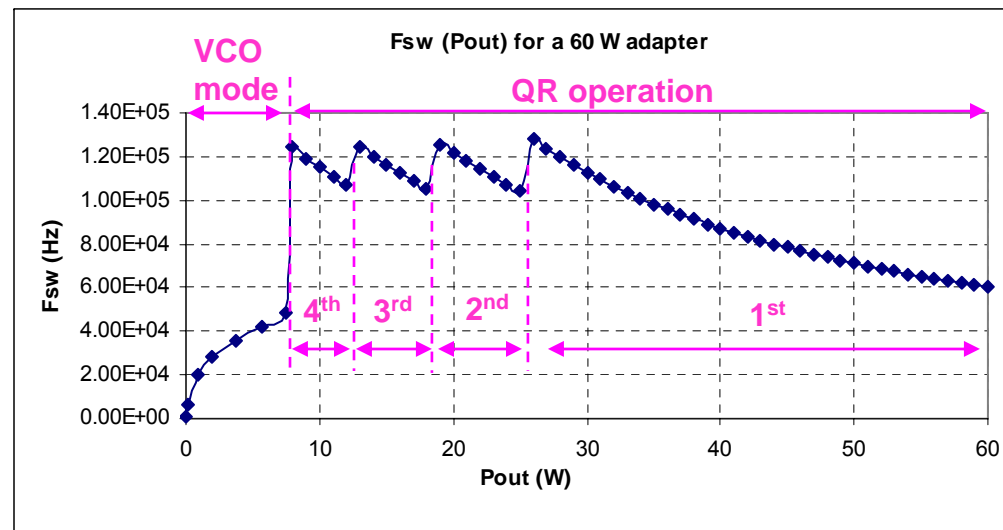 - Locks the controller into a valley (up to the 4th) according to FB voltage.
- Peak current adjusts according to FB voltage to deliver the necessary output power.




- **Advantages**

- Solves the valley jumping instability in QR converters
- Achieves higher min F_{sw} and lower max F_{sw} than in traditional QR converters
- Reduce the transformer size



VCO Mode

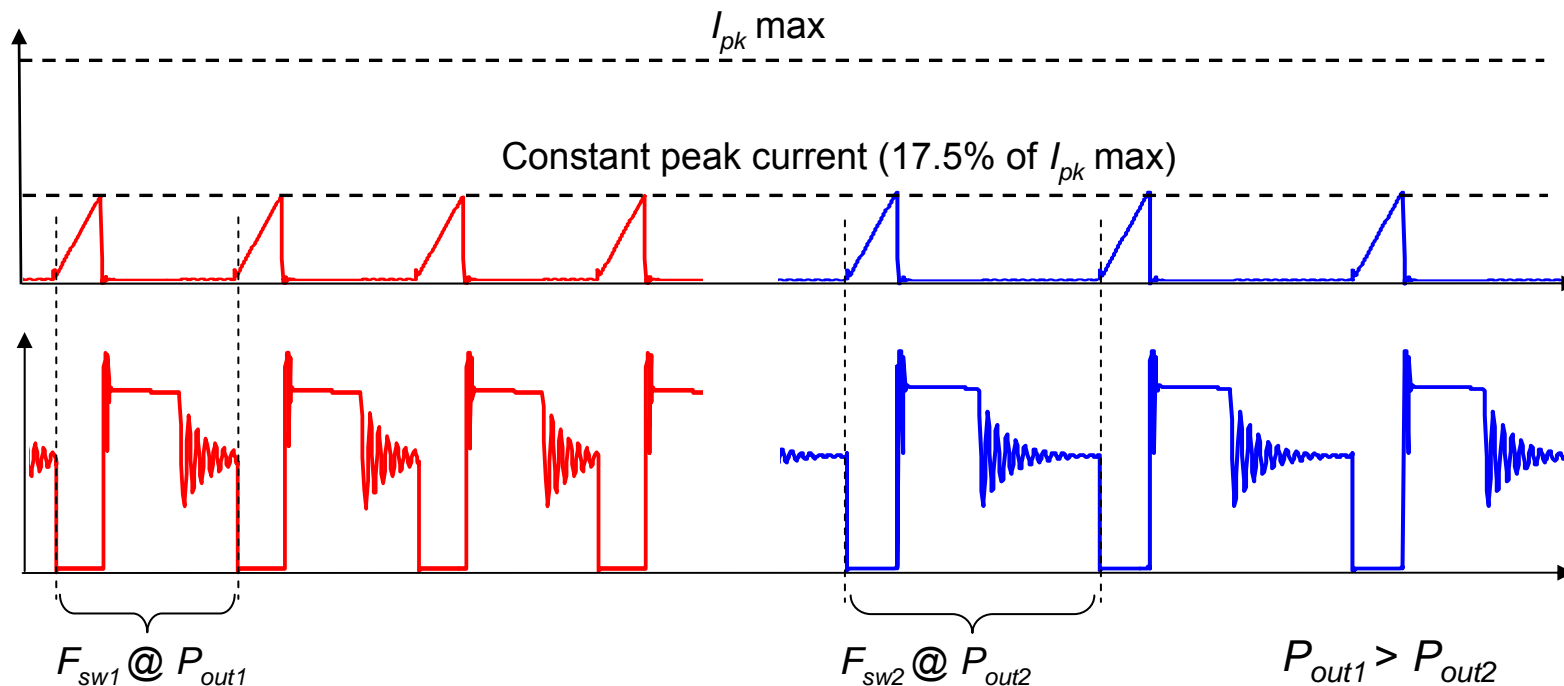- Occurs when $V_{FB} < 0.8\text{ V}$ (P_{out} decreasing) or $V_{FB} < 1.4\text{ V}$ (P_{out} increasing)
- Fixed peak current (17.5% of $I_{pk,max}$), variable frequency set by the FB loop.



Combined ZCD and OPP

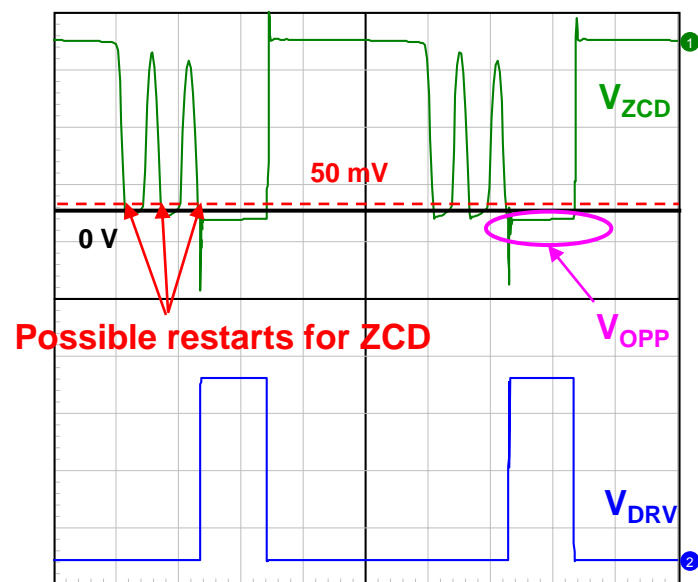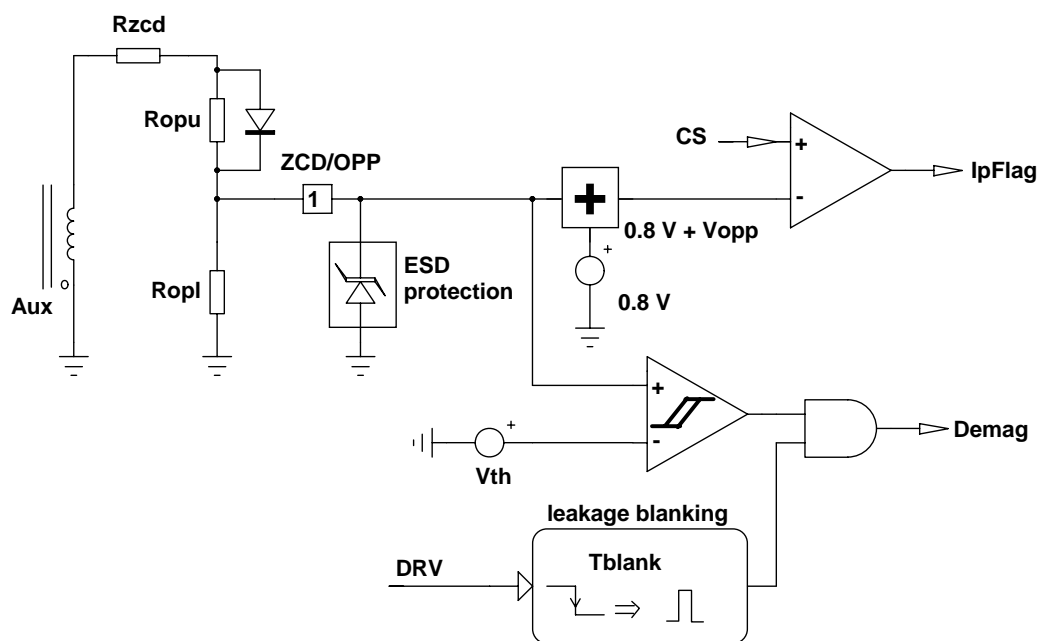- Zero-Crossing Detection (ZCD) and Over Power Protection (OPP) are achieved by reading the Aux. winding voltage
 - ZCD function used during the off-time of MOSFET (positive voltage).
 - OPP function used during the on-time of MOSFET (negative voltage)



NCP1380 Versions

- 4 versions of NCP1380: A, B, C and D

	OTP	OVP	BO	Auto-Recovery Over current protection	Latched Over current protection
NCP1380 / A	X	X			X
NCP1380 / B	X	X		X	
NCP1380 / C		X	X		X
NCP1380 / D		X	X	X	


OTP: Over Temperature Protection

OVP: Over Voltage Protection

BO: Bown-Out


Short-Circuit Protection

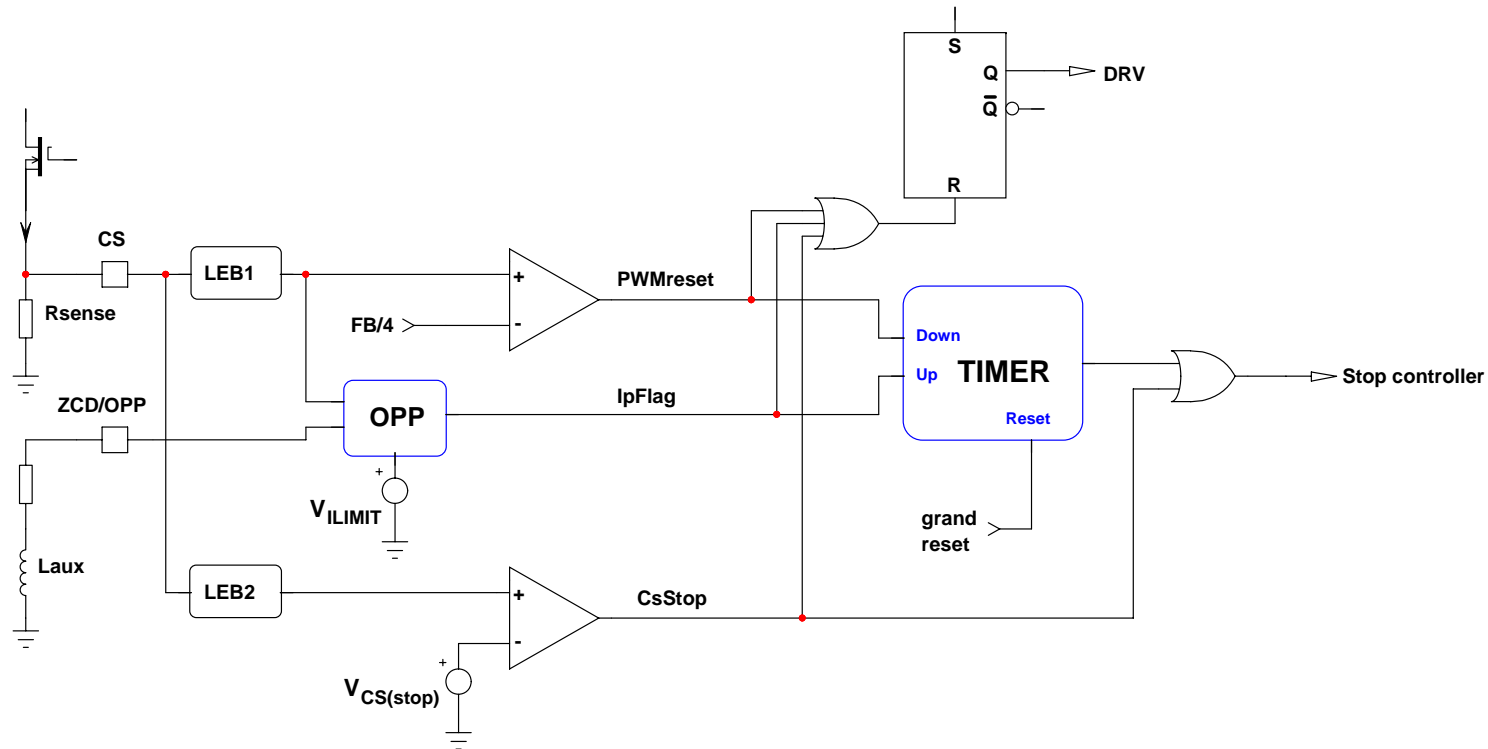- Internal 80 ms timer for short-circuit validation.
- Additional CS comparator with reduced LEB to detect winding short-circuit.
- $V_{CS(stop)} = 1.5 * V_{ILIMIT}$



Short-Circuit Protection (A and C versions)

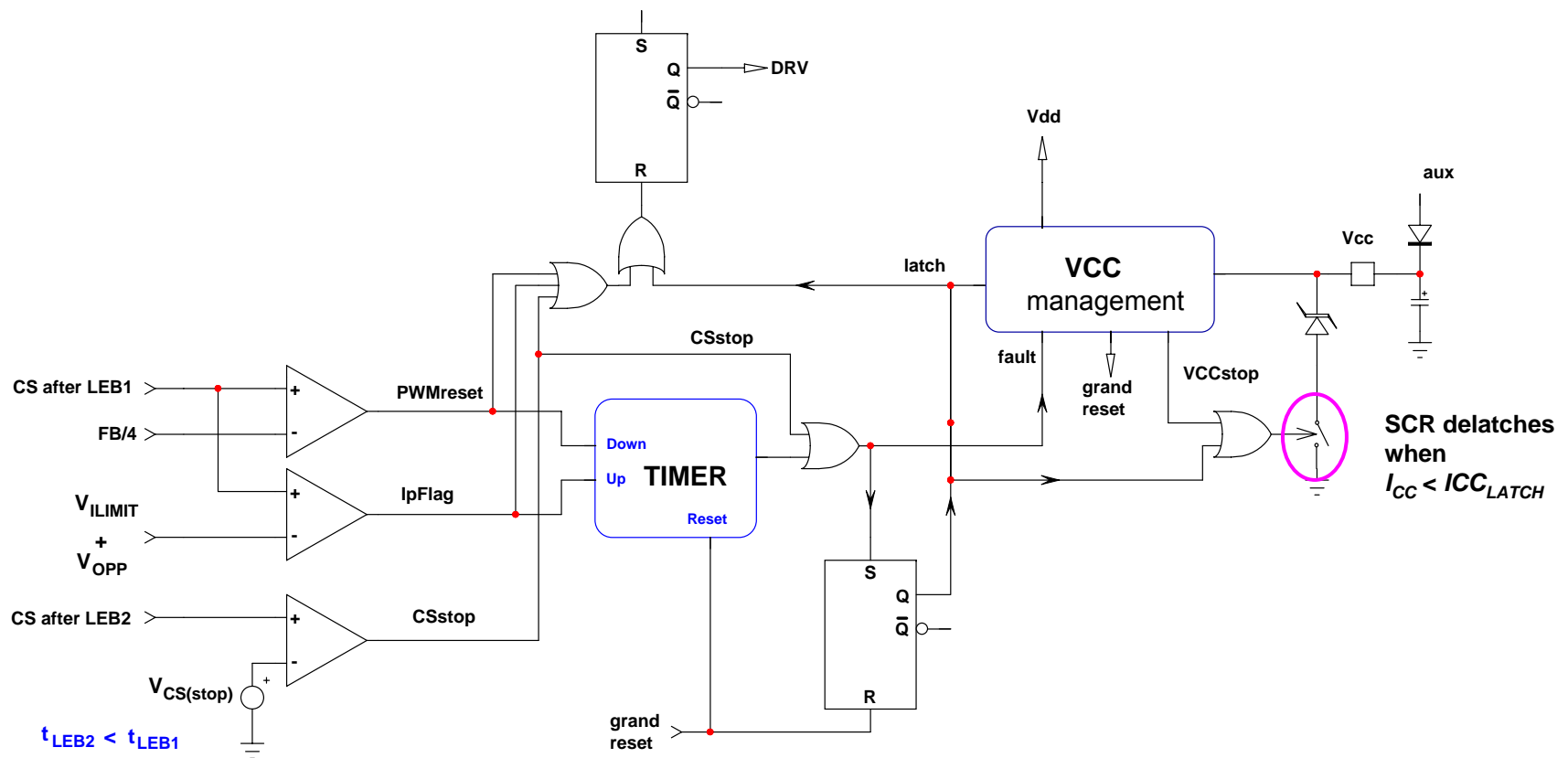
- A and C versions: the fault is latched.
 - V_{CC} is pulled down to 5 V and waits for ac removal.



Short Circuit Protection (B and D)

- Auto-recovery short circuit protection: the controller tries to restart
- Auto-recovery imposes a low burst in fault mode.

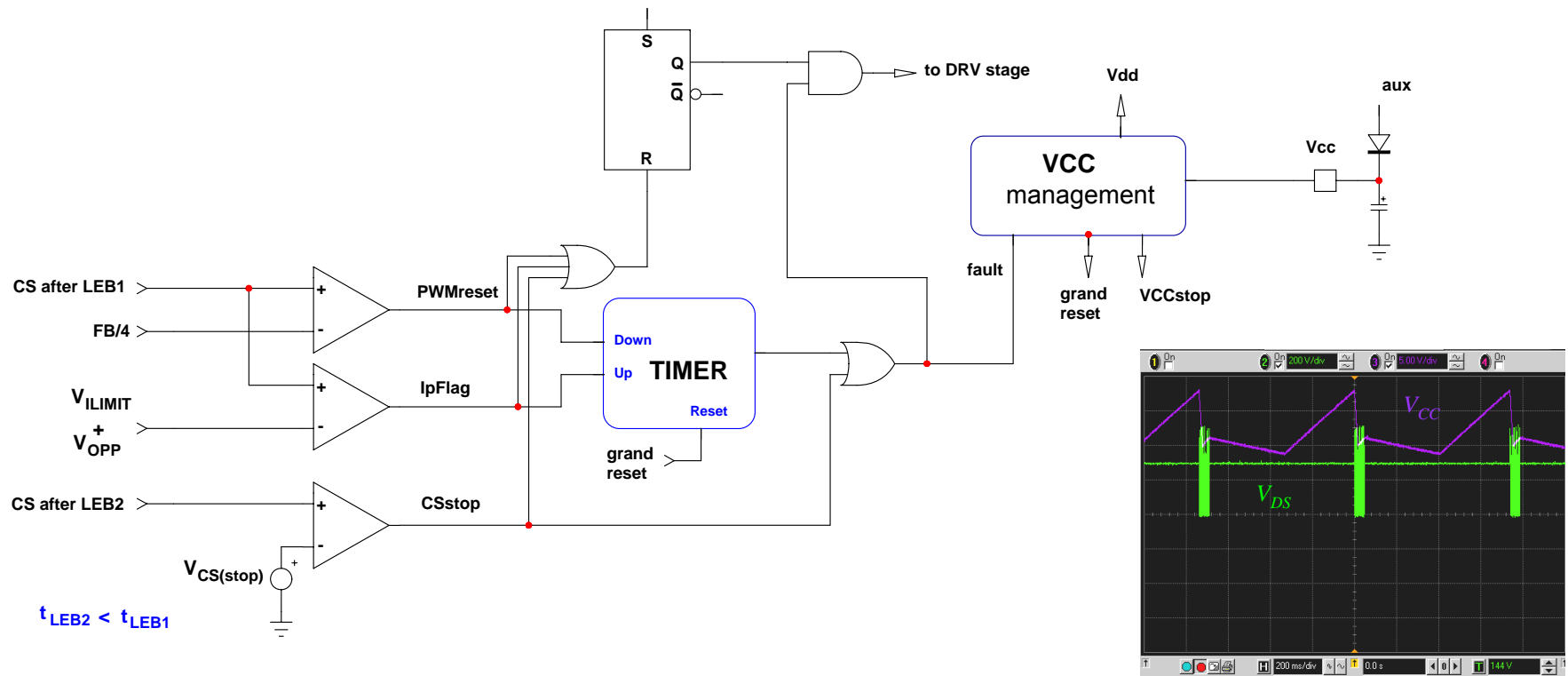
➡ Low average input power in fault condition



Fault Pin Combinations


- OVP / OTP

- NCP1380 A & B versions

 

- OVP / BO

- NCP1380 C & D versions,
NCP1379

 

- OVP and OTP or OVP and BO combined on one pin.
- Less external components needed.

Agenda

1. Quasi-Resonance (QR) Generalities
2. The Valley Lockout Technique
3. The NCP1379/1380
- 4. Step by Step Design Procedure**
5. Performances of a 60 W Adapter Featuring Valley Lockout




Step by Step Design Procedure

- Calculating the QR transformer
- Predicting the switching frequency
- Implementing Over Power Compensation
- Improving the efficiency at light load with the VCO mode
- Choosing the startup resistors
- Implementing synchronous rectification



Design Example

 - Power supply specification:
 - $V_{out} = 19\text{ V}$
 - $P_{out} = 60\text{ W}$
 - $F_{sw,min} = 45\text{ kHz}$ (at $V_{in} = 100\text{ Vdc}$)
 - 600 V MOSFET
 - $V_{in} = 85 \sim 265\text{ Vrms}$
 - Standby power consumption $< 100\text{ mW}$ @ 230 Vrms



Turns Ratio Calculation

- Derate maximum MOSFET BV_{dss} :

$$V_{ds,max} = BV_{dss} k_D \rightarrow k_D: \text{derating factor}$$

- For a maximum bulk voltage, select the clamping voltage:


$$V_{clamp} = V_{ds,max} - V_{in,max} - V_{os} \rightarrow V_{os}: \text{diode overshoot}$$

- Deduce turns ratio:

$$N_{ps} = \frac{N_s}{N_p} = \frac{k_c (V_{out} + V_f)}{V_{clamp}}$$


k_c : clamping coef.

$$k_c = V_{clamp} / V_{reflect}$$

 

How to Choose k_c

 - k_c choice dependant of L_{leak} (leakage inductance of the transformer)
- k_c value can be chosen to equilibrate MOS conduction losses and clamping resistor losses.



$$\left\{ \begin{array}{l} P_{Rclamp} = k_{leak} \frac{P_{out}}{\eta} \frac{k_c}{k_c - 1} \\ P_{MOS,on} = R_{dson} \frac{4P_{out}^2}{3\eta^2 V_{in,min}} \left(\frac{1}{V_{in,min}} + \frac{k_c}{BV_{dss} k_D - V_{in,max} - V_{os}} \right) \end{array} \right.$$

Curves plotted for:



$$R_{dson} = 0.77 \Omega \text{ at } T_j = 110$$

$$P_{out} = 60 \text{ W}$$

$$V_{in,min} = 100 \text{ Vdc}$$

Primary Peak Current and Inductance
  
$$\square P_{out} = \frac{1}{2} L_{pri} I_{pri,peak}^2 F_{sw} \eta \quad \boxed{\text{DCM}}$$



$$\square T_{sw} = \frac{I_{pri,peak} L_{pri}}{V_{in,min}} + \frac{I_{pri,peak} L_{pri} N_{ps}}{V_{out} + V_f} + \pi \sqrt{L_{pri} C_{lump}} \leftarrow C_{oss} \text{ contribution alone.}$$

$$I_{pri,peak} = 2 \frac{P_{out}}{\eta} \left(\frac{1}{V_{in,min}} + \frac{N_{ps}}{V_{out} + V_f} \right) + \pi \sqrt{\frac{2P_{out} C_{lump} F_{sw}}{\eta}}$$

$$L_{pri} = \frac{2P_{out}}{I_{pri,peak}^2 F_{sw} \eta}$$

RMS Current


- Calculate maximum duty-cycle at maximum P_{out} and minimum V_{in} :

$$d_{max} = \frac{I_{pri,peak} L_{pri}}{V_{in,min}} F_{sw,min}$$

- Deduce primary and secondary RMS current value:

$$I_{pri,rms} = I_{pri,peak} \sqrt{\frac{d_{max}}{3}}$$

$$I_{sec,rms} = \frac{I_{pri,peak}}{N_{ps}} \sqrt{\frac{1-d_{max}}{3}}$$

$I_{pri,rms}$ and $I_{sec,rms}$  Losses calculation

Design Example



□ Based on equations from slides 11 to 14:

➤ Turns ratio:
$$N_{ps} = \frac{k_c (V_{out} + V_f)}{B_{Vdss} k_D - V_{in,max} - V_{os}} = \frac{1.3 \times (19 + 0.8)}{600 \times 0.85 - 375 - 10} \Rightarrow N_{ps} \approx 0.25$$

➤ Peak current:
$$I_{pri,peak} = \frac{2P_{out}}{\eta} \left(\frac{1}{V_{in,min}} + \frac{N_{ps}}{V_{out} + V_f} \right) + \pi \sqrt{\frac{2P_{out} C_{lump} F_{sw}}{\eta}}$$

$$= \frac{2 \times 60}{0.85} \left(\frac{1}{100} + \frac{0.25}{19.8} \right) + \pi \sqrt{\frac{2 \times 60 \times 250 p \times 45k}{0.85}} \Rightarrow I_{pri,peak} = 3.32 A$$

➤ Inductance:
$$L_{pri} = \frac{2P_{out}}{I_{pri,peak}^2 F_{sw} \eta} = \frac{2 \times 60}{3.32^2 \times 45k \times 0.85} \Rightarrow L_{pri} = 285 \mu H$$


➤ Max. duty-cycle:
$$d_{max} = \frac{I_{pri,peak} L_{pri}}{V_{in,min}} F_{sw,min} = \frac{3.32 \times 285 \mu}{100} 45k \Rightarrow d_{max} = 0.43$$

➤ Primary rms current:
$$I_{pri,rms} = I_{pri,peak} \sqrt{\frac{d_{max}}{3}} = 3.32 \sqrt{\frac{0.43}{3}} \Rightarrow I_{pri,rms} = 1.26 A$$

➤ Secondary rms current:
$$I_{sec,rms} = \frac{I_{pri,peak}}{N_{ps}} \sqrt{\frac{1-d_{max}}{3}} = \frac{3.32}{0.25} \sqrt{\frac{1-0.43}{3}} \Rightarrow I_{sec,rms} = 5.8 A$$

Predicting the Switching Frequency

 - The controller changes valley as the load decreases.
=> How can we predict the switching frequency evolution as the load varies ?



- Depending upon the power increase or decrease, the FB levels at which the controller changes valley are different => valley lockout

Predicting the Switching Frequency


- Knowing the FB threshold values, we can calculate F_{sw} evolution and the corresponding P_{out} .

$$F_{sw} = \frac{1}{\left(\frac{V_{FB}}{4R_{sense}} + V_{in,dc} \frac{t_{prop}}{L_p} \right) L_p \left(\frac{1}{V_{in,dc}} + \frac{N_{ps}}{V_{out} + V_f} \right) + (1 + 2n) \pi \sqrt{L_p C_{lump}}}$$
$$P_{out} = \frac{1}{2} L_p \left(\frac{V_{FB}}{4R_{sense}} + V_{in,dc} \frac{t_{prop}}{L_p} \right)^2 F_{sw} \eta$$

Replace V_{FB} by the valley thresholds values in the previous slide




Predicting the Switching Frequency

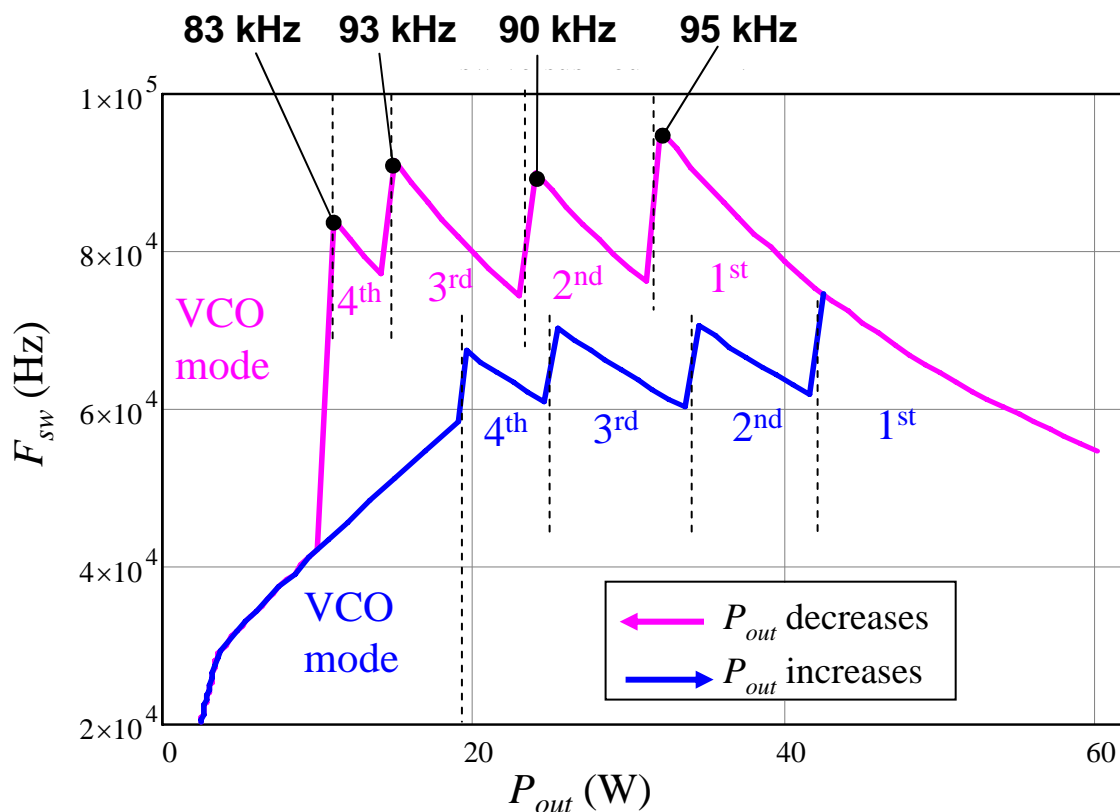- Calculate by hand (using the previous equations) or use the Mathcad spreadsheet to deduce the maxima of the switching frequency => EMI




VCO Mode

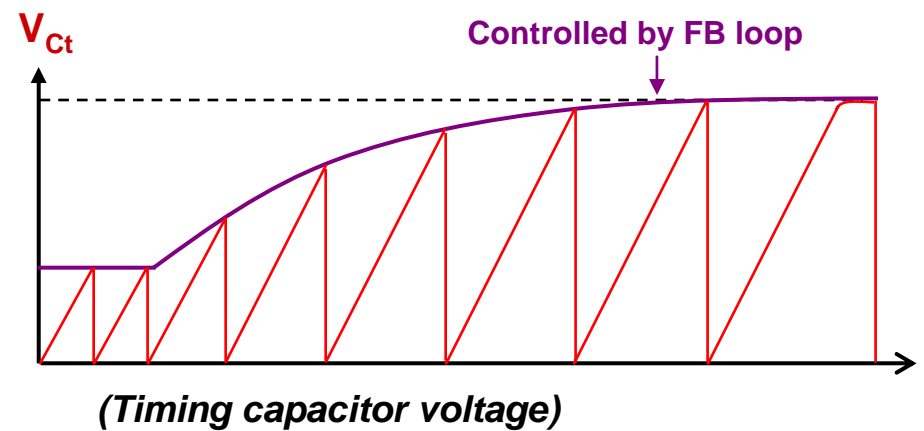 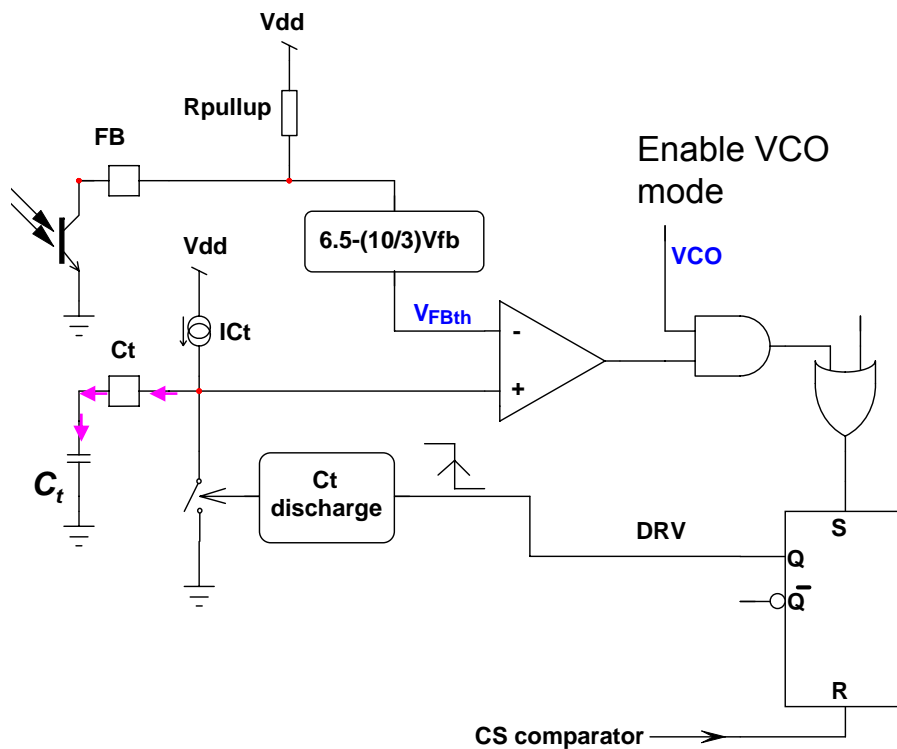- The switching frequency is set by the end of charge of C_t capacitor
- The end of charge of C_t capacitor is controlled by the FB loop



4th Valley to VCO Mode Transition

- Output load slightly decreases:

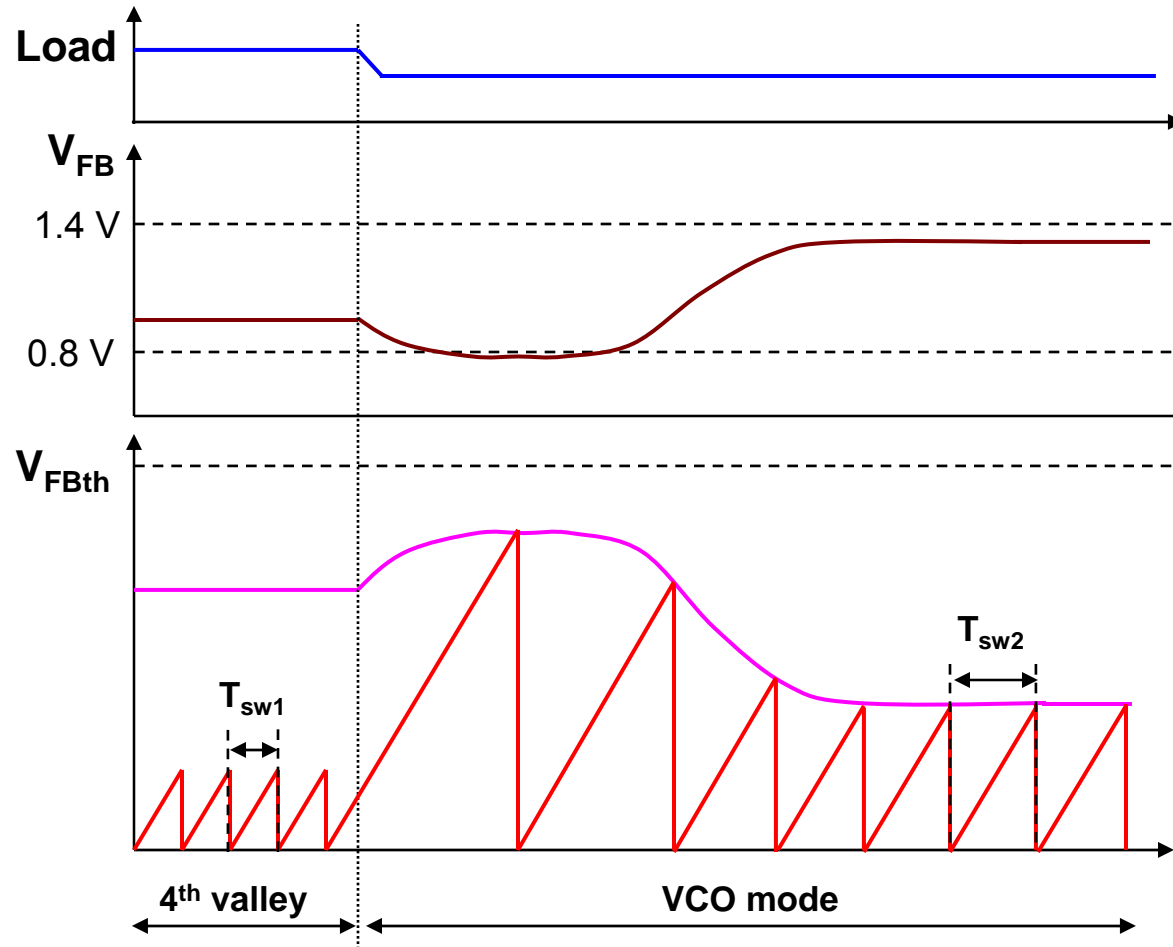

How to Calculate C_t Capacitor ?

- Switching frequency at the end of the 4th valley operation ($V_{FB} = 0.8 \text{ V}$):

$$T_{sw,4th-VCO} = \left(\frac{0.8}{4R_{sense}} + t_{prop} \frac{V_{in,max} \sqrt{2}}{L_p} \right) L_p \left(\frac{1}{V_{in,max} \sqrt{2}} + \frac{N_{ps}}{V_{out} + V_f} \right) + 7\pi \sqrt{L_p C_{OSS}}$$

- T_{sw} gap between 4th valley and VCO mode must not exceed **10 μs** (based on lab experiments) for $V_{FB} = 1.4 \text{ V}$ (hysteresis):

$$T_{sw,VCO} = T_{sw,4th-VCO} + 10 \mu\text{s}$$

- The relationship between V_{FB} and V_{Ct} is:

$$V_{Ct} = 6.5 - (10/3)V_{FB} = 6.5 - (10/3) \times 1.4 = 1.83 \text{ V}$$

$$C_t = \frac{I_{Ct} T_{sw,VCO}}{1.83}$$

C_t Design Example

- Switching frequency at the end of the 4th valley operation :

$$T_{sw,4th-VCO} = \left(\frac{0.8}{4 \times 0.23} + 300n \frac{265\sqrt{2}}{285\mu} \right) 285\mu \left(\frac{1}{265\sqrt{2}} + \frac{0.25}{19+0.8} \right) + 7\pi\sqrt{285\mu \times 250p}$$
$$= 10.7 \mu s$$

- T_{sw} gap between 4th valley and VCO mode must not exceed 10 μs (based on lab experiments):

$$T_{sw,VCO} = T_{sw,4th-VCO} + 10 \mu s = 10.7\mu + 10\mu = 20.7 \mu s$$



- The timing capacitor value is:

$$C_t = \frac{I_{Ct} T_{sw,VCO}}{1.83} = \frac{20\mu \times 20.7\mu}{1.83} = 226 pF$$

- Finally, we choose $C_t = 200 pF$

OPP: How it Works ?

 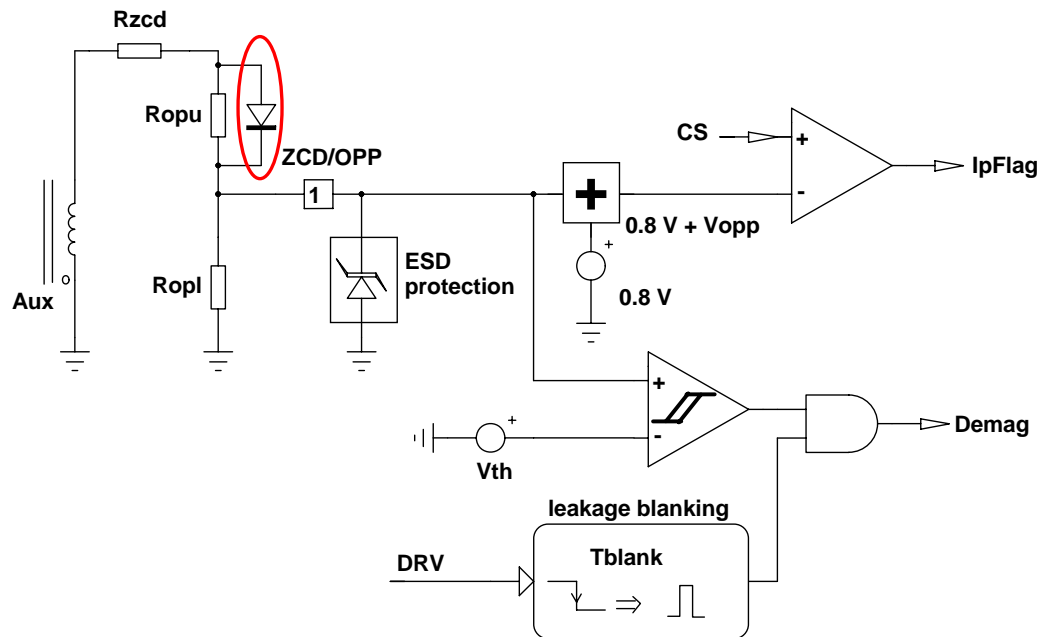- L_{aux} with flyback polarity swings to $-NV_{IN}$ during the on time.
- Adjust amount of OPP voltage with $(R_{zcd} + R_{opu}) // R_{opl}$.
- $V_{CS,max} = 0.8 V + V_{OPP}$
- The diode bypass R_{opu} during the off-time for optimum zero-crossing detection.



OPP Amount Needed for the Design

- Because of the propagation delay, at high line:

$$I_{pk(high)} = \frac{0.8}{R_{sense}} + V_{in,max} \sqrt{2} \frac{t_{prop}}{L_p} \quad \longrightarrow \quad I_{pk(high)} = \frac{0.8}{0.23} + 265\sqrt{2} \frac{600 \times 10^{-9}}{290 \times 10^{-6}} = 4.32 \text{ A}$$

- The switching frequency is:

$$T_{sw(high)} = I_{pk(high)} L_p \left(\frac{1}{V_{in,max} \sqrt{2}} + \frac{N_{ps}}{V_{out} + V_f} \right) + \pi \sqrt{L_p C_{lump}}$$
$$\longrightarrow T_{sw(high)} = 4.32 \times 290 \times 10^{-6} \left(\frac{1}{265\sqrt{2}} + \frac{0.25}{19 + 0.8} \right) + \pi \sqrt{285 \times 10^{-6} \times 250 \times 10^{-12}} = 19.5 \mu s$$

- The power capability at high line is:

$$P_{out(high)} = \frac{1}{2} L_p I_{pk(high)}^2 \frac{1}{T_{sw(high)}} \eta$$
$$\longrightarrow P_{out(high)} = \frac{1}{2} 290 \times 10^{-6} \times 4.32^2 \frac{1}{19.5 \times 10^{-6}} 0.85 = 116 \text{ W}$$

Amount of OPP Voltage Needed

- Limit the output power to $P_{out(limit)} = 70 \text{ W}$ at high line.
- What is the peak current $I_{pk(limit)}$ corresponding to $P_{out(limit)}$?

$$I_{pk(limit)} = \frac{L_p \left(\frac{1}{V_{in(max),dc}} + \frac{N_{ps}}{V_{out} + V_f} \right) + \sqrt{L_p^2 \left(\frac{1}{V_{in(max),dc}} + \frac{N_{ps}}{V_{out} + V_f} \right)^2 - 2 \frac{L_p \eta}{P_{out(limit)}} \pi \sqrt{L_p C_{lump}}}}{\frac{L_p \eta}{P_{out(limit)}}}$$

$$\rightarrow I_{pk(limit)} = \frac{285\mu \left(\frac{1}{375} + \frac{0.25}{19+0.8} \right) + \sqrt{(285\mu)^2 \left(\frac{1}{375} + \frac{0.25}{19+0.8} \right)^2 - 2 \frac{285\mu \times 0.85}{70} \pi \sqrt{285\mu \times 250p}}}{\frac{285\mu \times 0.85}{70}} = 2.67 \text{ A}$$

- Amount of OPP voltage needed:

$$V_{OPP} = 0.8 \left(1 - \frac{I_{pk(limit)}}{I_{pk(max)}} \right)$$


$$\rightarrow V_{OPP} = 0.8 \left(1 - \frac{2.67}{4.32} \right) = 300 \text{ mV}$$

Calculating the OPP Resistors

- The amount of OPP voltage needed to limit P_{out} to 70 W is : $V_{OPP} = 300$ mV
- Resistor divider law:

$$\frac{R_{opu} + R_{zcd}}{R_{opl}} = \frac{N_{p,aux} V_{IN} - V_{OPP}}{V_{OPP}}$$
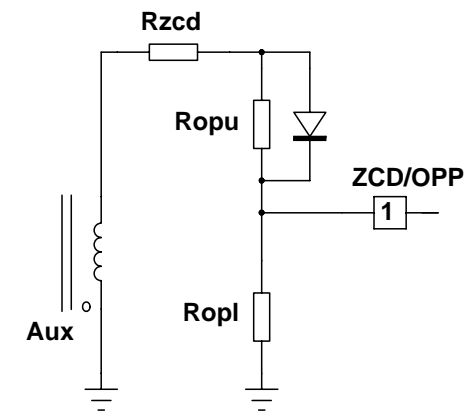
$$\rightarrow \frac{R_{opu} + R_{zcd}}{R_{opl}} = \frac{0.18 \times 375 - 0.3}{0.3} = 224$$



- We choose: $R_{opl} = 1$ k Ω and $R_{zcd} = 1$ k Ω

$$R_{opu} = 221 R_{opl} - R_{zcd}$$

$$\rightarrow R_{opu} = 223 \text{ k}\Omega$$

Why is the OPP Non Dissipative ?

- Input voltage information given by auxiliary winding
- In light load: VCO mode => T_{sw} expands, thus the average current in the resistor bridge decreases


$$I_{bridge,avg} = \frac{1}{R_{zcd} + R_{opu} + R_{opl}} \left(\frac{t_{on}}{T_{sw}} \right) N_{p,aux} V_{IN} + \frac{1}{R_{opu} + R_{opl}} \left(\frac{t_{off}}{T_{sw}} \right) (V_{CC} + V_f)$$

➤ Previous example: $R_{opu} = 220 \text{ k}\Omega$, $R_{opl} = 1 \text{ k}\Omega$, $R_{zcd} = 1 \text{ k}\Omega$

At light load ($P_{out} = 4 \text{ W}$), $t_{on} = 1.2 \text{ }\mu\text{s}$, $t_{off} = 3.6 \text{ }\mu\text{s}$, $T_{sw} = 40 \text{ }\mu\text{s}$

$$I_{bridge,mean} = \frac{1}{220k + 1k + 1k} \frac{1.2\mu}{40\mu} \times 0.18 \times 375 + \frac{1}{220k + 1k} \frac{3.6\mu}{40\mu} 16 = 15 \text{ }\mu\text{A}$$

Startup Network

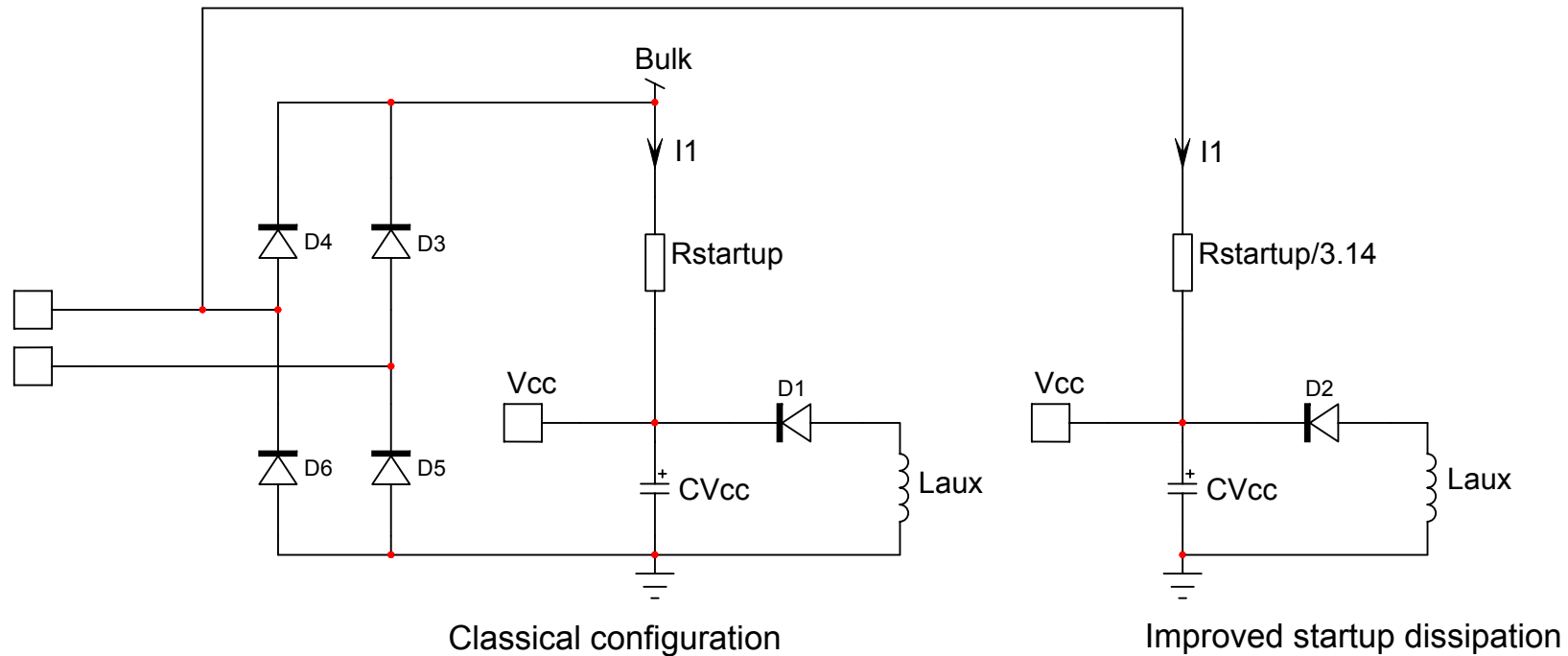

- The startup resistor can either be connected:
 - To the bulk capacitor with $R_{startup}$
 - To the half-wave – for a similar charging current, take $R_{startup}/\pi$


Startup Capacitor Calculation

- $C_{V_{CC}}$ calculated to allow the power supply to close the loop before V_{CC} falls below $V_{CC(off)}$

$$C_{V_{CC}} = \frac{(I_{CC3A} + Q_g F_{sw}) t_{reg}}{V_{CC(on)} - V_{CC(off)}}$$


$$C_{V_{CC}} = \frac{(2.4m + 17n \times 45000) \times 10m}{17 - 9} = 3.9 \mu F$$

We choose $C_{V_{CC}} = 4.7 \mu F$

 

- Needed startup current to charge $C_{V_{CC}}$:
 
$$I_{C_{V_{CC}}} = \frac{V_{CC(on)} C_{V_{CC}}}{t_{startup}} \quad \rightarrow \quad I_{C_{V_{CC}}} = \frac{17 \times 4.7 \mu}{2.8} = 28.5 \mu A$$



Startup Resistor Calculation

- **Bulk capacitor connection**

➤ Resistor calculation:

$$R_{startup} = \frac{V_{in,min} \sqrt{2}}{I_{Cvcc} + I_{CC(start)}}$$

$$R_{startup} = \frac{85\sqrt{2}}{28.5\mu + 15\mu} = 2.76 M\Omega$$

➤ Power dissipation:

$$P_{startup} = \frac{(V_{in,max} \sqrt{2} - V_{CC})^2}{R_{startup}}$$

$$P_{startup} = \frac{(265\sqrt{2} - 16)^2}{2.68M} = 55 mW$$

- **Half wave connection**

➤ Resistor calculation:


$$R_{startup} = \frac{V_{in,min} \sqrt{2}}{I_{Cvcc} + I_{CC(start)}}$$

$$R_{startup} = \frac{85\sqrt{2}/\pi}{28.5\mu + 15\mu} = 880 k\Omega$$

➤ Power dissipation:

$$P_{startup} = \frac{\left(\frac{V_{in,max} \sqrt{2}}{\pi} - V_{CC}\right)^2}{R_{startup}}$$
 
$$P_{startup} = \frac{(265\sqrt{2}/\pi - 16)^2}{880k} = 16 mW$$




Half wave connection saves 39 mW !

Synchronous Rectification

- High rms currents in secondary side → increased losses in the output diode.
- Replace the diode with a MOSFET featuring a very low $R_{DS(on)}$.

+	-
Increased efficiency	Degraded light load and standby power consumption

 

Losses in the Sync. Rect. Switch

$$P_{Qsync} = P_{ON} + P_{Qdiode}$$

- Body diode conduction losses

$$P_{Qdiode} = V_f I_{out} F_{sw} t_{delay}$$

➡ Low if t_{delay} small


- MOSFET conduction losses

$$P_{ON} = R_{DS(on)} I_{sec,rms}^2$$

- Losses in the Sync. Rect. switch are mainly conduction losses.

- Body diode conducts before the MOSFET is turned-on.

➡ No switching losses

 


Choosing the Sync. Rect. MOSFET

- Target around 1 W conduction losses in Sync. Rect. switch to avoid using an heatsink.

$$R_{DSon120} = \frac{1W}{I_{sec,RMS}^2}$$

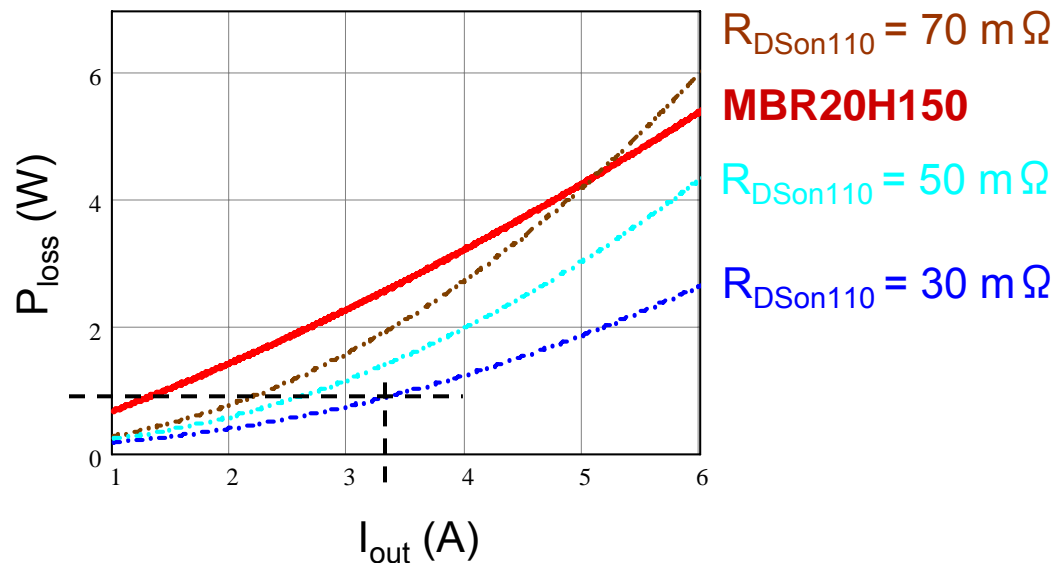$V_{out} = 19V$
 $F_{sw,min} = 45kHz$
Universal mains



60 W QR Sync. Rect. Calculations

□ Body diode losses: $P_{Qdiode} = V_f I_{out} F_{sw} t_{delay} = 0.7 \times 3.2 \times 45000 \times 70n$

$$P_{Qdiode} = 7 \text{ mW}$$

□ MOSFET losses: $P_{ON} = R_{DS(on)120} I_{sec,rms}^2 = 30m \times 5.8^2$

$$P_{ON} = 1 \text{ W}$$



□ Total Sync. Rect. switch losses: $P_{Qsync} = 1 + 0.007 \approx 1 \text{ W}$

□ Losses into the MBR20200 diode: 2.6 W

➡ Power loss saving: 1.6 W

Agenda

1. Quasi-Resonance (QR) Generalities
2. The valley lockout technique
3. The NCP1379/1380
4. Step by step design procedure
5. Performances of a 60 W adapter featuring valley lockout



Startup


- Startup resistor connected to the **bulk rail** ($R_{\text{startup}} = 2.7 \text{ M}\Omega$)
- $T_{\text{startup}} = 2.68 \text{ s}$



- Startup resistor connected to the **half-wave** ($R_{\text{startup}} = 910 \text{ k}\Omega$)
- $T_{\text{startup}} = 2.1 \text{ s}$




Transient Load Step

 

- Load step:
3% to 100% of output load
with a slew rate of 1 A / μ s
- $V_{in} = 230$ Vrms

The overshoot / undershoot is 1% of the nominal value of V_{out}

Short-Circuit

 

- A short-circuit is made at the board output.
- The circuit pulses with a low burst (5%)
- The measured averaged input power is: $P_{in} = 412.4 \text{ mW}$ for $V_{in} = 230 \text{ Vrms}$

Efficiency

115 Vrms			
P_{out} (W)	P_{out} (%)	P_{in} (W)	Eff. (%)
60.6	100	68.65	88.3
45.5	75	51.29	88.7
30.3	50	34.40	88.2
15.2	25	17.61	86.4
1.0		1.30	76.4
0.7		0.94	74.5
0.5		0.69	72.0

Average efficiency

(25, 50, 75, 100% of $P_{out,max}$): **87.9%**


230 Vrms			
P_{out} (W)	P_{out} (%)	P_{in} (W)	Eff. (%)
60.6	100	68.00	89.1
45.5	75	51.43	88.4
30.3	50	34.78	87.3
15.2	25	17.66	86.1
1.0		1.325	75.4
0.7		0.958	73.0
0.5		0.71	70.2

Average efficiency

(25, 50, 75, 100% of $P_{out,max}$): **87.7%**

Improving the No Load Consumption

 - At very low output load, the TL431 bias is removed using a special circuit:



No Load Consumption

- $R_{startup}$ connected to the bulk rail:

- Without TL431 bias:

	115 Vrms	230 Vrms
$P_{out} = 0 \text{ W}$	$P_{in} = 60 \text{ mW}$	$P_{in} = 98 \text{ mW}$

- With TL431 bias:

	115 Vrms	230 Vrms
$P_{out} = 0 \text{ W}$	$P_{in} = 98 \text{ mW}$	$P_{in} = 128 \text{ mW}$

3 M Ω resistor to discharge X2 capacitor included


No Load Consumption

- $R_{startup}$ connected to the half wave:
 - Without TL431 bias, $R_{startup} = 1.1 \text{ M}\Omega$ ($T_{startup} = 2.6 \text{ s @ } 85 \text{ Vrms}$)

	115 Vrms	230 Vrms
$P_{out} = 0 \text{ W}$	$P_{in} = 55 \text{ mW}$	$P_{in} = 90 \text{ mW}$

3 M Ω resistor to discharge X2 capacitor included

Synchronous Rectification Schematic

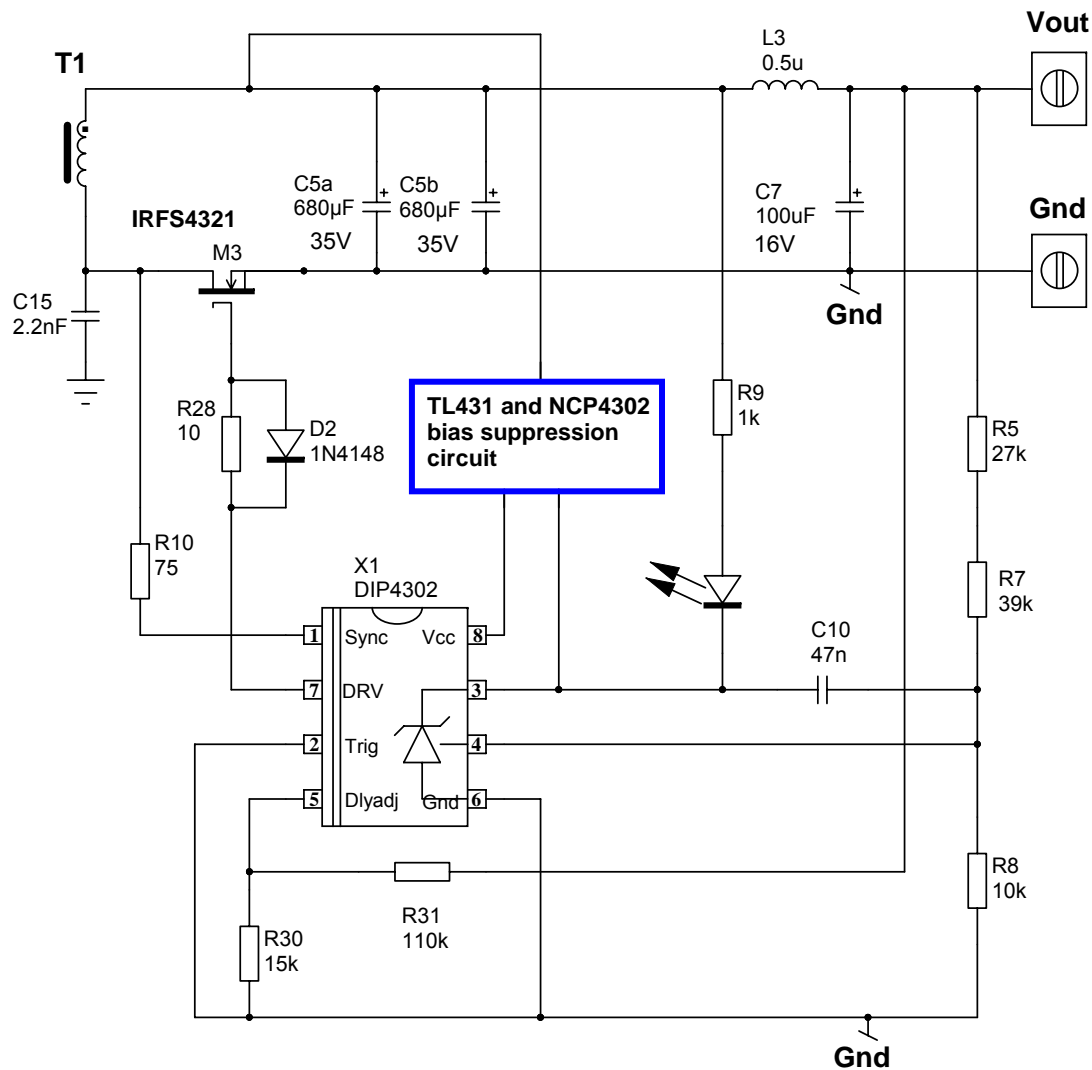

- TL431 and NCP4302 bias removed at light load.

Efficiency and No Load Consumption

115 Vrms			
P_{out} (W)	P_{out} (%)	P_{in} (W)	Eff. (%)
60.5	100	67.18	90.1
45.4	75	50.23	90.5
30.3	50	33.78	89.8
15.2	25	17.39	87.4
1.0		1.319	75.7
0.7		0.945	74.0
0.5		0.690	72.4

230 Vrms			
P_{out} (W)	P_{out} (%)	P_{in} (W)	Eff. (%)
60.5	100	66.48	91.0
45.4	75	50.38	90.1
30.3	50	34.2	88.6
15.2	25	17.48	86.8
1.0		1.368	72.9
0.7		0.992	70.5
0.5		0.737	67.6

Average efficiency (25, 50, 75, 100% of $P_{out,max}$): **89.5%**

Average efficiency (25, 50, 75, 100% of $P_{out,max}$): **89.1%**

❑ No load consumption:

	115 Vrms	230 Vrms
$P_{out} = 0$ W	$P_{in} = 62$ mW	$P_{in} = 107$ mW

Conclusion

- The valley lockout technique allows to solve the valley jumping problem in QR power supplies.
- NCP1380, NCP1379 features:
 - QR current-mode with valley lockout for noise immunity for high load.
 - VCO mode in light load for improved efficiency.
 - OPP, OVP, BO, OTP, soft-start for building safe power supplies
- A complete design method has been presented.
- It is possible to achieve standby power consumption below 100 mW at 230 Vrms with the NCP1380.
- Good efficiency at light load with Sync. Rect if the bias of the TL431 and the Sync. Rec. controller is removed.
- Mathcad spreadsheet and simulations models available.

For More Information

- View the extensive portfolio of power management products from ON Semiconductor at www.onsemi.com
- View reference designs, design notes, and other material supporting the design of highly efficient power supplies at www.onsemi.com/powersupplies

